

第幾回	命題教師	作業範圍	班級	學號	姓名	
3	邱建文	Ch8. 1-Ch. 8. 4	電子二乙			

本次作業完成方式: 獨立完成 與他人討論完成 參考別人完成, 參考 \_\_\_\_\_ 同學(請誠實勾選一項)

1. A  $V_s = 5 \angle 0^\circ$  (V) generator operating at 500 (MHz) with an internal resistance  $50 \Omega$  is connected to a 2-meter-long lossless  $50 \Omega$  air line that is terminated in a  $30 + j30 \Omega$  load. Find (a)  $V(z)$  at a location  $z$  from the generator, (b)  $V_i$  at the input terminals and  $V_L$  at the load, (c) the SWR on the line, (d) the average power delivered to the load.

$V_g = 5 \angle 0^\circ$      $Z_g = 50 \Omega$      $R_0 = 50 \Omega$      $Z_L = 30 + j30 = 30\sqrt{2} \angle 45^\circ$      $l = 2m$   
 $f = 500MHz = 5 \times 10^8 Hz$      $\beta l = \frac{\omega}{c} l = \frac{2\pi \times 5 \times 10^8}{3 \times 10^8} \times 2 = \frac{20\pi}{3}$      $\beta = \frac{10}{3}\pi$      $\approx 10.513\pi$

$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{30 + j30 - 50}{30 + j30 + 50} = \frac{-20 + j30}{80 + j30} \times \frac{80 - j30}{80 - j30} = \frac{-1600 + j3000}{7300} = -0.096 + j0.411 = 0.422 \angle 103.147^\circ$

(a)  $V(z=l) = V_i = \frac{I_L}{2} (Z_L + Z_0) e^{j\beta(l-z)} [1 + \Gamma e^{-2j\beta(l-z)}]$ ,  $I(z=l) = I_L = \frac{V_L}{Z_L} (Z_L + Z_0) e^{j\beta(l-z)} [1 - \Gamma e^{-2j\beta(l-z)}]$   
 $V_g = V_i + I_L Z_0 = I_L (Z_L + Z_0) e^{j\beta(l-z)} [1 + \Gamma e^{-2j\beta(l-z)}]$   
 $V(z) = \frac{V_g}{2} e^{-j\beta z} [1 + 0.422 e^{j(10.513 - \frac{40}{3})\pi} e^{j\frac{40}{3}\pi z}] = 2.5 [e^{-j\frac{40}{3}\pi z} + 0.422 e^{j(\frac{40}{3}\pi z - 0.76)\pi}] (V)$

2. The open-circuit and short-circuit impedances at the input terminals of a 2-meter-long lossless transmission line, which is less than a quarter wavelength, are  $-j50 \Omega$  and  $j200 \Omega$ , respectively. (a) Find  $Z_0$  and  $\beta$  of the line. (b) Without changing the frequency, find  $Z_{in}$  of a short-circuited line with  $l = 4$  m.

(b)  $V_L = V(z) = 2.5 [1 + 0.422 e^{-j(10.513 - 0.513)\pi}] = 2.5 [1 + 0.422 e^{-j10.0\pi}] = 2.5 (0.692 - j0.289)$

$V_L = V(z) = 2.5 [e^{-j0.692\pi} + 0.422 e^{j0.097\pi}] = 18.148 \angle -22.75^\circ (V)$   
 $= 2.5 (-0.106 - j0.989) = 24.81 \angle 83.81^\circ (V)$

(c)  $S = \frac{1 + |\Gamma|^2}{1 - |\Gamma|^2} = \frac{1 + 0.422^2}{1 - 0.422^2} = 2.4602$


(d)  $P_{av} = \frac{1}{2} | \frac{V_L}{Z_L} |^2 R_L = \frac{1}{2} (\frac{24.81}{42.4264})^2 \times 50 = 5.129 (W)$

第二題解答在後面(另一頁)

2 題 請 背 面

3. For the transmission line shown in below,  $f=600MHz$ ,  $v = 2 \times 10^8$  m/s,  $l = 53$  cm,  $Z_0 = 75 \Omega$ ,  $V_g = 20 \angle 40^\circ$ ,  $Z_g = 30 \Omega$ ,  $Z_L = 100 - j300 \Omega$ . Determine (a) the line length as a fraction of a wavelength, (b) the voltage reflection coefficient at the input to the line and at the load, (c) the input impedance to the line, (d) the time-domain voltages at the input to the line and at the load, (e) the average power delivered to the load, and the VSWR.

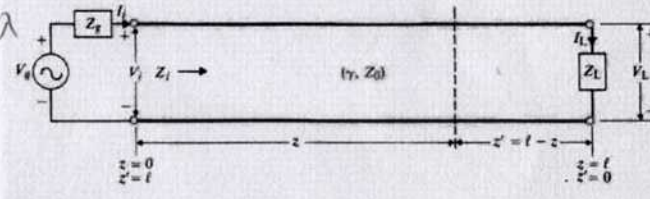(a)  $\lambda = \frac{v}{f} = \frac{2 \times 10^8}{6 \times 10^8} = \frac{1}{3} m$ ,  $l = 0.53m$      $\beta l = \frac{2\pi}{\lambda} \times 1.59\lambda$   
 $\therefore \frac{l}{\lambda} = \frac{0.53}{\frac{1}{3}} = 1.59 \Rightarrow k = \frac{l}{\lambda} = 1.59$



(b)  $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 - j300}{100 - j300 + 75} \times \frac{175 + j300}{175 + j300} = \frac{94375 - j45000}{120625}$

$= 0.78 - j0.373 = 0.86 \angle -25.56^\circ$

$\Gamma_{in} = \Gamma_L e^{-2j\beta l} = (0.86 \angle -25.56^\circ) e^{-j6.36\pi} = 0.86 \angle -90.36^\circ$

(c)  $Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} = 75 \times \frac{100 - j300 + j75 \tan 212.4^\circ}{75 + j(100 - j300) \tan 212.4^\circ} = 75 \times \frac{100 - j252.4}{265.386 + j63.467} = 75 \times \frac{271.488 \angle -68.386^\circ}{272.868 \angle 13.4486^\circ} = 74.67 \angle -81.8353^\circ$

(d)  $V(z=-l) = V_g \times \frac{Z_{in}}{Z_g + Z_{in}} \Rightarrow Z_g + Z_{in} = 30 + 10.597 - j73.864 = 40.597 - j73.864 = 84.285 \angle -61.206^\circ$

$V = \frac{20 \angle 40^\circ}{84.285 \angle -61.206^\circ} = 17.7066 \angle 19.3907^\circ$     (e)  $VSWR = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + 0.86}{1 - 0.86} = 13.28$