

## Attenuator Design Tutorial

### Introduction


Attenuators are devices used to adjust signal levels, to control impedance mismatch and to isolate circuit stages.

### Passive design

Passive attenuators consist of two types 'pi' and 'Tee' attenuators.

#### (1) Pi Attenuator

The circuit for the Pi attenuator is shown in Figure 1.

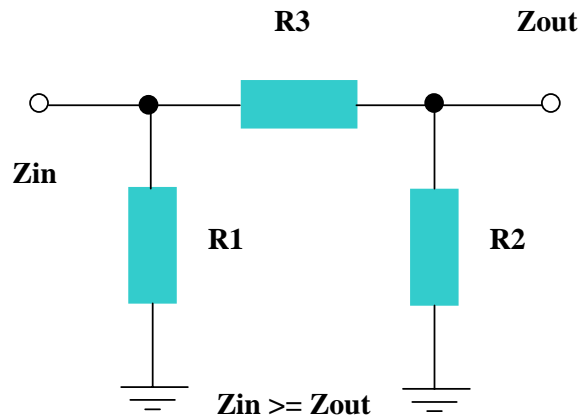

**Figure 1 Pi Attenuator**

$$R3 = \frac{1}{2} \left( 10^{\frac{L}{10}} - 1 \right) \sqrt{\frac{Z_{in} * Z_{out}}{10^{\frac{L}{10}}}}$$

$$R2 = \frac{1}{\frac{10^{\frac{L}{10}} + 1}{Z_{out} \left( 10^{\frac{L}{10}} - 1 \right)} - \frac{1}{R3}}$$

$$R1 = \frac{1}{\frac{10^{\frac{L}{10}} + 1}{Z_{in} \left( 10^{\frac{L}{10}} - 1 \right)} - \frac{1}{R3}}$$


Where L = desired loss in dB

Zin = desired input impedance (ohms)

Zout = desired output impedance (ohms)

**(2) Tee Attenuator**

The circuit for the T attenuator is shown in Figure 2

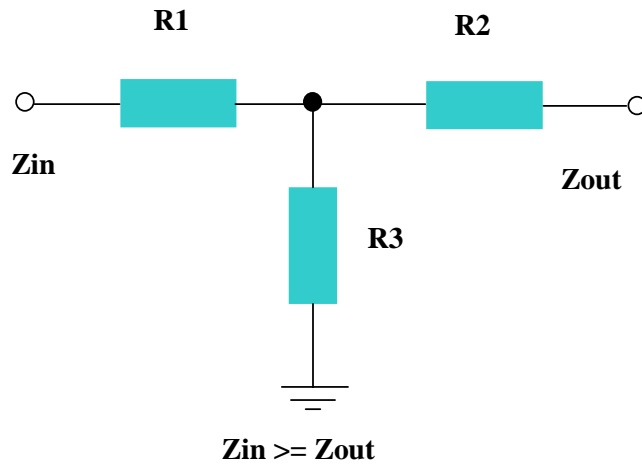

**Figure 2 Circuit of the T attenuator**

$$R3 = \frac{2\sqrt{Z_{in} * Z_{out} * 10^{\frac{L}{10}}}}{10^{\frac{L}{10}} - 1}$$

$$R2 = \frac{10^{\frac{L}{10}} + 1}{10^{\frac{L}{10}} - 1} Z_{out} - R3$$

$$R2 = \frac{10^{\frac{L}{10}} + 1}{10^{\frac{L}{10}} - 1} Z_{in} - R3$$


Where L = desired loss in dB

Zin = desired input impedance (ohms)

Zout = desired output impedance (ohms)

**(3) Bridged T Attenuator**

The circuit of the bridge T attenuator is shown in Figure 3

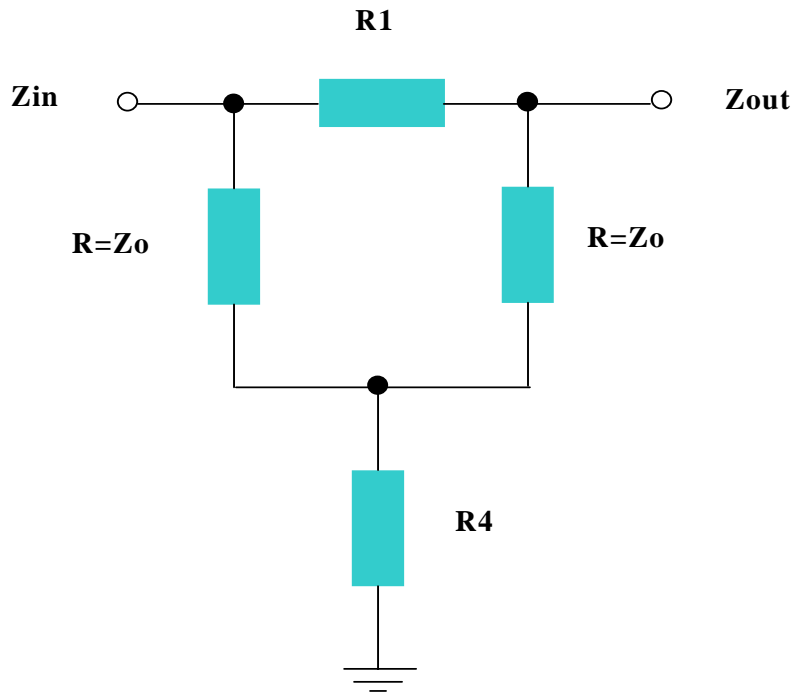

**Figure 3 Circuit of the Bridged-T attenuator**

$$R1 = Z_0 \left( 10^{\frac{L}{20}} - 1 \right)$$

$$R4 = \frac{Z_0}{10^{\frac{L}{20}} - 1}$$

Where L = desired loss in dB

Zin = desired input impedance (ohms)

Zout = desired output impedance (ohms)

Zo = Circuit characteristic impedance (ohms)


This circuit is commonly used with PIN diodes to form an electronic attenuator, as only two variable resistors are required (instead of 3 for the Pi or T attenuators).

**Narrow-band active variable attenuator design**

If we use the bridged-T network as a basis of an active attenuator we need to add the bias circuits to complete a basic design. Figure 4 Shows the complete electronic bridged-T attenuator together with the correct bias circuits.

The circuit has been set up such that the currents through D1 and D4 are inverse to each other ie when D1 current is high then D4 current is low and visa versa. When the PIN diode is on (high current)is has low attenuation. So when D1 is on and D4 is off, the two R's and D4 are out of circuit and the attenuation through the circuit is low.

When D1 is off and D4 is on the signal instead of passing through D1 will pass to ground via D4 and the circuit will be in a high attenuation state. Intermediate currents through D1 & D4 will allow attenuation from max to min.

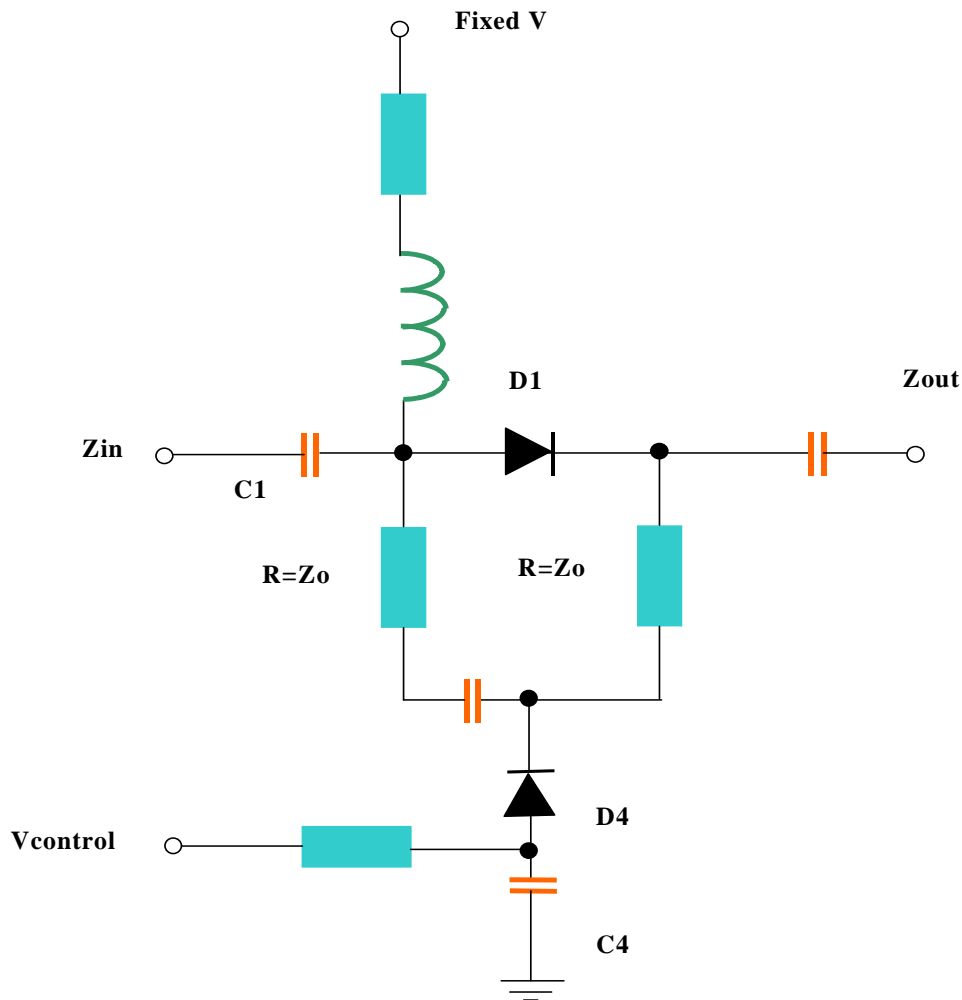

**Figure 4 Electronic version of the Bridged T attenuator, where resistors R1 & R4 have been replaced by PIN diodes D1 and D4.**

A typical microwave PIN diode is from Agilent HSMP-3810 has a low resistance of 10 ohms and a high resistance of 1500 ohms.

Therefore, using such a device we could design an attenuator with the following min and max attenuations:-

Minimumattenuation


$$L = 20\log\left(\frac{R1}{50} + 1\right) = 20\log\left(\frac{10}{50} + 1\right) = 1.58\text{dB approx}$$

Where L = desiredloss in dB

Maximumattenuation

$$L = 20\log\left(\frac{R1}{50} + 1\right) = 20\log\left(\frac{1500}{50} + 1\right) = 29\text{dB approx}$$

Using the data sheet it is possible to design a model in ADS and the resulting circuit is shown in Figure 5.

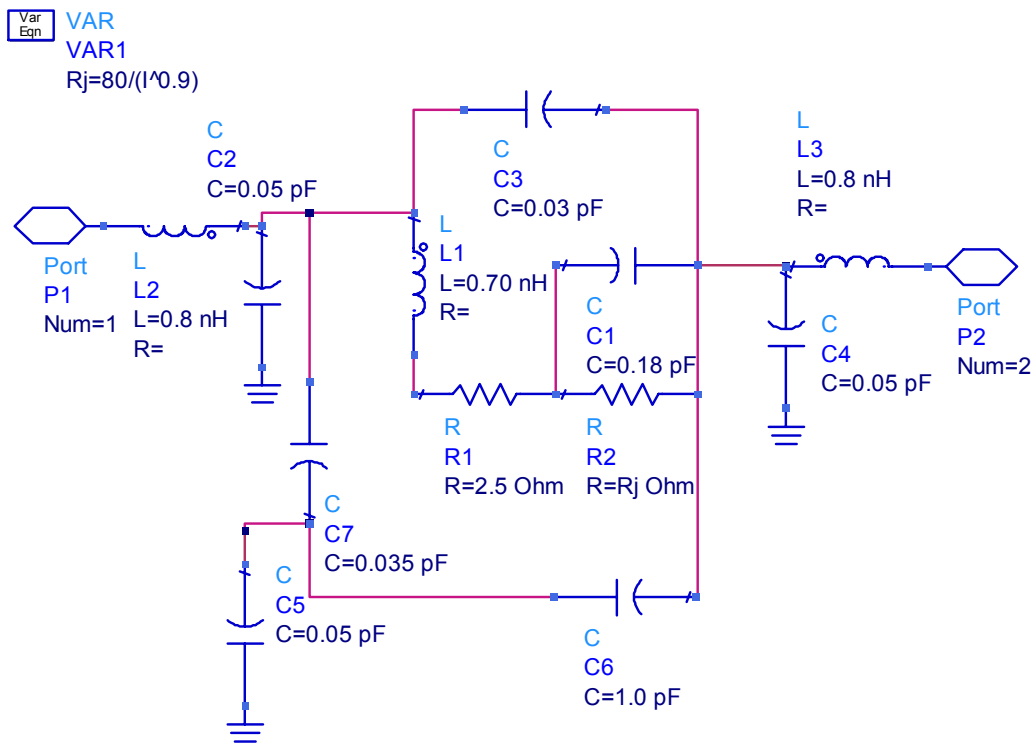


**Figure 5 ADS sub-circuit of the PIN diode Agilent HSMP-3810. The diode chip consists of R1, C2 and the variable resistor R2 defined by the equation Rj. When designing sub-circuits in ADS you need to select File-Design Parameters and add any variables you want to pass through a higher simulation in this case I has been added and given a default value of 1mA. You can also switch to create/edit schematic symbol (under the view menu) to draw the component symbol.**

The Bridge-T circuit was set up in ADS to include an S-parameter simulation box set to 2-2GHz and is shown in .

**S-PARAMETERS**


S\_Param  
SP1  
Start=1 GHz  
Stop=2.0 GHz  
Step=2 MHz

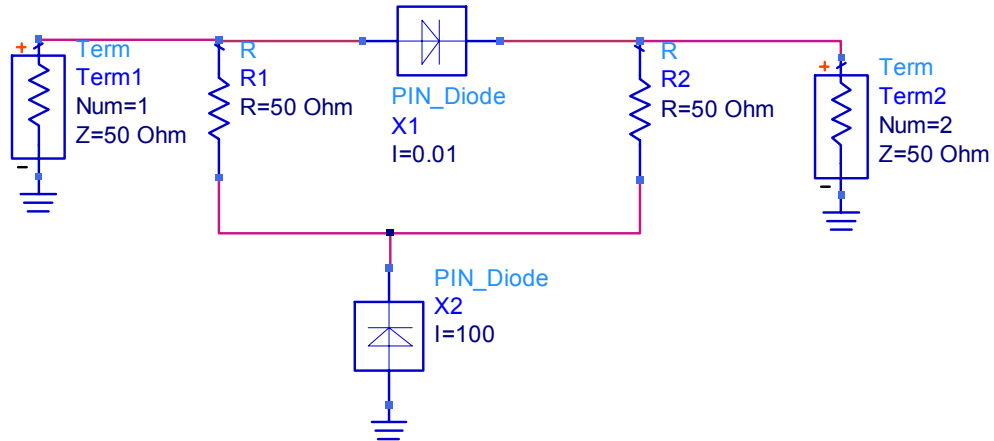

**Figure 6 ADS schematic of the bridged-T attenuator. If you push into either X1 or X2 you will see the circuit shown in Figure 5. The values of I are set to 0.01 and 100 and then swapped to view the resulting simulations.**

The two resulting simulations of the circuit shown above in Figure 6 are shown in Figure 8 (Minimum attenuation state) and Figure 9 (High attenuation state).

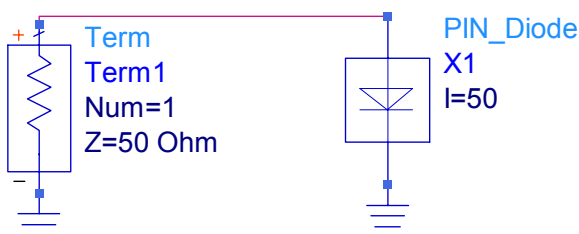Note how the slope changes with frequency and attenuation. It's possible to 'match' the PIN diodes using lumped or distributed matching circuits to minimise this slope. If look at the input return loss of the diode at mid-bias using the circuit shown in Figure 7, we obtain the smith chart shown in




**S-PARAMETERS**


S\_Param  
SP1  
Step=1.0 GHz  
Center=1.5 GHz  
Span=100 MHz



Figure 7 ADS schematic to measure the input return loss of the PIN diode at 1.5GHz.

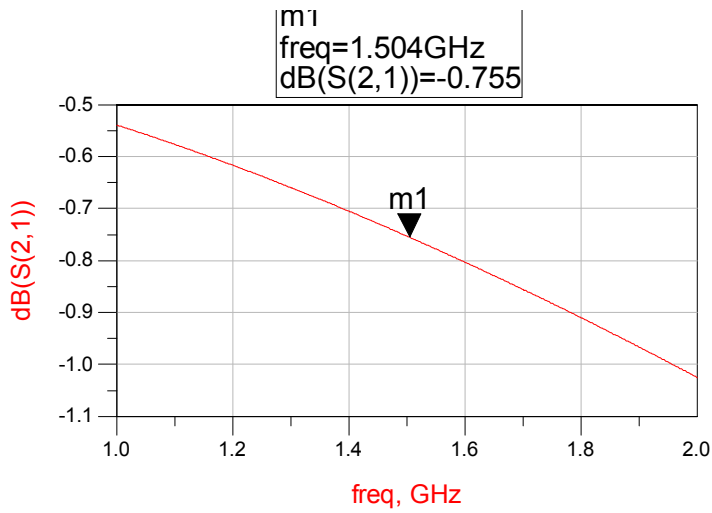

**Figure 8 Minimum attenuation state with D1 set to 100mA and D4 set to 0.01mA (ie off)**

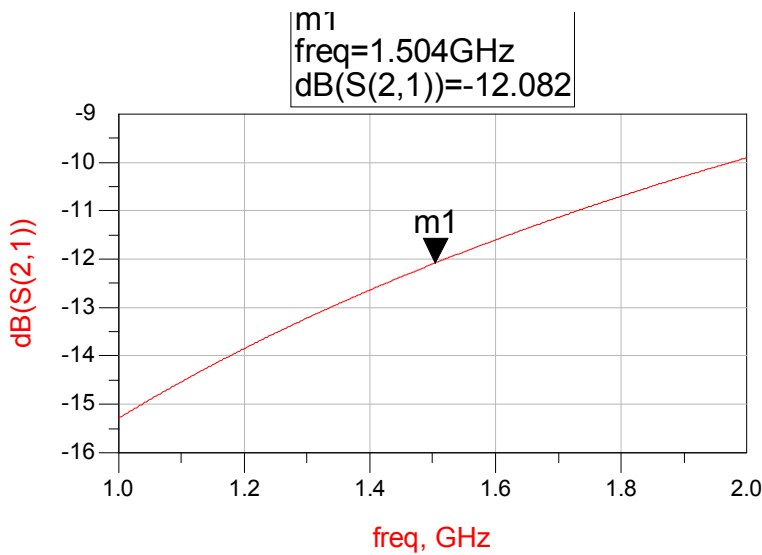


**Figure 9 High attenuation state with D1 set to 0.01mA (ie off) and D4 set to 100mA.**

Figure 10 Shows the input return loss of the Pin diode showing that it has inductance at 1.5GHz of some 22 ohms this equates to an inductance of ~ 2nH. So if we resonate this inductance with a capacitor of 4pF we should improve our frequency response. The new set of plots is shown in





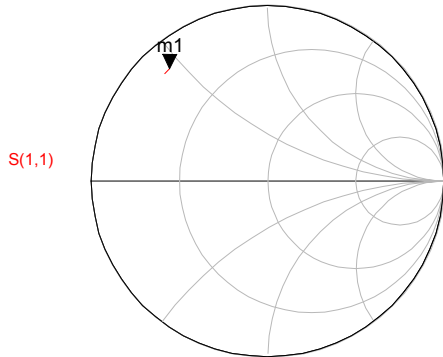m1  
freq=1.550E9Hz  
S(1,1)=0.846 / 130.962  
impedance = Z0 \* (0.101 + j0.452)



freq (1.450GHz to 1.550GHz)

Figure 10 Input return loss of the PIN diode showing that at 1.5GHz it has an inductive impedance with a value of  $+j0.452 \times 50 = 22$  ohms.

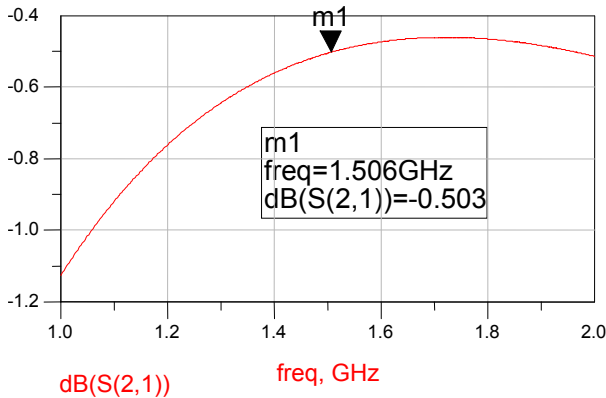


Figure 11 Minimum attenuation state with series 4pF capacitors added to each Pin diode.

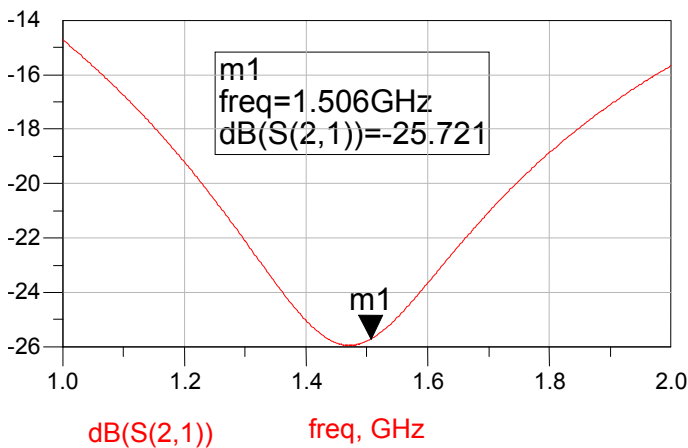


Figure 12 Maximum attenuation state with series 4pF capacitors added to each PIN diode.

Clearly such circuits have narrow band attenuation and for broader band type circuits large couplers can be used:


**Broad-band active variable attenuator design**

In many situations it is better to have a broad-band attenuator that can be used at many different frequencies. So for example assume we to design a broad-band attenuator with the following parameters:-

Parameter		Units
Frequency range	6 to 10	GHz
Minimum attenuation	<1	dB
Maximum attenuation	>20	dB
Frequency ripple	< 2	dB pk-pk
Return loss	< -10	dB

The first thing we need to do is select a Pin diode that is designed for these frequencies. In this case a MaCom MA4P202 PIN diode was chosen as it's operating frequency range is specified as 50MHz to 18GHz and is available in chip form.

The model of the Pin is very simple and is shown in Figure 13. The variable resistance is actually non-linear but for the purposes of this example we will only be looking at max and min attenuation cases ie currents of 20uA and 10mA.

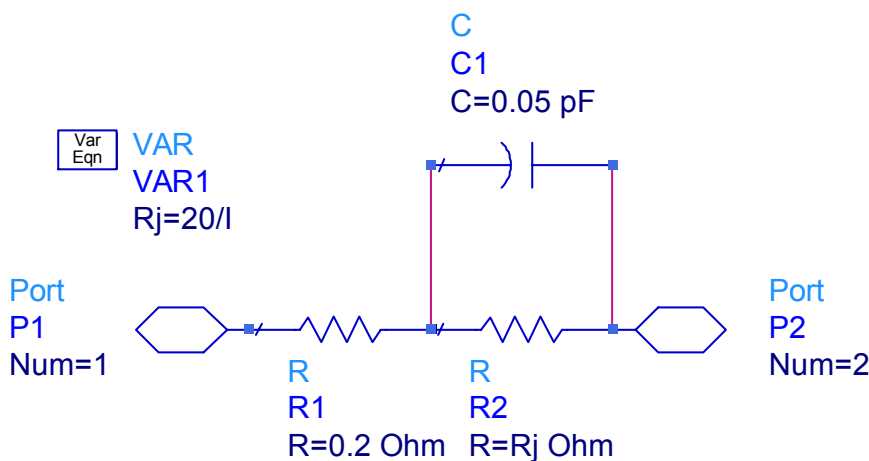

**Figure 13 Simple model of the MACOM MAP202 PIN diode in chip form. The full circuit of the broad-band attenuator circuit is shown in Figure 14.**

The circuit is configured as a balanced attenuator with the use of the two Lange couplers – as with balanced amplifiers the poor return loss of the PIN diodes is greatly improved using quadrature hybrids. The inductors LB are the bond wires required to connect the chip to micro-strip lines either side of it (the other connection to ground is made on the underside of the PIN diode).

Capacitor CB is added to cancel out the effects of the bond wires and is set as an optimised variable as are the Lange variables Finger\_spacing, Finger\_length and Lange length.


The Msub box defines the micro-strip substrate the circuit is to be made on – in this case Alumina 10 thou (0.25mm) thick.

There are three goals each tied to the S-parameter simulation 'SP1'. Each goal has a specified parameter in these cases dB S-parameters, a frequency range and a minimum/maximum goal.

The OPTIM box is used to specify the optimiser ie how many runs, the type of optimisation etc.

When a simulation is run and completed and the results satisfactory – update optimisation variables under the simulate menu to update the schematic – you can then check the simulation after disabling the OPTIM dialogue.

The first case to be run was minimum attenuation setting and for this the diodes were set to 20uA through the Ibias variable. The results of the optimisation are shown in

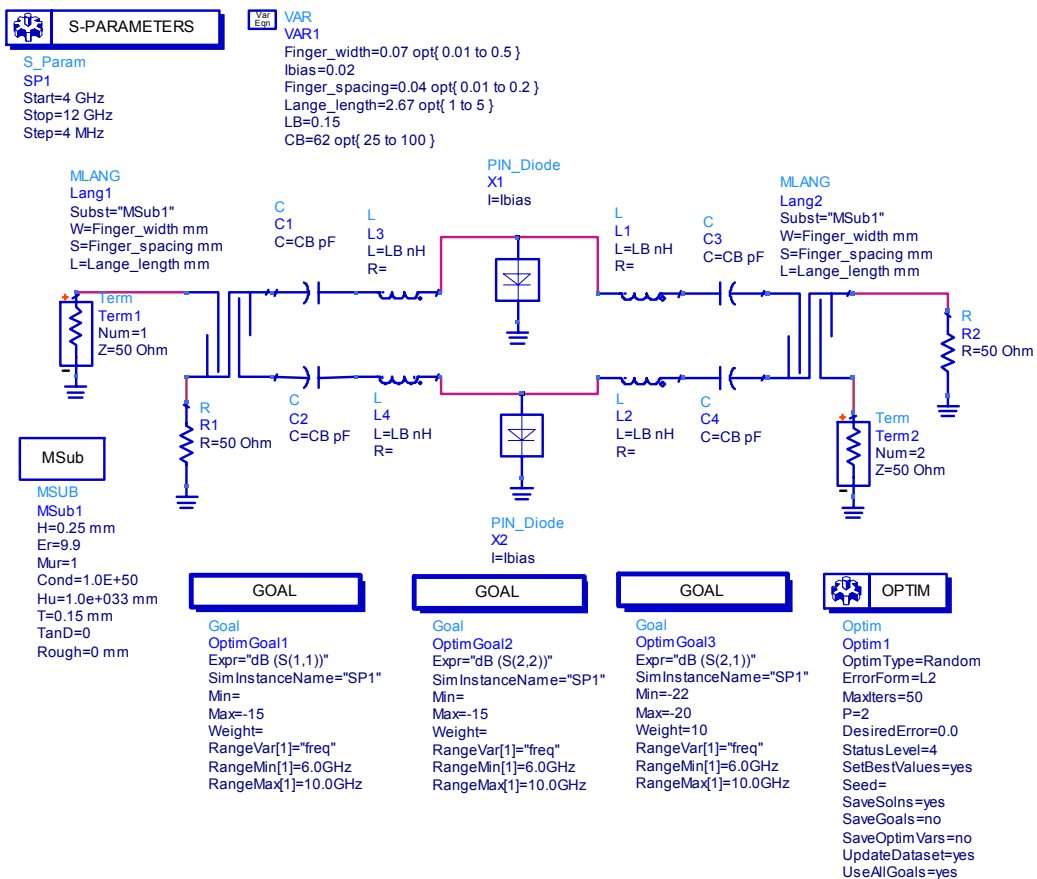

**Figure 14 ADS simulation of the broad-band attenuator – see text for details on all the elements.**


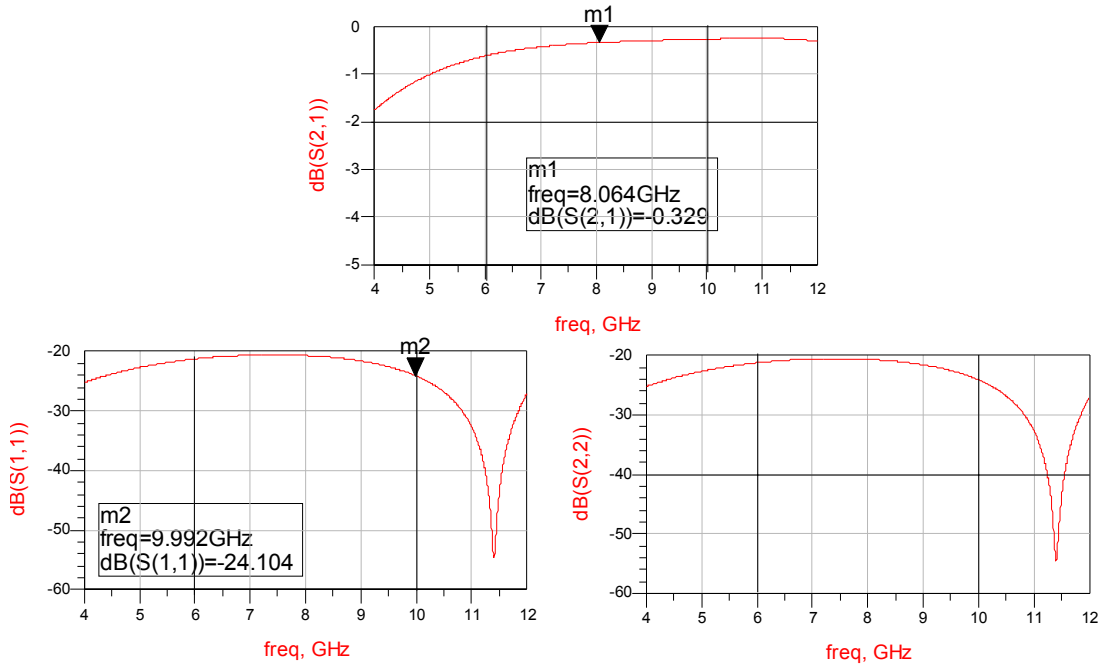


Figure 15 Minimum attenuation result after optimisation

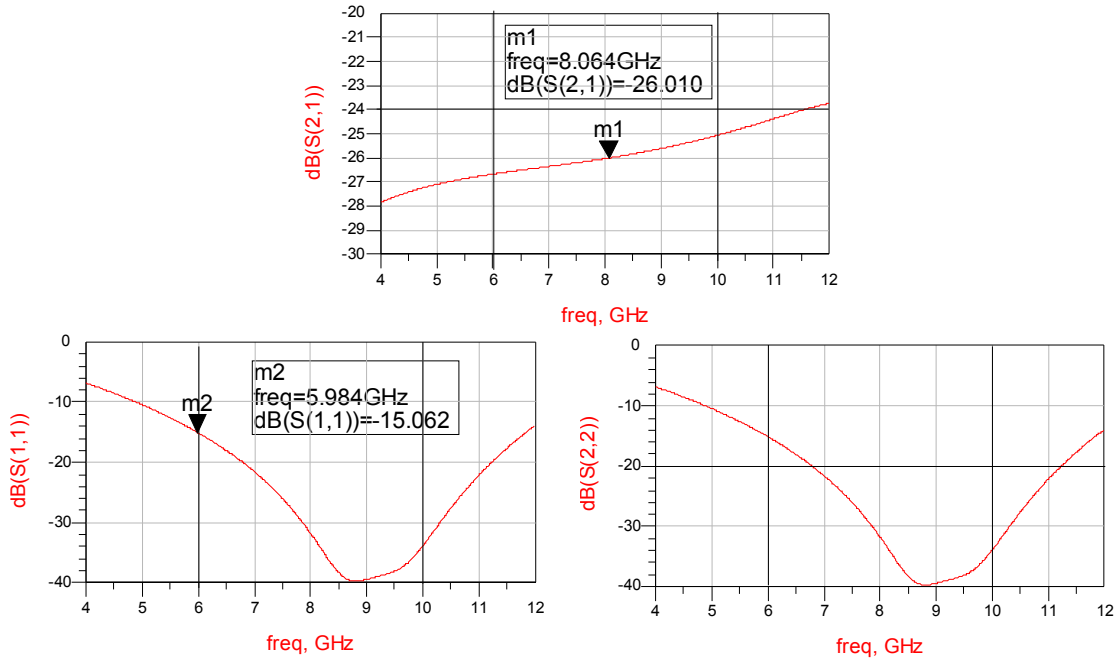


**Figure 16 Maximum attenuation result, using values obtained during the minimum attenuation optimisation. The return losses have degraded but are still > 15dB as required by our specification.**

### Summary

The broad-band attenuator uses Lange couplers to provide a wide bandwidth attenuator capable of providing < 1dB loss over the pass-band with return losses >15dB as shown in Figure 15. In maximum attenuation state, the attenuator can insert >20dB of attenuation with again >15dB return loss as shown in Figure 16.

### Broad-band active switched attenuator design

In some circumstances we want to be able to switch in a fixed amount of attenuation. The easiest way of doing this is to use two SPDT FET switches and a broad-band fixed attenuator as shown in.

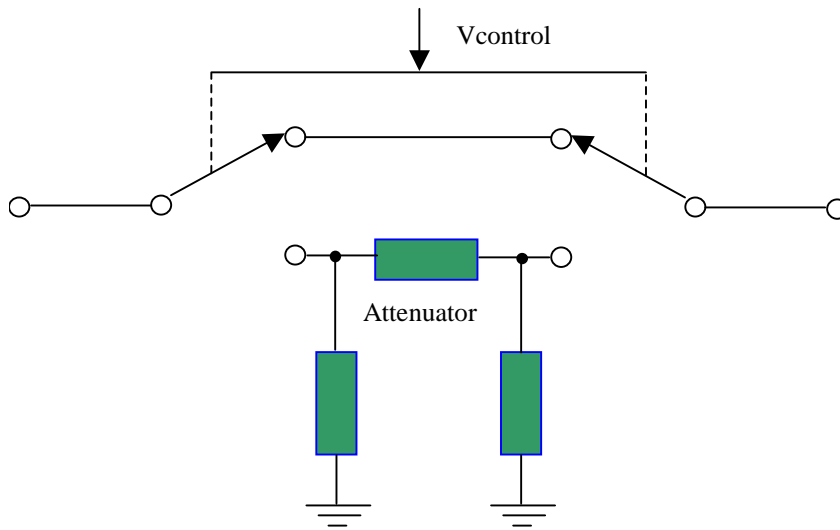

**Figure 17 Switching fixed attenuator circuit – used in gain step applications where the switches are formed by GaAs SPDT switches eg MA4AGSW2 50MHz to 70GHz SPDT MMIC.**

## 射频和天线设计培训课程推荐

易迪拓培训([www.edatop.com](http://www.edatop.com))由数名来自于研发第一线的资深工程师发起成立,致力并专注于微波、射频、天线设计研发人才的培养;我们于 2006 年整合合并微波 EDA 网([www.mweda.com](http://www.mweda.com)),现已发展成为国内最大的微波射频和天线设计人才培养基地,成功推出多套微波射频以及天线设计经典培训课程和 ADS、HFSS 等专业软件使用培训课程,广受客户好评;并先后与人民邮电出版社、电子工业出版社合作出版了多本专业图书,帮助数万名工程师提升了专业技术能力。客户遍布中兴通讯、研通高频、埃威航电、国人通信等多家国内知名公司,以及台湾工业技术研究院、永业科技、全一电子等多家台湾地区企业。

易迪拓培训课程列表: <http://www.edatop.com/peixun/rfe/129.html>



### 射频工程师养成培训课程套装

该套装精选了射频专业基础培训课程、射频仿真设计培训课程和射频电路测量培训课程三个类别共 30 门视频培训课程和 3 本图书教材;旨在引领学员全面学习一个射频工程师需要熟悉、理解和掌握的专业知识和研发设计能力。通过套装的学习,能够让学员完全达到和胜任一个合格的射频工程师的要求...

课程网址: <http://www.edatop.com/peixun/rfe/110.html>

### ADS 学习培训课程套装

该套装是迄今国内最全面、最权威的 ADS 培训教程,共包含 10 门 ADS 学习培训课程。课程是由具有多年 ADS 使用经验的微波射频与通信系统设计领域资深专家讲解,并多结合设计实例,由浅入深、详细而又全面地讲解了 ADS 在微波射频电路设计、通信系统设计和电磁仿真设计方面的内容。能让您在最短的时间内学会使用 ADS,迅速提升个人技术能力,把 ADS 真正应用到实际研发工作中去,成为 ADS 设计专家...



课程网址: <http://www.edatop.com/peixun/ads/13.html>



### HFSS 学习培训课程套装

该套课程套装包含了本站全部 HFSS 培训课程,是迄今国内最全面、最专业的 HFSS 培训教程套装,可以帮助您从零开始,全面深入学习 HFSS 的各项功能和在多个方面的工程应用。购买套装,更可超值赠送 3 个月免费学习答疑,随时解答您学习过程中遇到的棘手问题,让您的 HFSS 学习更加轻松顺畅...

课程网址: <http://www.edatop.com/peixun/hfss/11.html>

## CST 学习培训课程套装

该培训套装由易迪拓培训联合微波 EDA 网共同推出,是最全面、系统、专业的 CST 微波工作室培训课程套装,所有课程都由经验丰富的专家授课,视频教学,可以帮助您从零开始,全面系统地学习 CST 微波工作的各项功能及其在微波射频、天线设计等领域的设计应用。且购买该套装,还可超值赠送 3 个月免费学习答疑...

课程网址: <http://www.edatop.com/peixun/cst/24.html>



## HFSS 天线设计培训课程套装

套装包含 6 门视频课程和 1 本图书,课程从基础讲起,内容由浅入深,理论介绍和实际操作讲解相结合,全面系统的讲解了 HFSS 天线设计的全过程。是国内最全面、最专业的 HFSS 天线设计课程,可以帮助您快速学习掌握如何使用 HFSS 设计天线,让天线设计不再难...

课程网址: <http://www.edatop.com/peixun/hfss/122.html>

## 13.56MHz NFC/RFID 线圈天线设计培训课程套装

套装包含 4 门视频培训课程,培训将 13.56MHz 线圈天线设计原理和仿真设计实践相结合,全面系统地讲解了 13.56MHz 线圈天线的工作原理、设计方法、设计考量以及使用 HFSS 和 CST 仿真分析线圈天线的具体操作,同时还介绍了 13.56MHz 线圈天线匹配电路的设计和调试。通过该套课程的学习,可以帮助您快速学习掌握 13.56MHz 线圈天线及其匹配电路的原理、设计和调试...

详情浏览: <http://www.edatop.com/peixun/antenna/116.html>



### 我们的课程优势:

- ※ 成立于 2004 年,10 多年丰富的行业经验,
- ※ 一直致力并专注于微波射频和天线设计工程师的培养,更了解该行业对人才的要求
- ※ 经验丰富的一线资深工程师讲授,结合实际工程案例,直观、实用、易学

### 联系我们:

- ※ 易迪拓培训官网: <http://www.edatop.com>
- ※ 微波 EDA 网: <http://www.mweda.com>
- ※ 官方淘宝店: <http://shop36920890.taobao.com>