


# Op Amp Circuit Collection

National Semiconductor  
Application Note 31  
February 1978




## SECTION 1—BASIC CIRCUITS


### Inverting Amplifier

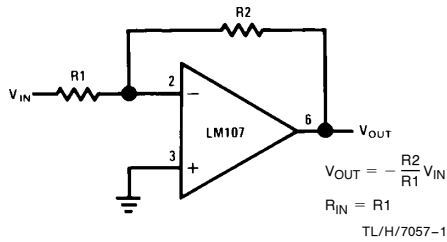


### Non-Inverting Amplifier

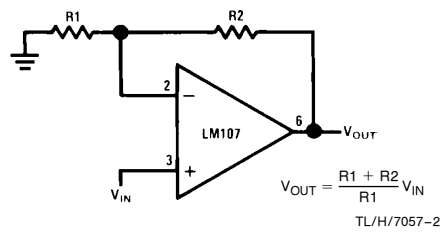


### Difference Amplifier

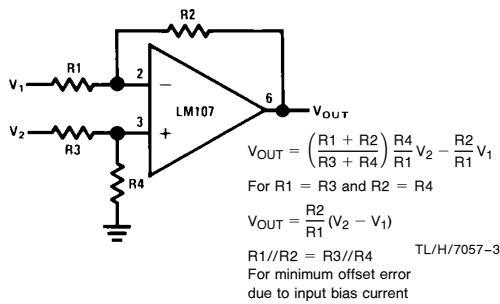


### Inverting Summing Amplifier

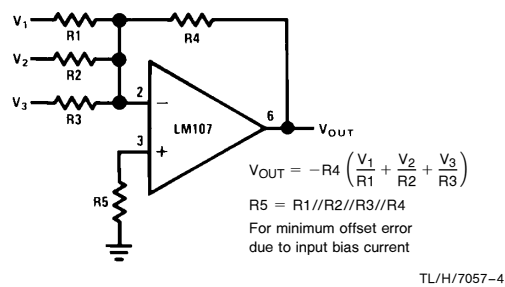


### Non-Inverting Summing Amplifier

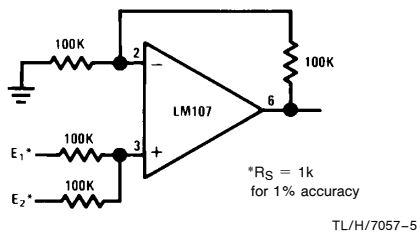

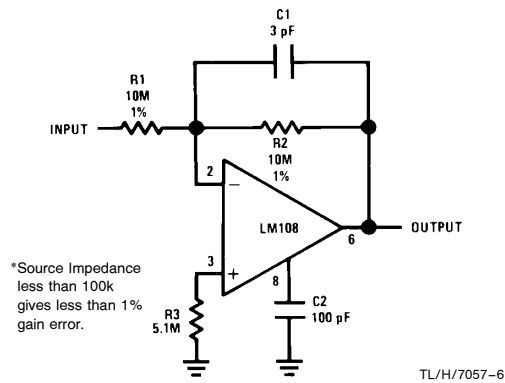
### Inverting Amplifier with High Input Impedance



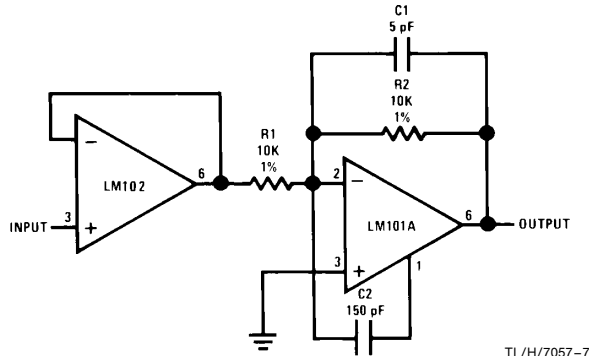
### Fast Inverting Amplifier with High Input Impedance



### Non-Inverting AC Amplifier

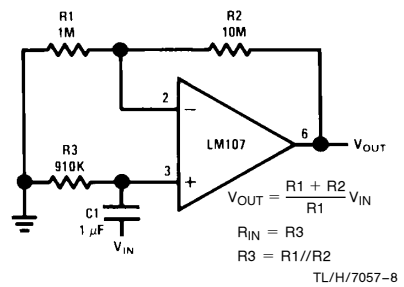

**Practical Differentiator**

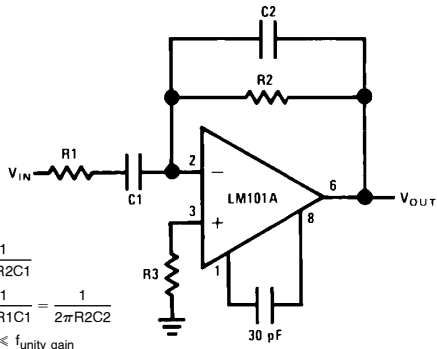


$$f_c = \frac{1}{2\pi R_2 C_1}$$

$$f_h = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi R_2 C_2}$$

$$f_c \ll f_h \ll f_{\text{unity gain}}$$

TL/H/7057-9

**Integrator**

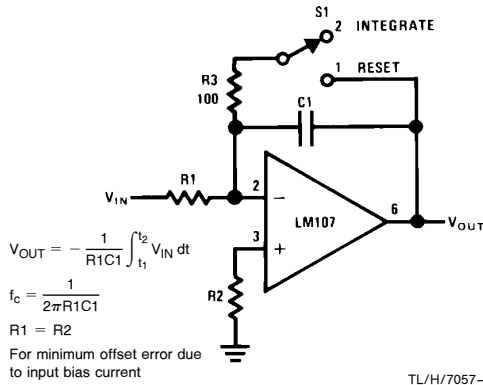

$$V_{OUT} = -\frac{1}{R_1 C_1} \int_{t_1}^{t_2} V_{IN} dt$$


$$f_c = \frac{1}{2\pi R_1 C_1}$$

$$R_1 = R_2$$

For minimum offset error due to input bias current


TL/H/7057-10

**Fast Integrator**

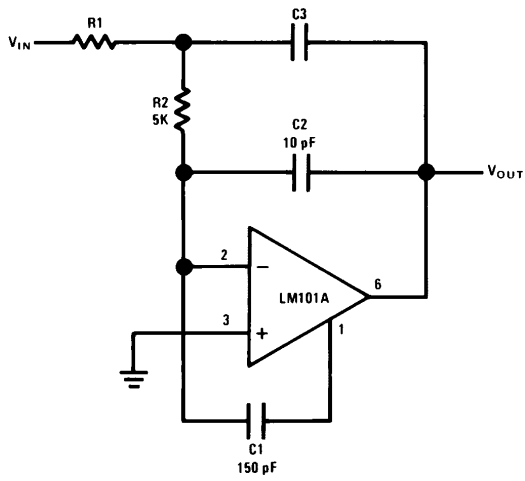

TL/H/7057-11

**Current to Voltage Converter**

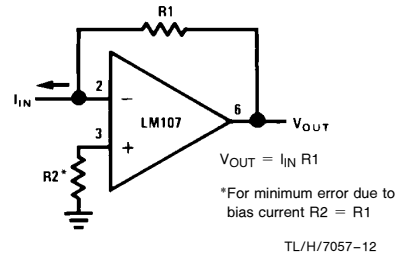


$$V_{OUT} = I_{IN} R_1$$

\*For minimum error due to bias current  $R_2 = R_1$


TL/H/7057-12

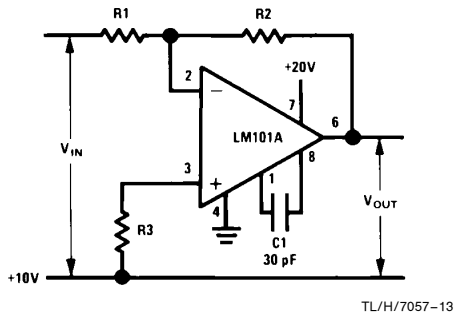**Circuit for Operating the LM101 without a Negative Supply**




TL/H/7057-13

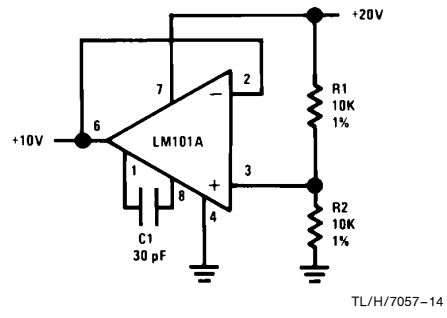**Circuit for Generating the Second Positive Voltage**




TL/H/7057-14

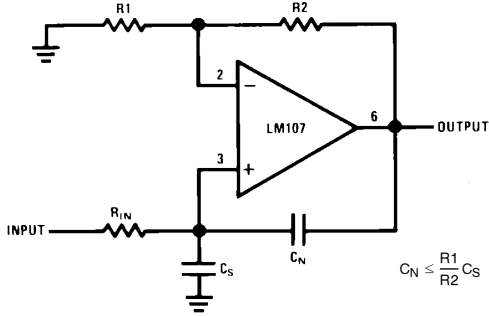**Neutralizing Input Capacitance to Optimize Response Time**




TL/H/7057-15

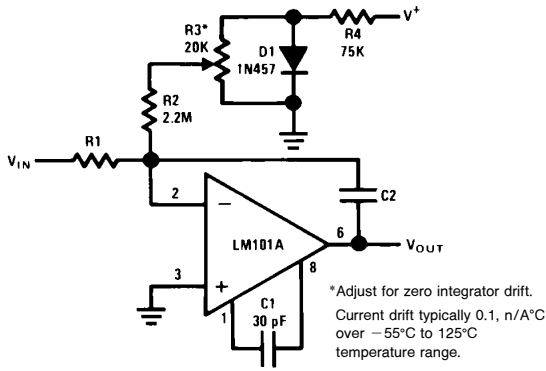**Integrator with Bias Current Compensation**




TL/H/7057-16

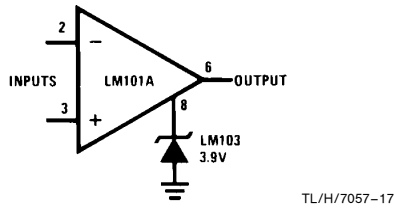**Voltage Comparator for Driving DTL or TTL Integrated Circuits**




TL/H/7057-17

**Threshold Detector for Photodiodes**

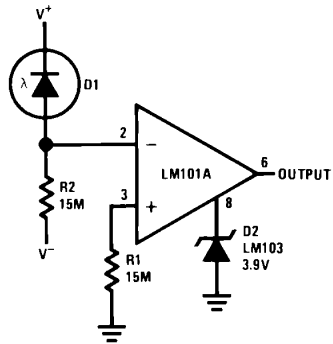


TL/H/7057-18

**Double-Ended Limit Detector**

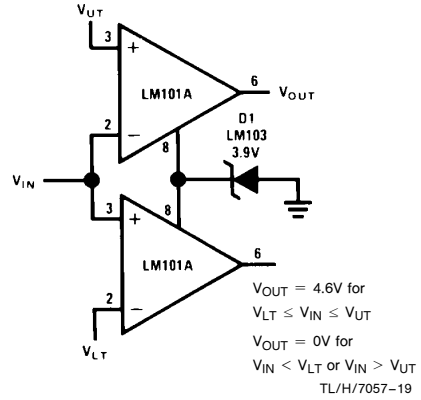


TL/H/7057-19

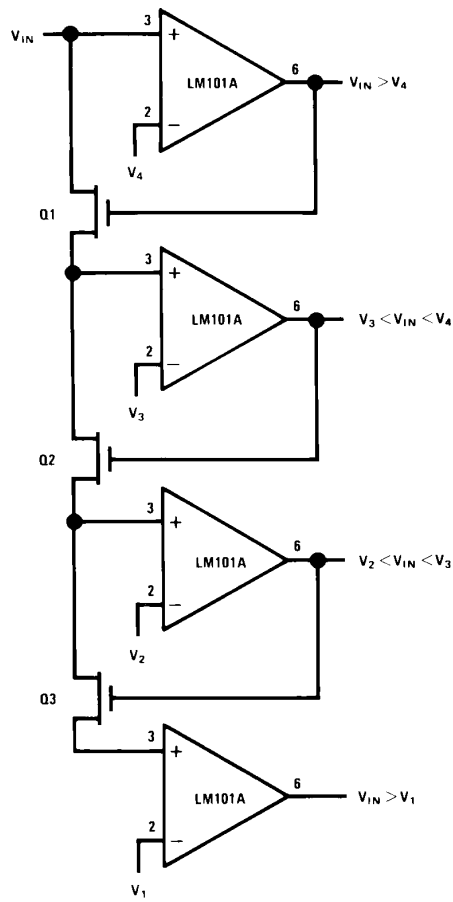**Multiple Aperture Window Discriminator**



TL/H/7057-20

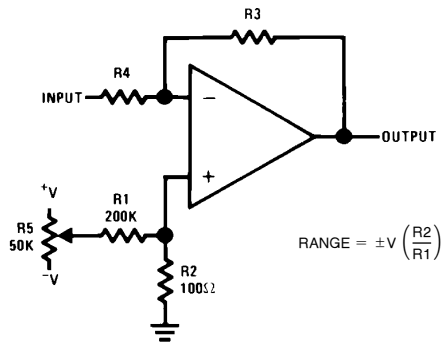
**Offset Voltage Adjustment for Inverting Amplifiers Using Any Type of Feedback Element**



$$\text{RANGE} = \pm V \left( \frac{R2}{R1} \right)$$

TL/H/7057-21

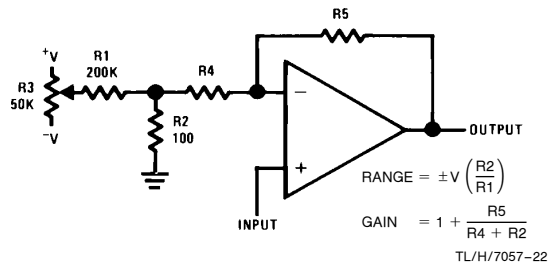**Offset Voltage Adjustment for Non-Inverting Amplifiers Using Any Type of Feedback Element**




$$\text{RANGE} = \pm V \left( \frac{R2}{R1} \right)$$

$$\text{GAIN} = 1 + \frac{R5}{R4 + R2}$$

TL/H/7057-22

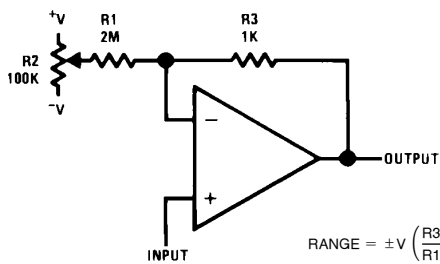
**Offset Voltage Adjustment for Voltage Followers**



$$\text{RANGE} = \pm V \left( \frac{R3}{R1} \right)$$

TL/H/7057-23

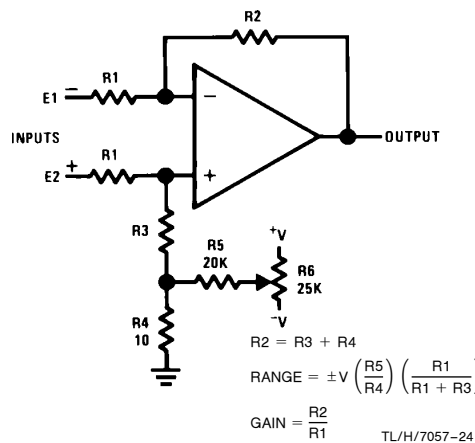**Offset Voltage Adjustment for Differential Amplifiers**




$$R2 = R3 + R4$$

$$\text{RANGE} = \pm V \left( \frac{R5}{R4} \right) \left( \frac{R1}{R1 + R3} \right)$$

$$\text{GAIN} = \frac{R2}{R1}$$

TL/H/7057-24

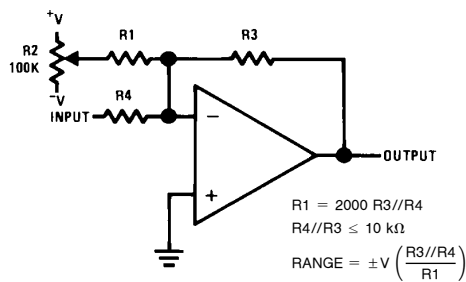**Offset Voltage Adjustment for Inverting Amplifiers Using 10 kΩ Source Resistance or Less**



$$R1 = 2000 R3 // R4$$


$$R4 // R3 \leq 10 \text{ k}\Omega$$

$$\text{RANGE} = \pm V \left( \frac{R3 // R4}{R1} \right)$$

TL/H/7057-25


SECTION 2 — SIGNAL GENERATION

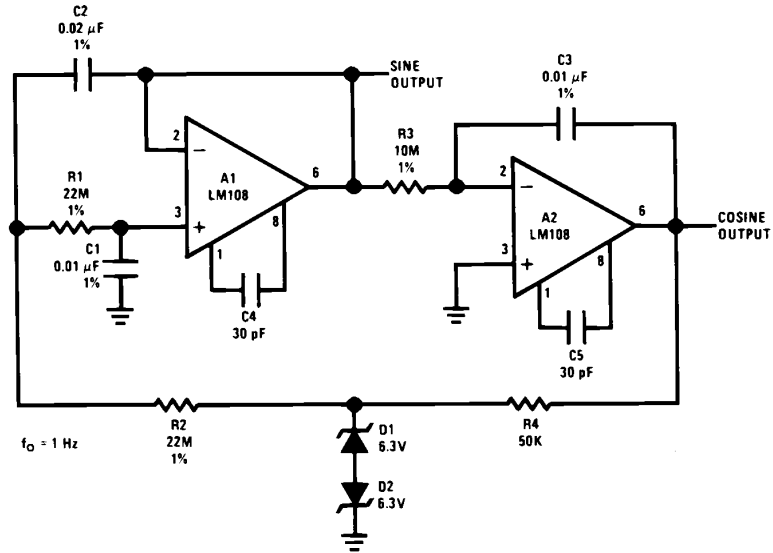Low Frequency Sine Wave Generator with Quadrature Output










TL/H/7057-26

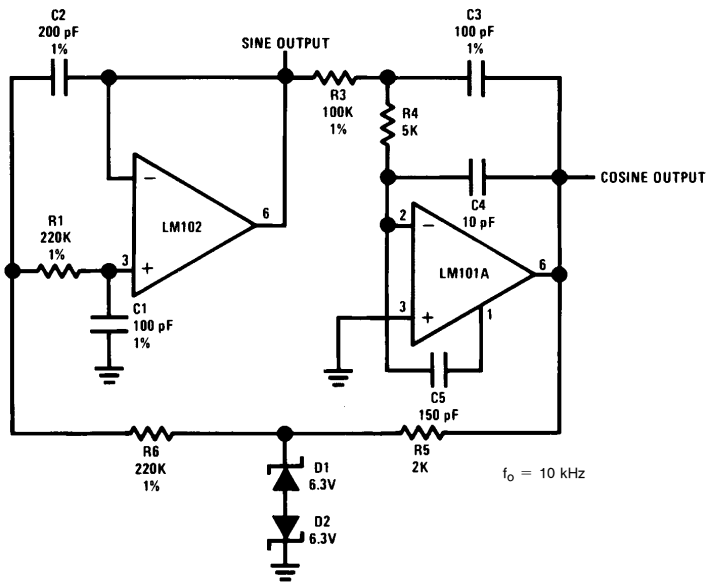High Frequency Sine Wave Generator with Quadrature Output




TL/H/7057-27

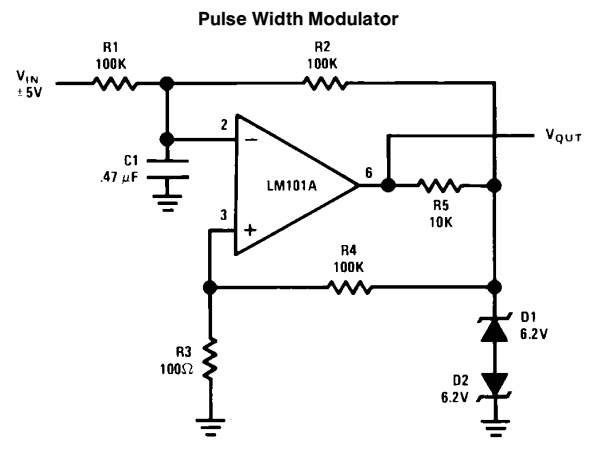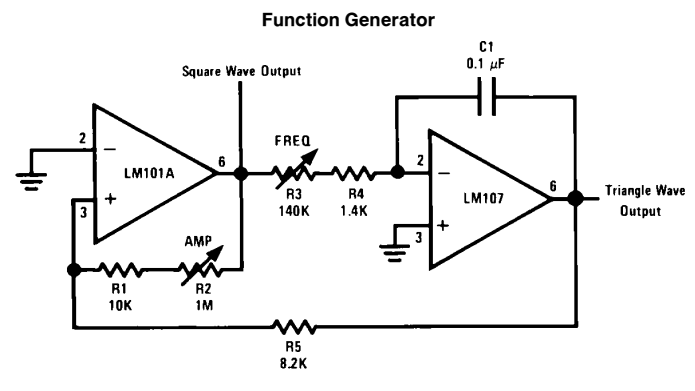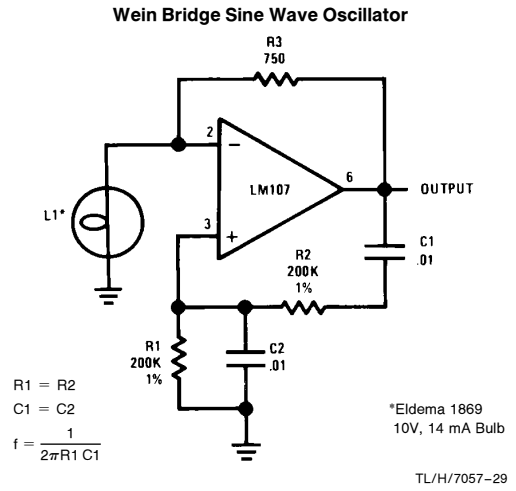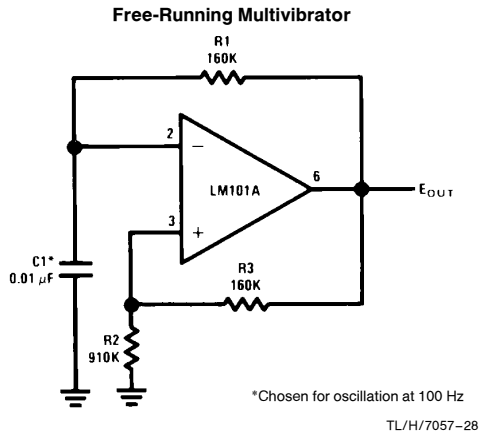


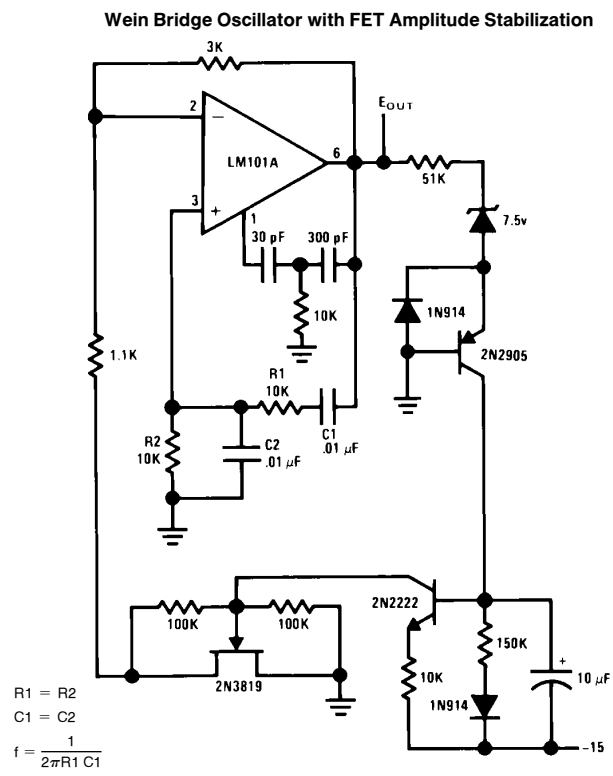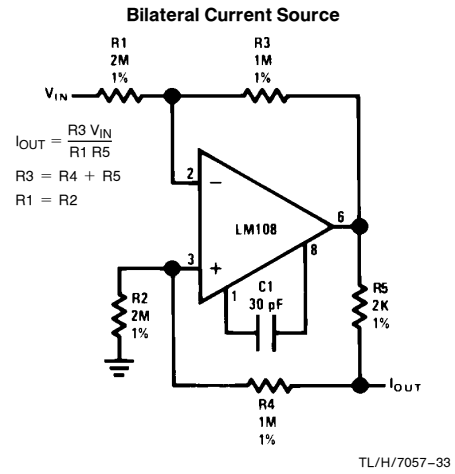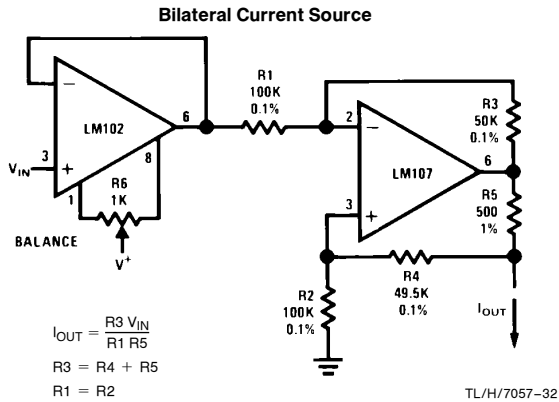

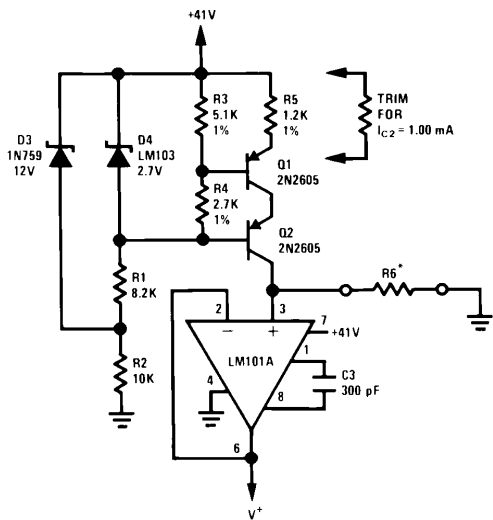Low Power Supply for Integrated Circuit Testing




TL/H/7057-35

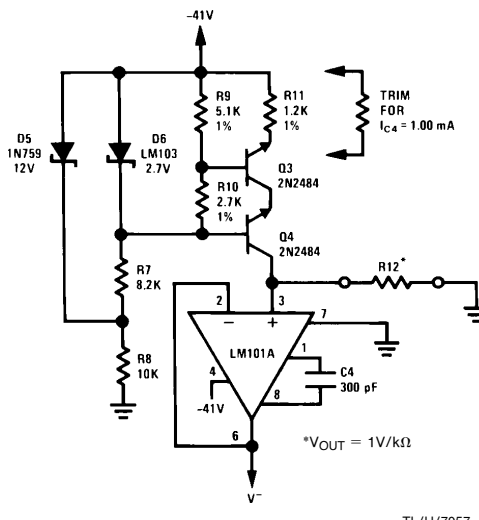


TL/H/7057-91

Positive Voltage Reference

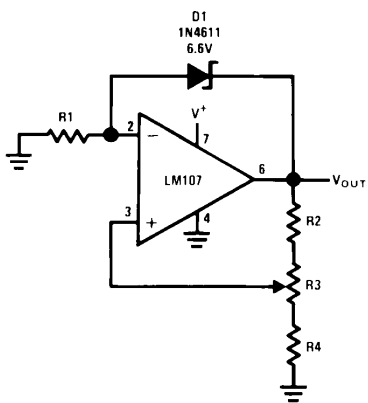

TL/H/7057-36


Positive Voltage Reference

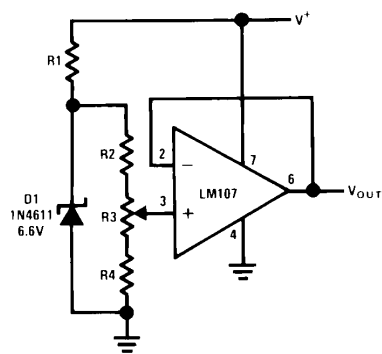

TL/H/7057-37




Negative Voltage Reference

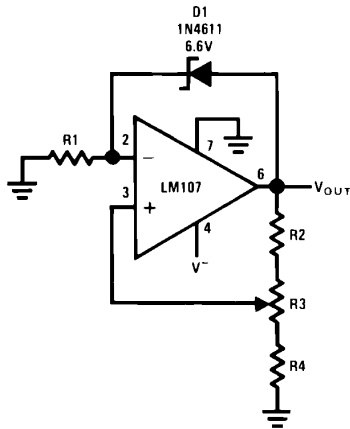


TL/H/7057-38

Negative Voltage Reference

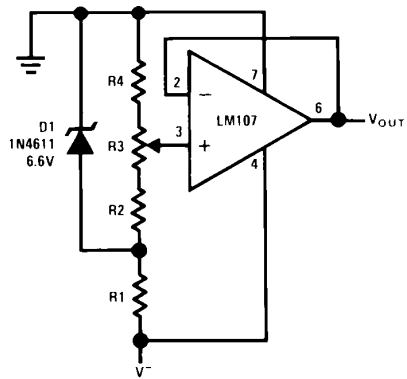

TL/H/7057-39

Precision Current Sink

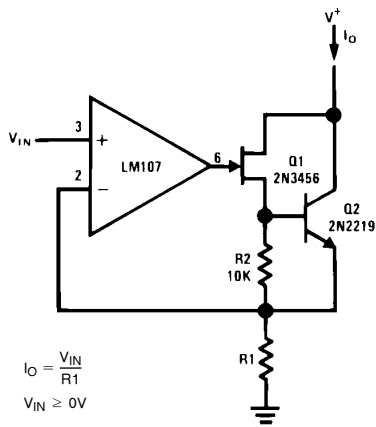


$$I_o = \frac{V_{IN}}{R1}$$

$$V_{IN} \geq 0V$$

TL/H/7057-40

Precision Current Source

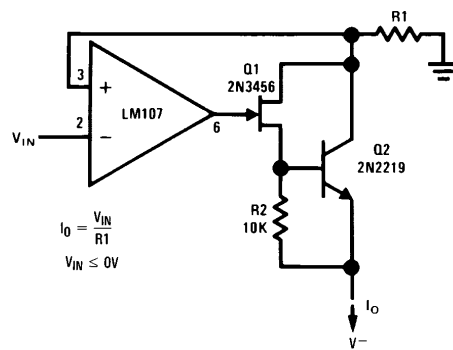


$$I_o = \frac{V_{IN}}{R1}$$

$$V_{IN} \leq 0V$$

TL/H/7057-41

SECTION 3 — SIGNAL PROCESSING

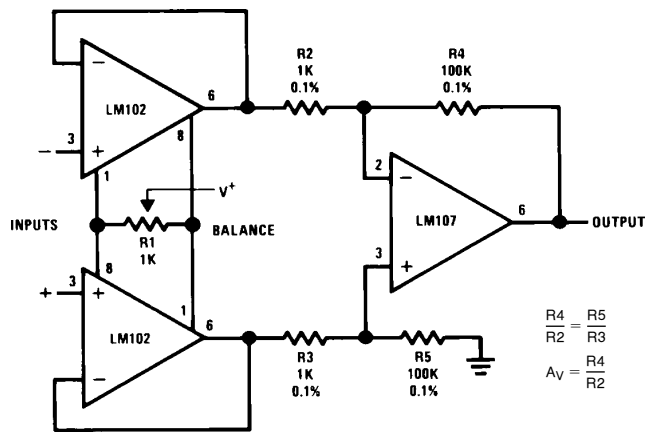Differential-Input Instrumentation Amplifier




$$\frac{R4}{R2} = \frac{R5}{R3}$$

$$A_v = \frac{R4}{R2}$$


TL/H/7057-42

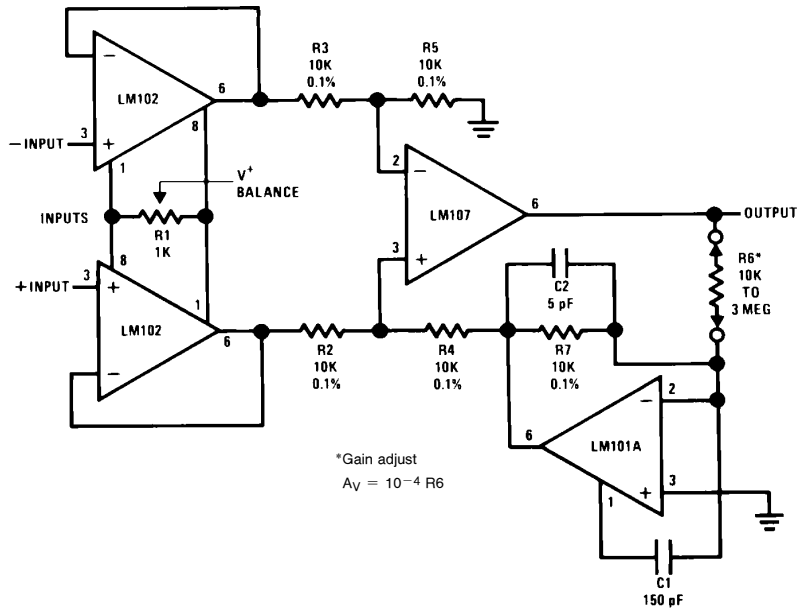Variable Gain, Differential-Input Instrumentation Amplifier




TL/H/7057-43

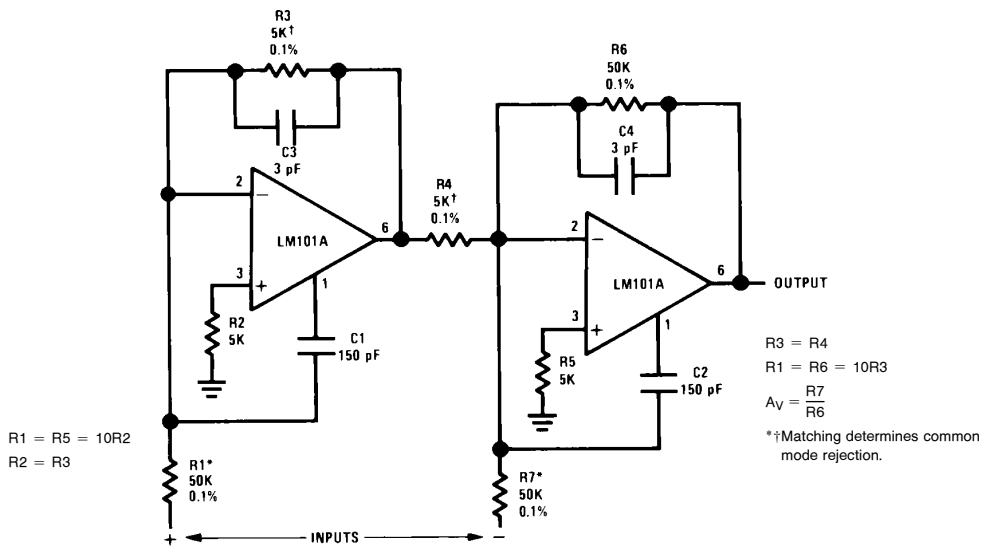Instrumentation Amplifier with  $\pm 100$  Volt Common Mode Range




TL/H/7057-44
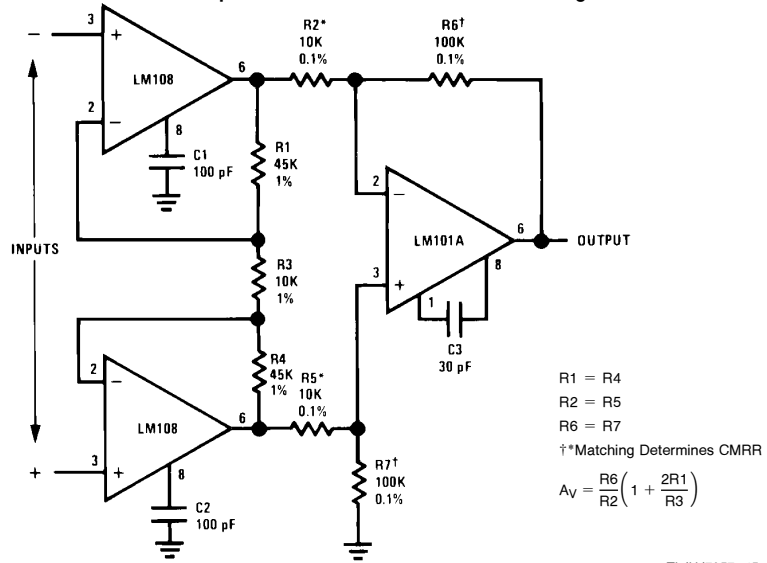
### Instrumentation Amplifier with ± 10 Volt Common Mode Range



TL/H/7057-45
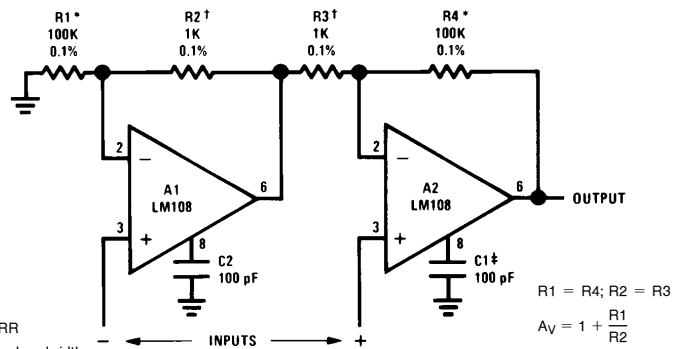
### High Input Impedance Instrumentation Amplifier




\*†Matching determines CMRR







‡May be deleted to maximize bandwidth

TL/H/7057-46

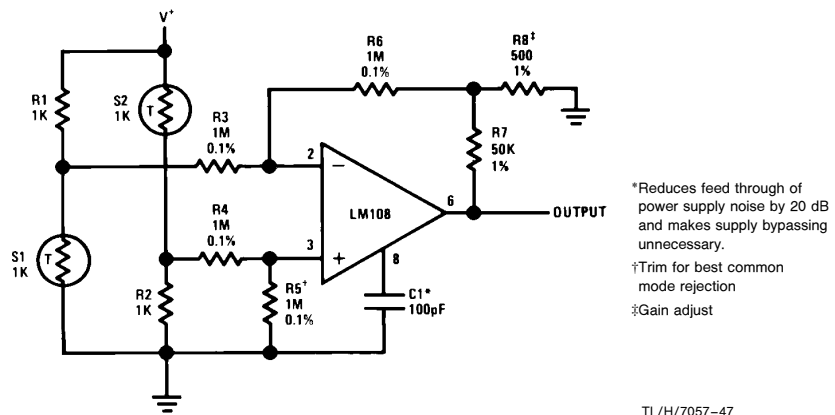
### Bridge Amplifier with Low Noise Compensation



TL/H/7057-47

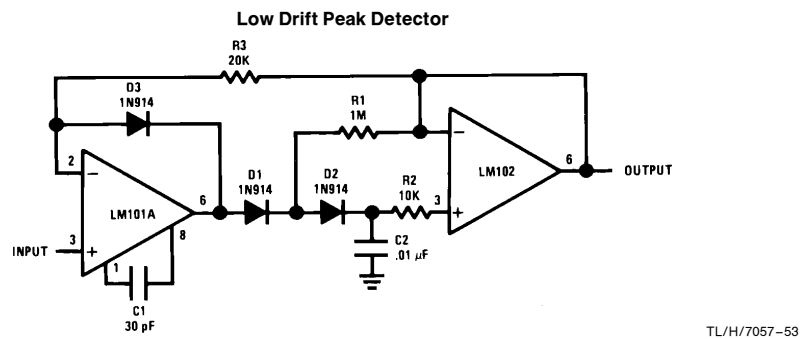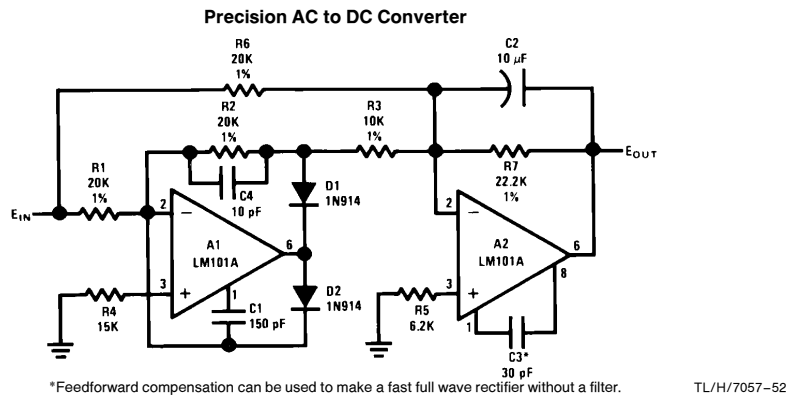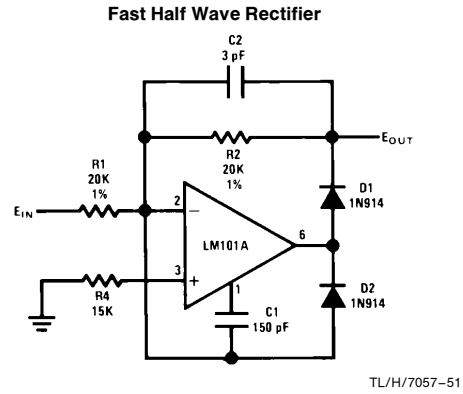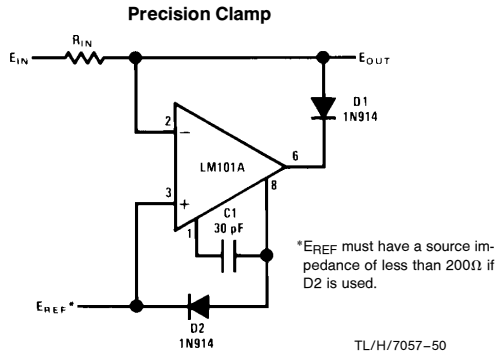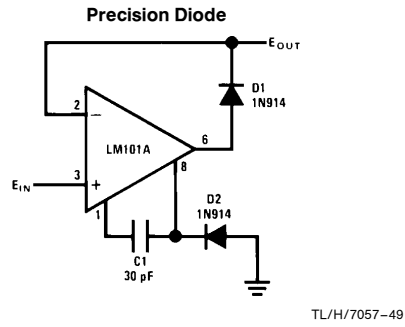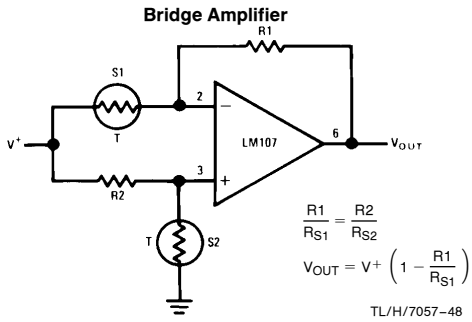

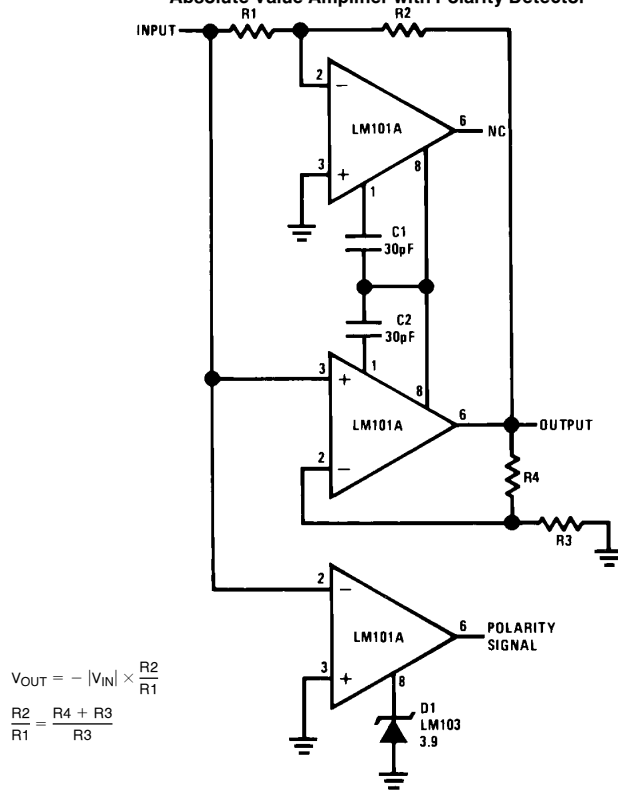
### Absolute Value Amplifier with Polarity Detector




TL/H/7057-54

### Sample and Hold

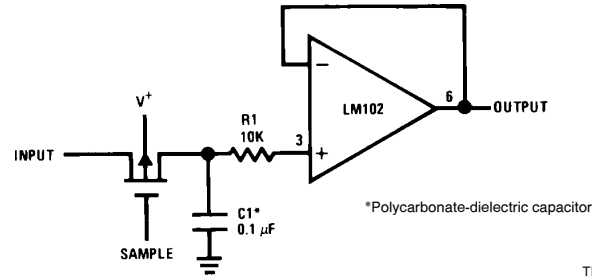


TL/H/7057-55

### Sample and Hold

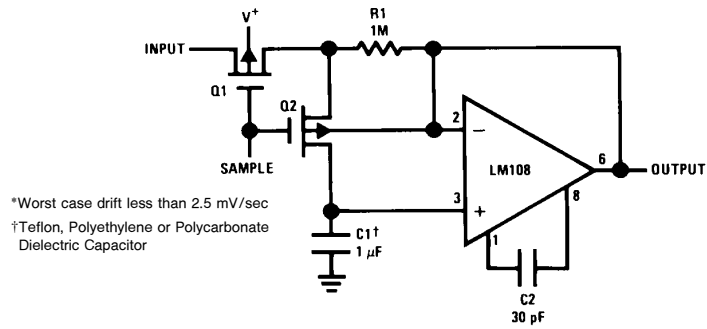

TL/H/7057-56

### Low Drift Integrator

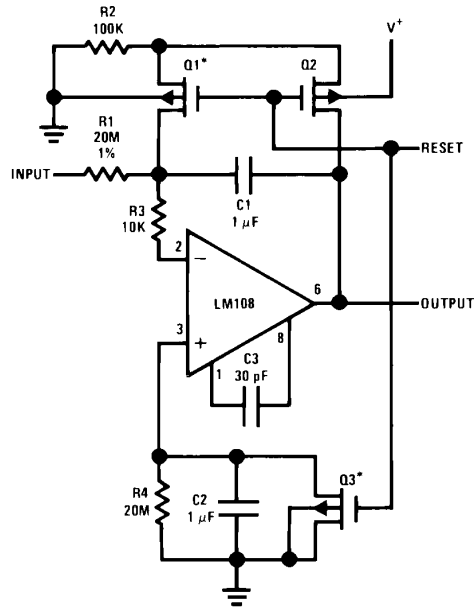


TL/H/7057-57

\*Q1 and Q3 should not have internal gate-protection diodes.

Worst case drift less than 500 μV/sec over -55°C to +125°C.
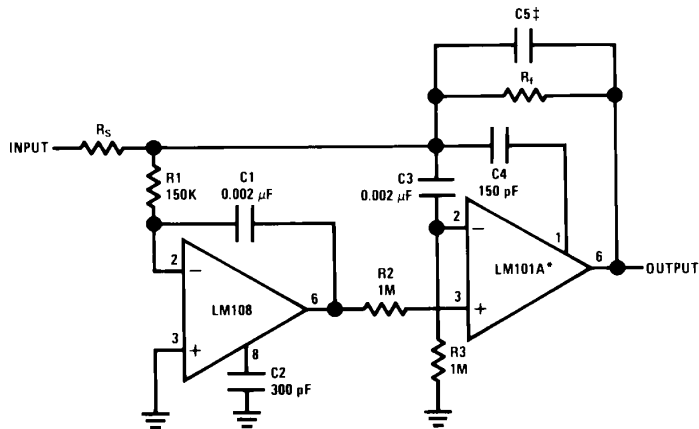
### Fast<sup>†</sup> Summing Amplifier with Low Input Current




TL/H/7057-58

\* In addition to increasing speed, the LM101A raises high and low frequency gain, increases output drive capability and eliminates thermal feedback.

† Power Bandwidth: 250 kHz  
Small Signal Bandwidth: 3.5 MHz  
Slew Rate: 10V/μs


$$\ddagger C5 = \frac{6 \times 10^{-8}}{R_f}$$
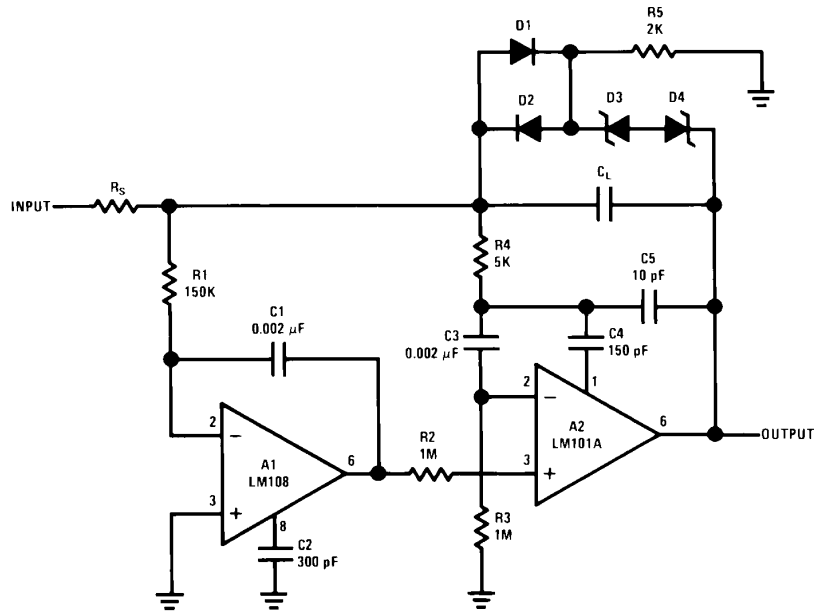
### Fast Integrator with Low Input Current



TL/H/7057-59

### Adjustable Q Notch Filter

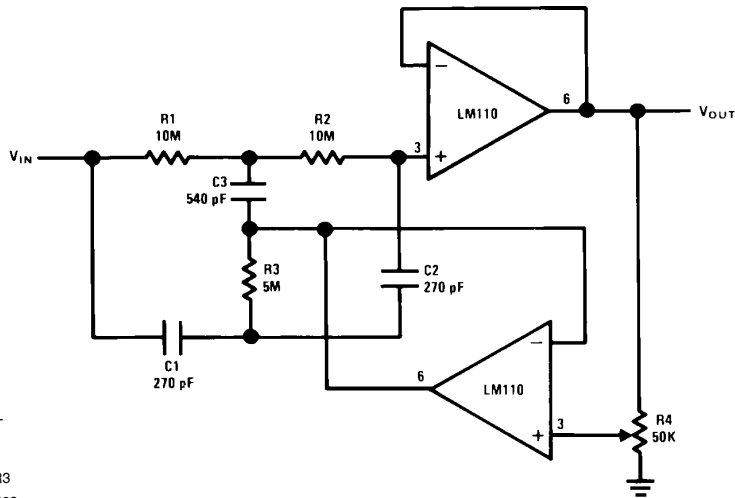


$$f_0 = \frac{1}{2\pi R_1 C_1}$$

$$= 60 \text{ Hz}$$

$R_1 = R_2 = R_3$   
 $C_1 = C_2 = C_3$


TL/H/7057-60

### Easily Tuned Notch Filter

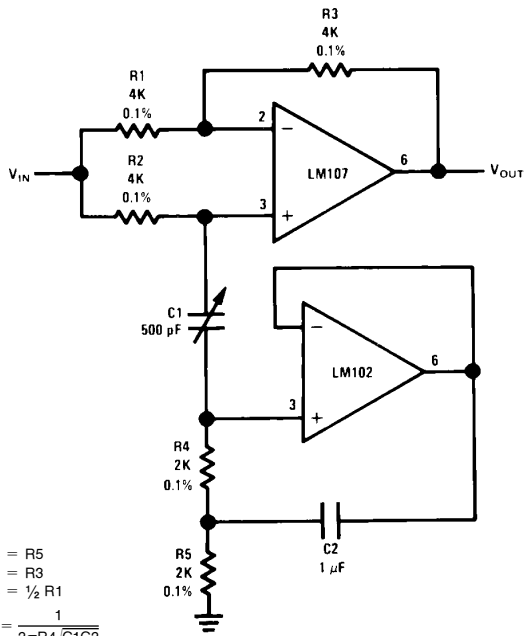


TL/H/7057-61

### Tuned Circuit

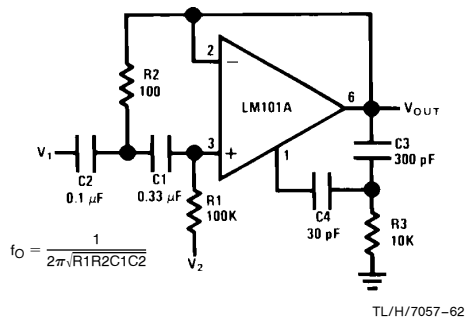


### Two-Stage Tuned Circuit

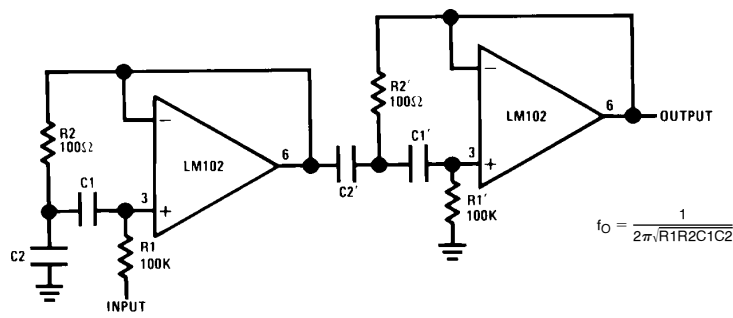



### Negative Capacitance Multiplier

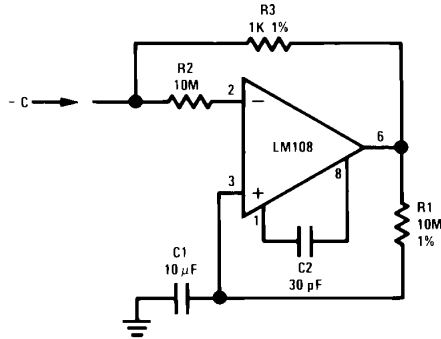


$$C = \frac{R_2}{R_3} C_1$$

$$I_L = \frac{V_{os} + R_2 I_{os}}{R_3}$$

$$R_S = \frac{R_3(R_1 + R_{IN})}{R_{IN} A_{VO}}$$

TL/H/7057-65


### Variable Capacitance Multiplier

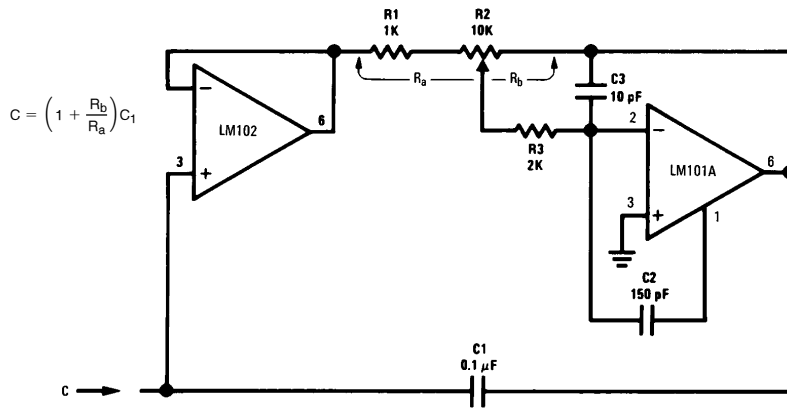

$$C = \left(1 + \frac{R_B}{R_A}\right) C_1$$

TL/H/7057-66

### Simulated Inductor

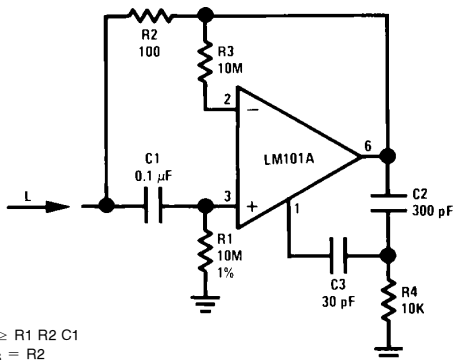


$$L \geq R_1 R_2 C_1$$

$$R_S = R_2$$

$$R_P = R_1$$

TL/H/7057-67

### Capacitance Multiplier

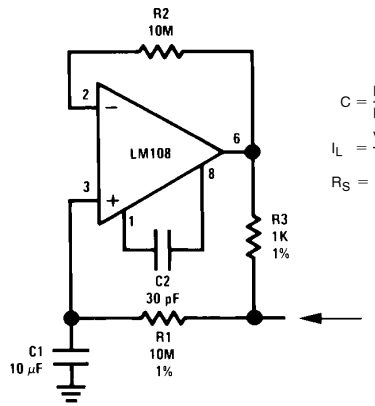


$$C = \frac{R_1}{R_3} C_1$$

$$I_L = \frac{V_{os} + I_{os} R_1}{R_3}$$

$$R_S = R_3$$

TL/H/7057-68


### High Pass Active Filter

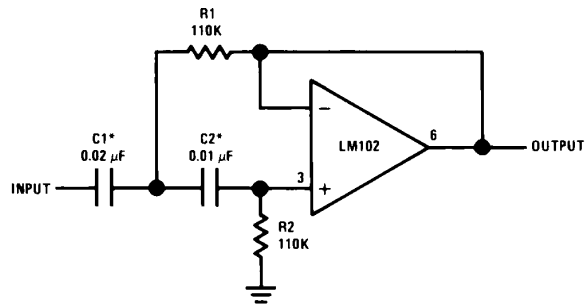

TL/H/7057-71

\*Values are for 100 Hz cutoff. Use metallized polycarbonate capacitors for good temperature stability.


### Low Pass Active Filter

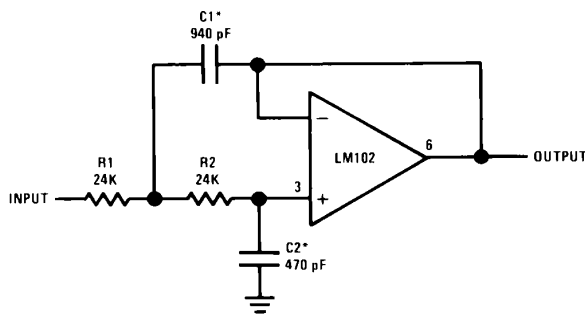


TL/H/7057-72

\*Values are for 10 kHz cutoff. Use silvered mica capacitors for good temperature stability.
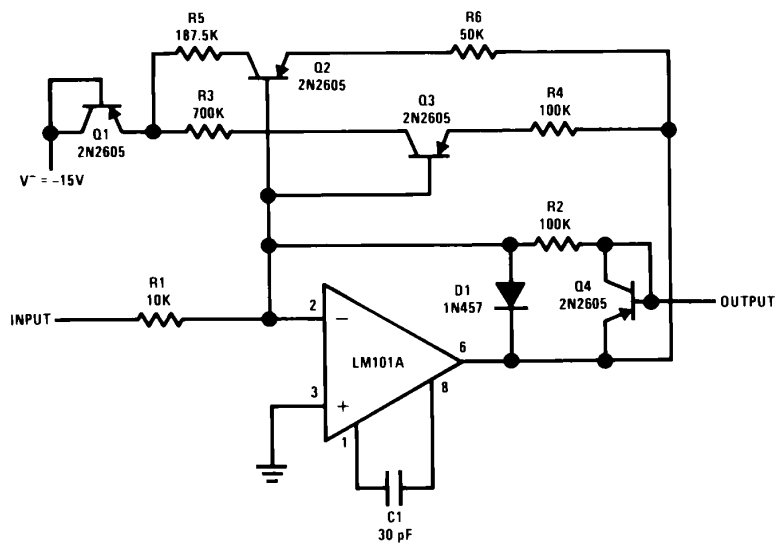
### Nonlinear Operational Amplifier with Temperature Compensated Breakpoints




TL/H/7057-73

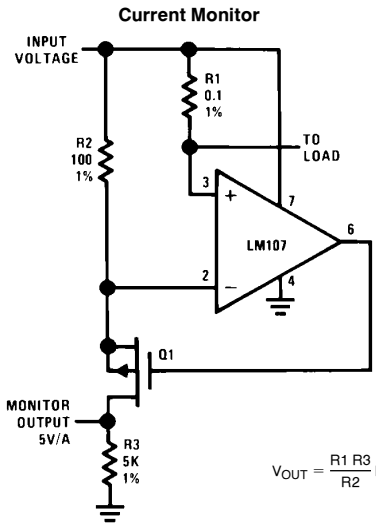


$$V_{OUT} = \frac{R_1 R_3}{R_2} I_L$$

TL/H/7057-74

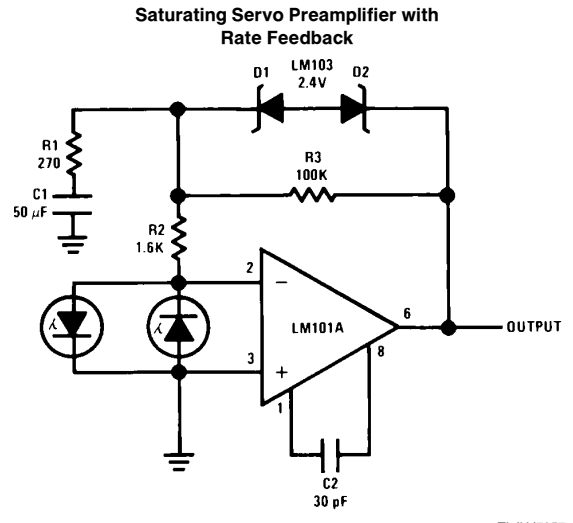


TL/H/7057-75

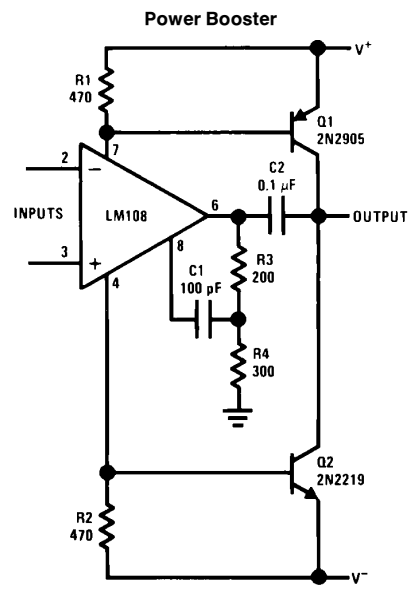

TL/H/7057-76

### Analog Multiplier

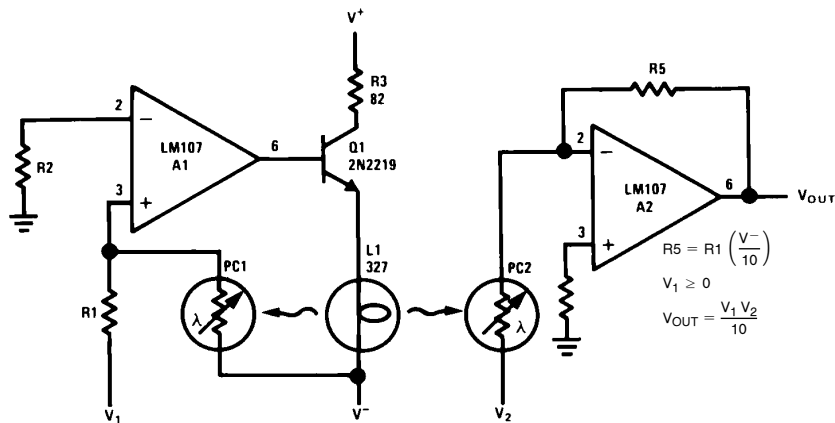


$$R5 = R1 \left( \frac{V^-}{10} \right)$$

$$V_1 \geq 0$$

$$V_{OUT} = \frac{V_1 V_2}{10}$$

TL/H/7057-77


### Long Interval Timer

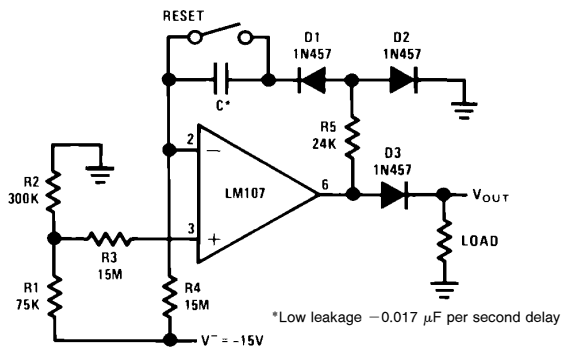

\*Low leakage -0.017 μF per second delay

TL/H/7057-78


### Fast Zero Crossing Detector

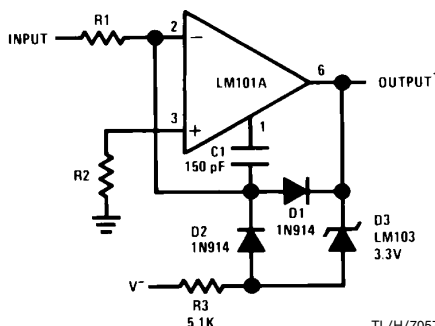

Propagation delay approximately 200 ns  
 †DTL or TTL fanout of three.  
 Minimize stray capacitance  
 Pin 8

TL/H/7057-79

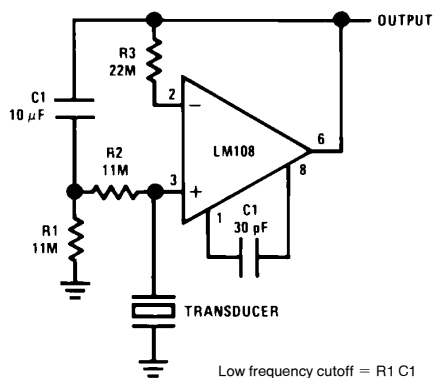
### Amplifier for Piezoelectric Transducer



Low frequency cutoff = R1 C1


TL/H/7057-80

### Temperature Probe

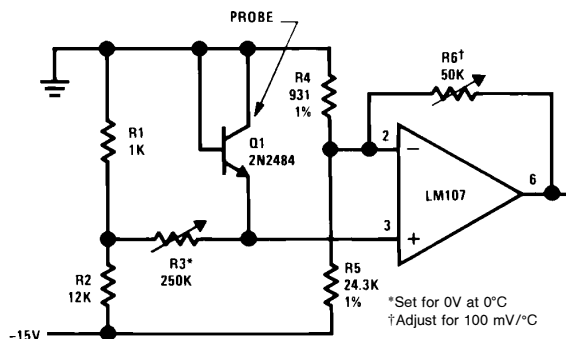


\*Set for 0V at 0°C  
 †Adjust for 100 mV/°C

TL/H/7057-81

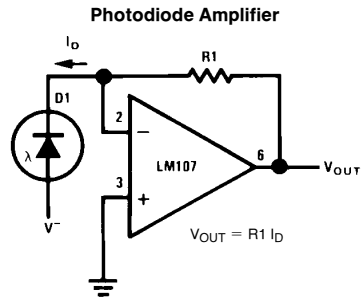


TL/H/7057-82

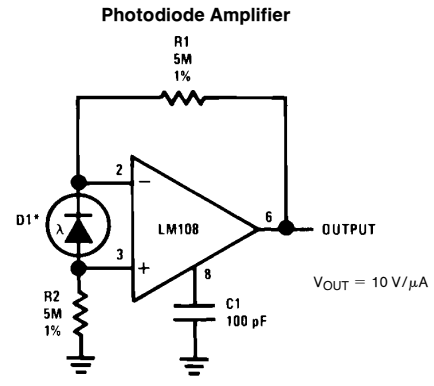


TL/H/7057-83

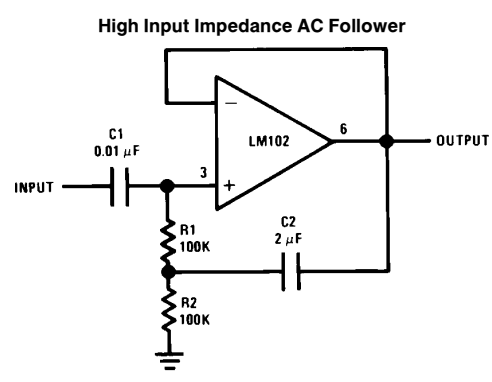\*Operating photodiode with less than 3 mV across it eliminates leakage currents.




TL/H/7057-84

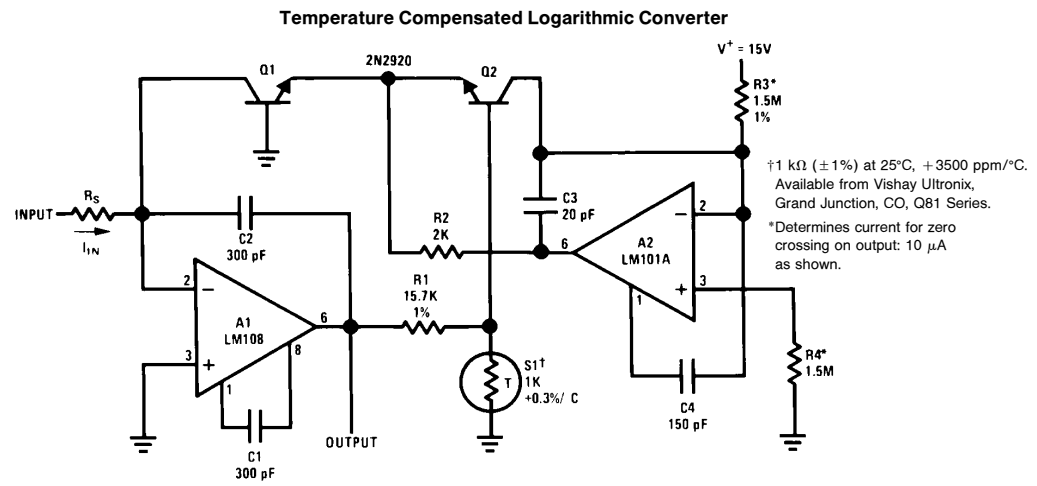

TL/H/7057-85

10 nA <  $I_{IN}$  < 1 mA  
Sensitivity is 1V per decade


### Root Extractor

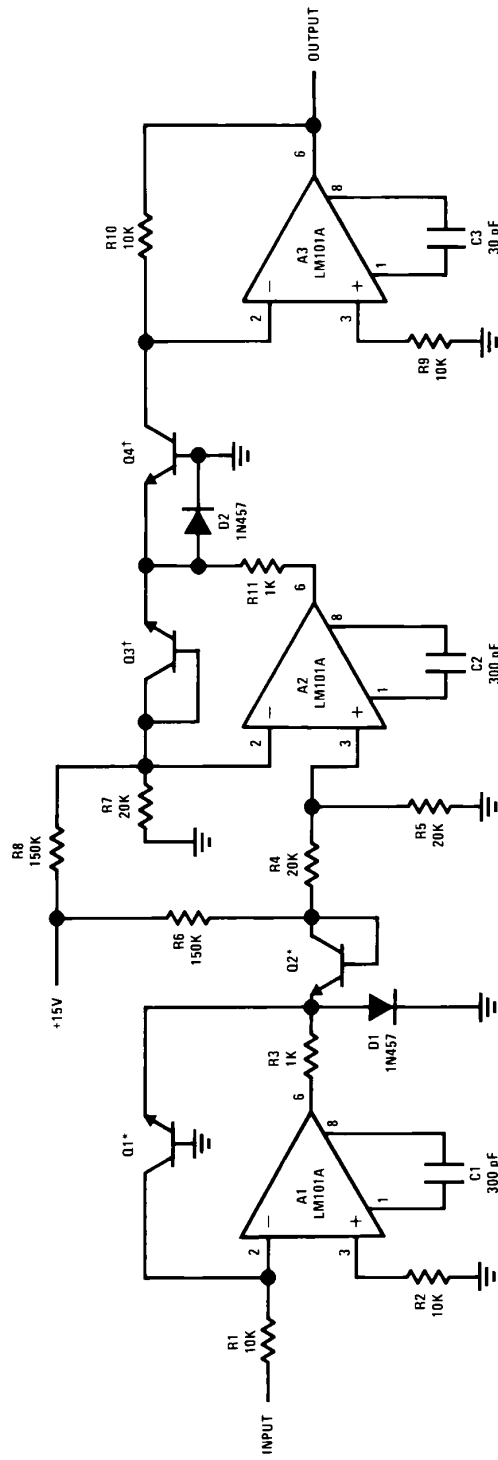

\*: 1/2N3728 matched pairs

TL/H/7057-86

### Multiplier/Divider

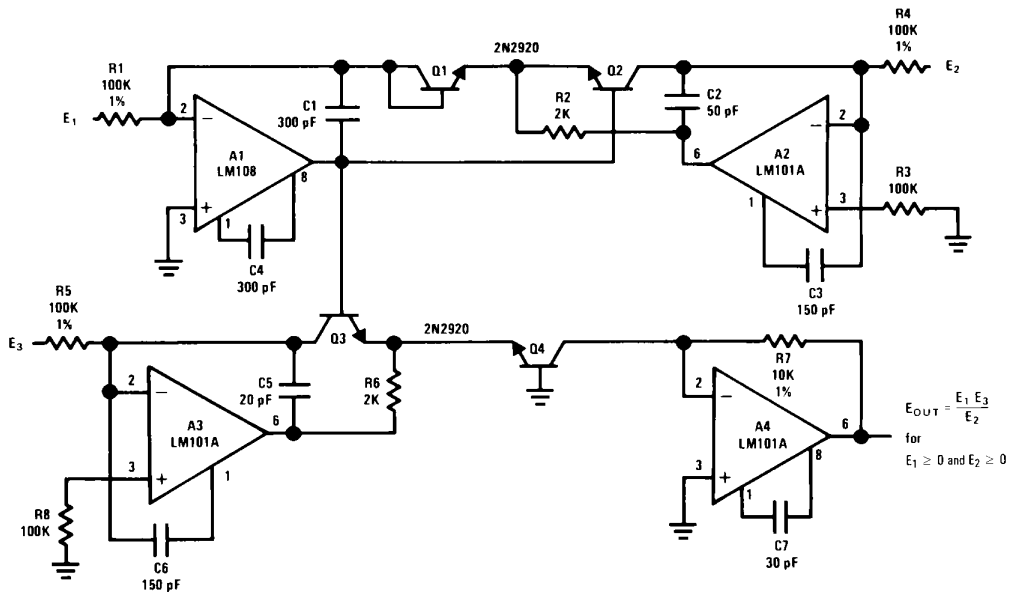


$$E_{OUT} = \frac{E_1 E_3}{E_2}$$


for  $E_1 \geq 0$  and  $E_2 \geq 0$

TL/H/7057-87


### Cube Generator

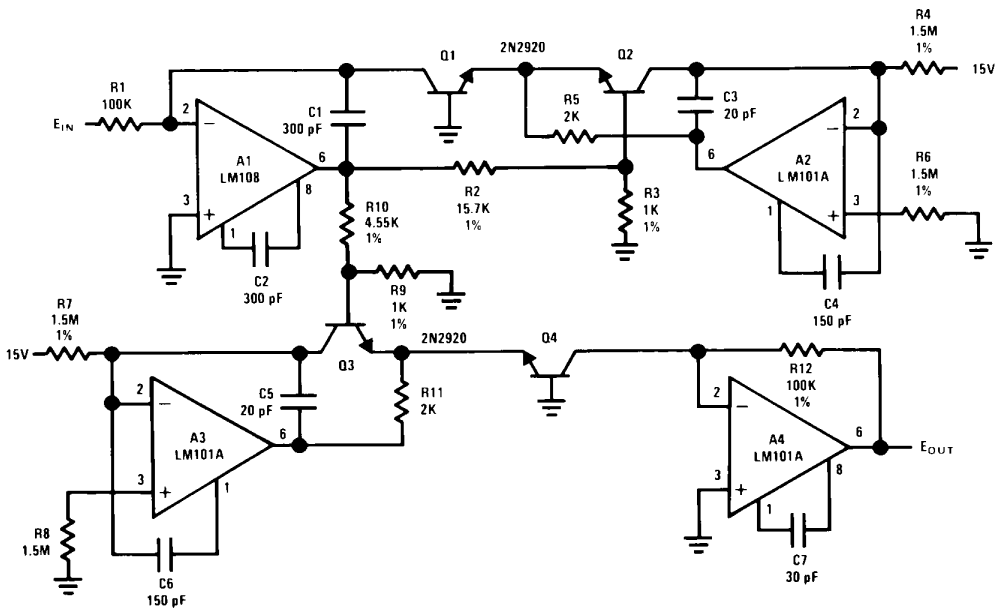

TL/H/7057-88

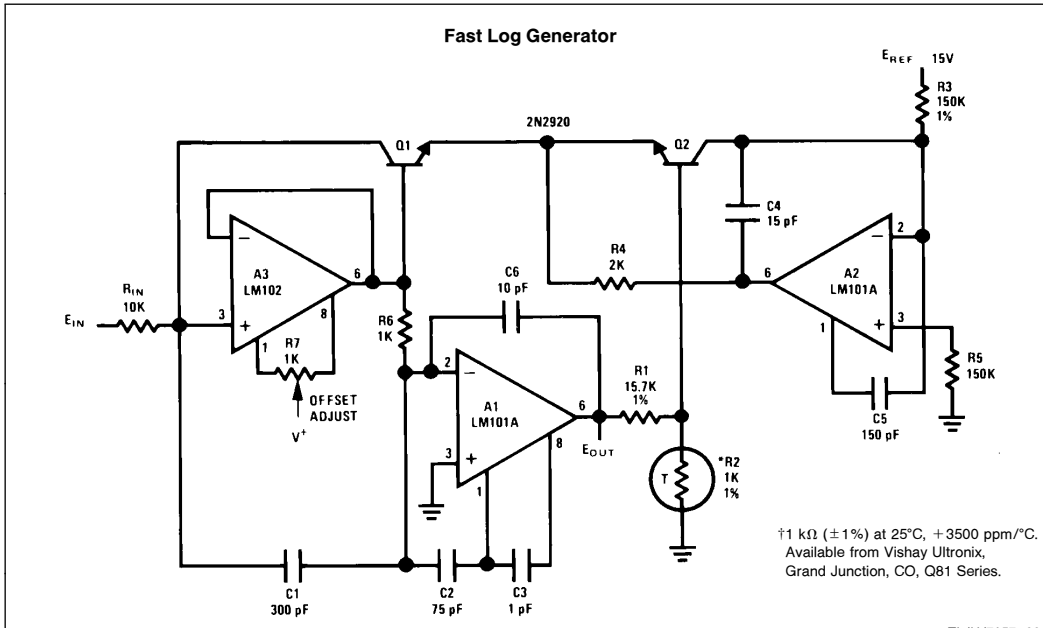

TL/H/7057-89

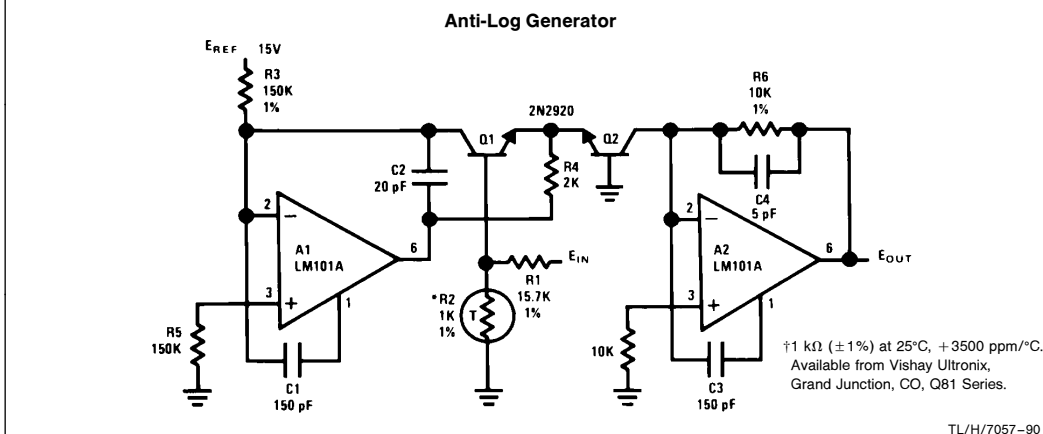

TL/H/7057-90

**LIFE SUPPORT POLICY**

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



**National Semiconductor Corporation**  
1111 West Bardin Road  
Arlington, TX 76017  
Tel: 1(800) 272-9959  
Fax: 1(800) 737-7018

**National Semiconductor Europe**  
Fax: (+49) 0-180-530 85 86  
Email: onjwge@tevm2.nsc.com  
Deutsch Tel: (+49) 0-180-530 85 85  
English Tel: (+49) 0-180-532 78 32  
Français Tel: (+49) 0-180-532 93 58  
Italiano Tel: (+49) 0-180-534 16 80

**National Semiconductor Hong Kong Ltd.**  
19th Floor, Straight Block,  
Ocean Centre, 5 Canton Rd.  
Tsimshatsui, Kowloon  
Hong Kong  
Tel: (852) 2737-1600  
Fax: (852) 2736-9960

**National Semiconductor Japan Ltd.**  
Tel: 81-043-299-2309  
Fax: 81-043-299-2408

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.



## 射频和天线设计培训课程推荐

易迪拓培训([www.edatop.com](http://www.edatop.com))由数名来自于研发第一线的资深工程师发起成立,致力并专注于微波、射频、天线设计研发人才的培养;我们于 2006 年整合合并微波 EDA 网([www.mweda.com](http://www.mweda.com)),现已发展成为国内最大的微波射频和天线设计人才培养基地,成功推出多套微波射频以及天线设计经典培训课程和 ADS、HFSS 等专业软件使用培训课程,广受客户好评;并先后与人民邮电出版社、电子工业出版社合作出版了多本专业图书,帮助数万名工程师提升了专业技术能力。客户遍布中兴通讯、研通高频、埃威航电、国人通信等多家国内知名公司,以及台湾工业技术研究院、永业科技、全一电子等多家台湾地区企业。

易迪拓培训课程列表: <http://www.edatop.com/peixun/rfe/129.html>



### 射频工程师养成培训课程套装

该套装精选了射频专业基础培训课程、射频仿真设计培训课程和射频电路测量培训课程三个类别共 30 门视频培训课程和 3 本图书教材;旨在引领学员全面学习一个射频工程师需要熟悉、理解和掌握的专业知识和研发设计能力。通过套装的学习,能够让学员完全达到和胜任一个合格的射频工程师的要求...

课程网址: <http://www.edatop.com/peixun/rfe/110.html>

### ADS 学习培训课程套装

该套装是迄今国内最全面、最权威的 ADS 培训教程,共包含 10 门 ADS 学习培训课程。课程是由具有多年 ADS 使用经验的微波射频与通信系统设计领域资深专家讲解,并多结合设计实例,由浅入深、详细而又全面地讲解了 ADS 在微波射频电路设计、通信系统设计和电磁仿真设计方面的内容。能让您在最短的时间内学会使用 ADS,迅速提升个人技术能力,把 ADS 真正应用到实际研发工作中去,成为 ADS 设计专家...



课程网址: <http://www.edatop.com/peixun/ads/13.html>



### HFSS 学习培训课程套装

该套课程套装包含了本站全部 HFSS 培训课程,是迄今国内最全面、最专业的 HFSS 培训教程套装,可以帮助您从零开始,全面深入学习 HFSS 的各项功能和在多个方面的工程应用。购买套装,更可超值赠送 3 个月免费学习答疑,随时解答您学习过程中遇到的棘手问题,让您的 HFSS 学习更加轻松顺畅...

课程网址: <http://www.edatop.com/peixun/hfss/11.html>

## CST 学习培训课程套装

该培训套装由易迪拓培训联合微波 EDA 网共同推出,是最全面、系统、专业的 CST 微波工作室培训课程套装,所有课程都由经验丰富的专家授课,视频教学,可以帮助您从零开始,全面系统地学习 CST 微波工作的各项功能及其在微波射频、天线设计等领域的设计应用。且购买该套装,还可超值赠送 3 个月免费学习答疑...

课程网址: <http://www.edatop.com/peixun/cst/24.html>



## HFSS 天线设计培训课程套装

套装包含 6 门视频课程和 1 本图书,课程从基础讲起,内容由浅入深,理论介绍和实际操作讲解相结合,全面系统的讲解了 HFSS 天线设计的全过程。是国内最全面、最专业的 HFSS 天线设计课程,可以帮助您快速学习掌握如何使用 HFSS 设计天线,让天线设计不再难...

课程网址: <http://www.edatop.com/peixun/hfss/122.html>

## 13.56MHz NFC/RFID 线圈天线设计培训课程套装

套装包含 4 门视频培训课程,培训将 13.56MHz 线圈天线设计原理和仿真设计实践相结合,全面系统地讲解了 13.56MHz 线圈天线的工作原理、设计方法、设计考量以及使用 HFSS 和 CST 仿真分析线圈天线的具体操作,同时还介绍了 13.56MHz 线圈天线匹配电路的设计和调试。通过该套课程的学习,可以帮助您快速学习掌握 13.56MHz 线圈天线及其匹配电路的原理、设计和调试...

详情浏览: <http://www.edatop.com/peixun/antenna/116.html>



### 我们的课程优势:

- ※ 成立于 2004 年,10 多年丰富的行业经验,
- ※ 一直致力并专注于微波射频和天线设计工程师的培养,更了解该行业对人才的要求
- ※ 经验丰富的一线资深工程师讲授,结合实际工程案例,直观、实用、易学

### 联系我们:

- ※ 易迪拓培训官网: <http://www.edatop.com>
- ※ 微波 EDA 网: <http://www.mweda.com>
- ※ 官方淘宝店: <http://shop36920890.taobao.com>