

# Lecture #11: LNA (Low Noise Amplifier) Design

1. Introduction
  2. Single-ended Single Device LNA
    - o Size of Device
      - Restriction of  $W/L$  due to the consideration of  $V_{gs}$
      - Optimum Width  $W_{opt}$  of Device
    - o Raw Device Set-up and Testing
      - Challenge for a Good LNA Design
      - Optimum of Source Reflection Coefficient,  $\Gamma_{opt}$
      - Simultaneously Approach to both  $NF_{min}$  and  $G_{max}$
      - Variation of Input Impedance due to Degeneration Inductor
    - o Input and Output Impedance Matching
    - o Gain Circles and Noise Circles
    - o Stability
    - o Non-linearity
      - Spectrum at LNA Output
      - 1 dB Compression Point
      - 3rd and 2nd Order Intercept Point,  $IP3$  and  $IP2$
    - o Design Procedures
    - o Other Examples
  3. Single-ended Cascode LNA
    - o Bipolar CE-CB Cascode Voltage Amplifier
    - o MOSFET CS-CG Cascode Voltage Amplifier
    - o Why Cascode
    - o Example
      - Raw Device Testing
      - Gain and Bandwidth
      - Noise
      - Non-linearity
  4. LNA with AGC (Automatic Gain Control)
    - o AGC Operation
    - o Traditional LNA with AGC
    - o Increase of AGC Dynamic Range
    - o Example
  5. Differential LNA --- (optional)
- Discussion
6. Key points to approach  $G_{max}$  and  $NF_{min}$
  7. Advantages and disadvantages of CS-CG or CE-CB cascode LNA
  8. Why AGC?
  9. Why differential?



# 1. Introduction

## o Importance of LNA in a communication system

- Sensitivity of a receiver is mainly determined by the noise figure of LNA
- Linearity
- Isolation
- AGC (Automatic Gain Control)

## o Topics

- Typical design procedure
- Improve of linearity
- Cascode LNA
- AGC

## o A great challenge : Simultaneously to get $G_{max}$ and $NF_{min}$



# 1. Single-ended single device LNA

## o Specification

## o Size of Device

Restriction of  $W/L$  due to the consideration of  $V_{gs}$

Optimum Width,  $W_{opt}$ , of Device due to consideration of  $NF_{min}$

## o Raw device setup and testing

“Zero” capacitors and “infinite” inductors

Tested parameters :  $S_{11}$ ,  $\Gamma_{opt}$ ,  $S_{21}$ ,  $S_{22}$ ,  $\mu$ , NF and G circles

## o A great challenge : Simultaneously to get $G_{max}$ and $NF_{min}$

Traditional status : Trade-off between  $G_{max}$  and  $NF_{min}$

Key Issue :  $S_{11}^* = \Gamma_{opt}$

## o Three way to get $G_{max}$ and $NF_{min}$ Simultaneously

Degeneration inductor

Variation of current drain

Variation of device size

## o Example

## oSpecification

The main goals for the design example are

<i>V<sub>cc</sub></i>	=3.0 V,
<i>I<sub>cc</sub></i>	<3.0 mA,
Frequency range	= 850 to 940 MHz,
<i>NF</i>	< 2.5 dB,
Gain	> 10 dB,
<i>IP3</i>	> 0 dBm,
<i>IP2</i>	> 40 dBm.

## o Size of Device

\* Restriction of  $W/L$  due to the consideration of  $V_{gs}$

$$I_d = \frac{m_n C_{ox}}{2} \frac{W}{L} (V_{gs} - V_{th})^2$$

---

$$g_m = m_n C_{ox} \frac{W}{L} (V_{gs} - V_{th})$$

$$I_d = \frac{1}{2} g_m (V_{gs} - V_{th})$$

$$C_{ox} = \frac{e_{ox}}{t_{ox}}$$

$$g_m = \sqrt{2m_n C_{ox} \frac{W}{L} I_d}$$

$$V_{gs} = 2 \frac{I_d}{g_m} + V_{th}$$

**Example:**

$$\epsilon_{ox} = 3.45 \times 10^{-13} \text{ F/cm},$$

$$t_{ox} = 23.3 \text{ \AA} = 23.3 \times 10^{-8} \text{ cm},$$

$$\mu_n = 170 \text{ cm}^2/\text{V-sec},$$

$$C_{ox} = 14.81 \text{ fF}/\mu^2,$$

$$V_{th} = 0.49 \text{ V},$$

---

$$\mu_n C_{ox} = 251.72 \mu\text{A}/\text{V}^2.$$

**Table 11.1 Restriction of  $W/L$  due to the consideration of  $V_{gs}$**

$\epsilon_{ox}$	$t_{ox}$	$t_{ox}$	$C_{ox}$	$\mu_n$	$\mu_n C_{ox}$	$I_d$	$W$	$L$	$W/L$	$g_m$	$R_d$	$V_{tn}$	$V_{gs}$
(F/cm)	(Å)	(cm)	(fF/ $\mu^2$ )	$cm^2/(V.s)$	( $\mu A/V^2$ )	(mA)	( $\mu m$ )	( $\mu m$ )		(mA/V)	(k $\Omega$ )	(V)	(V)
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	1.00	0.9	0.09	10.00	2.24	1.00	0.49	1.38
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	1.00	9	0.09	100.00	7.10	1.00	0.49	0.77
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	1.00	90	0.09	1000.00	22.44	1.00	0.49	0.58
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	1.00	204	0.09	2268.33	33.79	1.00	0.49	0.55
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	1.00	450	0.09	5000.00	50.17	1.00	0.49	0.53
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	1.00	900	0.09	10000.00	70.95	1.00	0.49	0.52
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	1.00	1800	0.09	20000.00	100.34	1.00	0.49	0.51
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	2.00	0.9	0.09	10.00	3.17	1.00	0.49	1.75
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	2.00	9	0.09	100.00	10.03	1.00	0.49	0.89
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	2.00	90	0.09	1000.00	31.73	1.00	0.49	0.62
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	2.00	204	0.09	2268.33	47.79	1.00	0.49	0.57
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	2.00	450	0.09	5000.00	70.95	1.00	0.49	0.55
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	2.00	900	0.09	10000.00	100.34	1.00	0.49	0.53
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	2.00	1800	0.09	20000.00	141.91	1.00	0.49	0.52
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	5.00	0.9	0.09	10.00	5.02	1.00	0.49	2.48
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	5.00	9	0.09	100.00	15.87	1.00	0.49	1.12
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	5.00	90	0.09	1000.00	50.17	1.00	0.49	0.69
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	5.00	204	0.09	2268.33	75.56	1.00	0.49	0.62
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	5.00	450	0.09	5000.00	112.19	1.00	0.49	0.58
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	5.00	900	0.09	10000.00	158.66	1.00	0.49	0.55
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	5.00	1800	0.09	20000.00	224.37	1.00	0.49	0.53

$\epsilon_{ox}$	$t_{ox}$	$t_{ox}$	$C_{ox}$	$\mu_n$	$\mu_n C_{ox}$	$I_d$	$W$	$L$	$W/L$	$g_m$	$R_d$	$V_m$	$V_{gs}$
(F/cm)	(Å)	(cm)	(fF/ $\mu^2$ )	(cm <sup>2</sup> /(V.s))	( $\mu$ A/V <sup>2</sup> )	(mA)	( $\mu$ m)	( $\mu$ m)		(mA/V)	(k $\Omega$ )	(V)	(V)
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	10.00	0.9	0.09	10.00	7.10	1.00	0.49	3.31
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	10.00	9	0.09	100.00	22.44	1.00	0.49	1.38
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	10.00	90	0.09	1000.00	70.95	1.00	0.49	0.77
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	10.00	204	0.09	2268.33	106.86	1.00	0.49	0.68
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	10.00	450	0.09	5000.00	158.66	1.00	0.49	0.62
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	10.00	900	0.09	10000.00	224.37	1.00	0.49	0.58
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	10.00	1800	0.09	20000.00	317.31	1.00	0.49	0.55
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	20.00	0.9	0.09	10.00	10.03	1.00	0.49	4.48
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	20.00	9	0.09	100.00	31.73	1.00	0.49	1.75
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	20.00	90	0.09	1000.00	100.34	1.00	0.49	0.89
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	20.00	204	0.09	2268.33	151.13	1.00	0.49	0.75
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	20.00	450	0.09	5000.00	224.37	1.00	0.49	0.67
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	20.00	900	0.09	10000.00	317.31	1.00	0.49	0.62
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	20.00	1800	0.09	20000.00	448.75	1.00	0.49	0.58
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	50.00	0.9	0.09	10.00	15.87	1.00	0.49	6.79
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	50.00	9	0.09	100.00	50.17	1.00	0.49	2.48
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	50.00	90	0.09	1000.00	158.66	1.00	0.49	1.12
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	50.00	204	0.09	2268.33	238.95	1.00	0.49	0.91
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	50.00	450	0.09	5000.00	354.77	1.00	0.49	0.77
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	50.00	900	0.09	10000.00	501.71	1.00	0.49	0.69
3.45E-13	23.3	2.33E-07	14.81	170.0	251.72	50.00	1800	0.09	20000.00	709.53	1.00	0.49	0.63

\* **Restriction of  $W/L$  due to the consideration of  $V_{gs}$**

- The underlined values of  $V_{gs}$  in the most right column in Table 4.1 are unacceptable because they are higher than  $0.7V$ , which is considered as a highest value of  $V_{gs}$  when the DC power supply is low, say,  $1.0$  to  $1.8 V$ .
- Therefore, the rows with the underlined values of  $V_{gs}$  in Table 4.1 must be abandoned in the selection of the ratio  $W/L$ . It implies that the ratio of  $W/L$  is restricted for the given values of  $I_d$  and  $g_m$  due to the limitation on  $V_{gs}$ .
- The rest rows in Table 4.1 are acceptable and are the candidates. They will be furthermore selected with the consideration of so-called “power-constrained noise optimization.”



\* **Optimum Width  $W_{opt}$  of Device**

$$W_{opt} = \frac{1}{3\omega LC_{ox} R_S}$$

where

$W_{opt}$  = Optimum width of device (MOSFET transistor);

$\omega$  = Operation angular frequency;

$L$  = Length of device (MOSFET transistor);

$C_{ox}$  = Capacitance per unit area of the gate oxide;

$R_S$  = Source resistance.

***Example:***

$$\epsilon_{ox} = 3.45 \times 10^{-13} \text{ F/cm},$$

$$t_{ox} = 23.3 \text{ \AA} = 23.3 \times 10^{-8} \text{ cm},$$

$$\mu_n = 170 \text{ cm}^2/\text{V-sec},$$

$$C_{ox} = 14.81 \text{ fF}/\mu^2,$$

$$V_{tn} = 0.49 \text{ V},$$

-----  
 $\mu_n C_{ox} = 251.72 \mu\text{A}/\text{V}^2.$

\* **Optimum of Length  $L_{opt}$  and Optimum of Width  $W_{opt}$  of Device**

$$W_{opt} = \frac{1}{3WL C_{ox} R_S}$$

$$I_d = \frac{m_n C_{ox}}{2} \frac{W_{opt}}{L} (V_{gs} - V_{th})^2$$

$$L = L_{opt} = \sqrt{\frac{m_n}{6WI_d R_S}} (V_{gs} - V_{th})$$
$$W = W_{opt} = \frac{1}{3WL_{opt} C_{ox} R_S}$$

## o Raw Device Set-up and Testing

\* The purpose of raw device testing is twofold:

- To see if this raw device can approach a good LNA design or not.  
A good LNA design is that  
The minimum of Noise figure and the maximum of gain  
can be obtained simultaneously.
- To create a starting point for impedance matching so as to continue the next design step.



\* **Set-up for raw device testing**


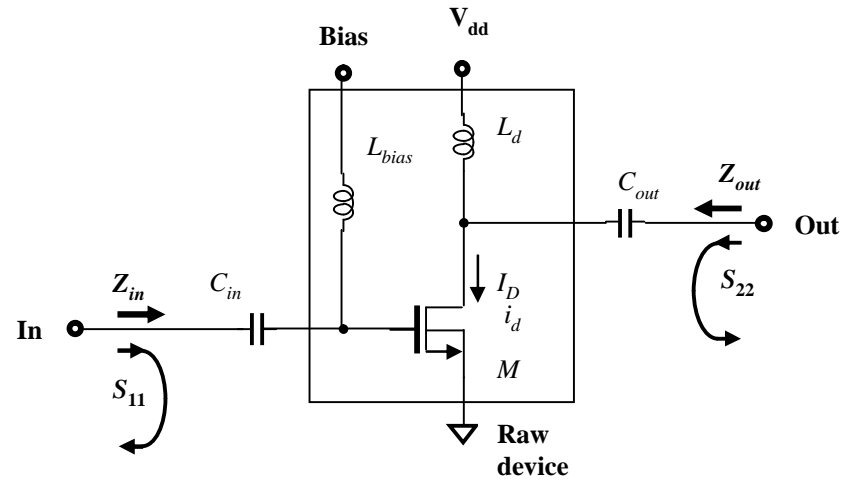


Figure 11.1 Setup for raw device testing,  $f=850$  to  $940$  MHz,  $I_D=2.6$  mA

$C_{in}, C_{out}$  : “Zero” capacitor;  
 $L_{bias}, L_c, L_d$  : “Infinite” inductor.

$$\frac{\Delta f}{f_o} = \frac{940 - 850}{895} = 10.05\%$$

\* **Raw device testing**  
**Main tested parameters:  $S_{11}$ ,  $\Gamma_{opt}$**

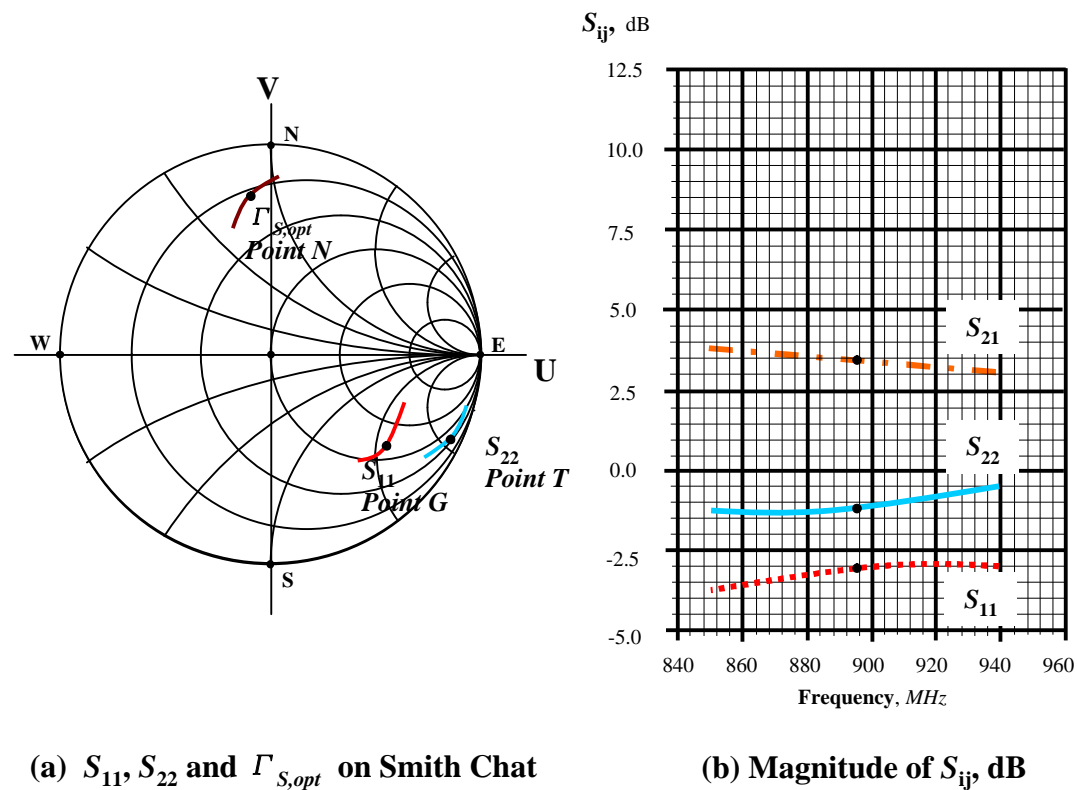

**Figure 11.2**  $S$  parameters from raw device testing,  $f=850$  to  $940$  MHz,  $I_D=2.6$  mA  
 (The intermediate frequency 895MHz is marked with dot on each trace.)

## \* Haus' Theory

(H. A. Haus et al., "Representation of Noise in Linear Twoports," Proceedings of the IRE, Vol. 48, pp. 69-74, January, 1960.)

$$NF = NF_{\min} + \frac{R_n}{G_s} \left[ \left( G_s - G_{S, \text{opt}} \right)^2 + \left( B_s - B_{S, \text{opt}} \right)^2 \right]$$

Where  $NF$  = Noise figure of the noisy block;  
 $NF_{\min}$  = Minimum of noise figure of the noisy block;  
 $R_n$  = Equivalent noise resistance;  
 $Y_s$  = Admittance of input source;  
 $G_s$  = Conductance of input source;  
 $B_s$  = Susceptance of input source.  
 $Y_{s, \text{opt}}$  = Optimum admittance of input source;  
 $G_{s, \text{opt}}$  = Optimum conductance of input source;  
 $B_{s, \text{opt}}$  = Optimum susceptance of input source.

$$Y_s = G_s + jB_s$$

$$Y_{s, \text{opt}} = G_{s, \text{opt}} + jB_{s, \text{opt}}$$

$$\Gamma_s = \Gamma_{s, \text{opt}}$$

\* **Raw device testing**  
**NF, Gain and NF circles**

At point G,  $G = G_{max} = 3.0 \text{ dB}$ , and  $NF = 8.7 \text{ dB}$ ,  
 At point N,  $G = -4.8 \text{ dB}$ , and  $NF = NF_{min} = 5 \text{ dB}$ .

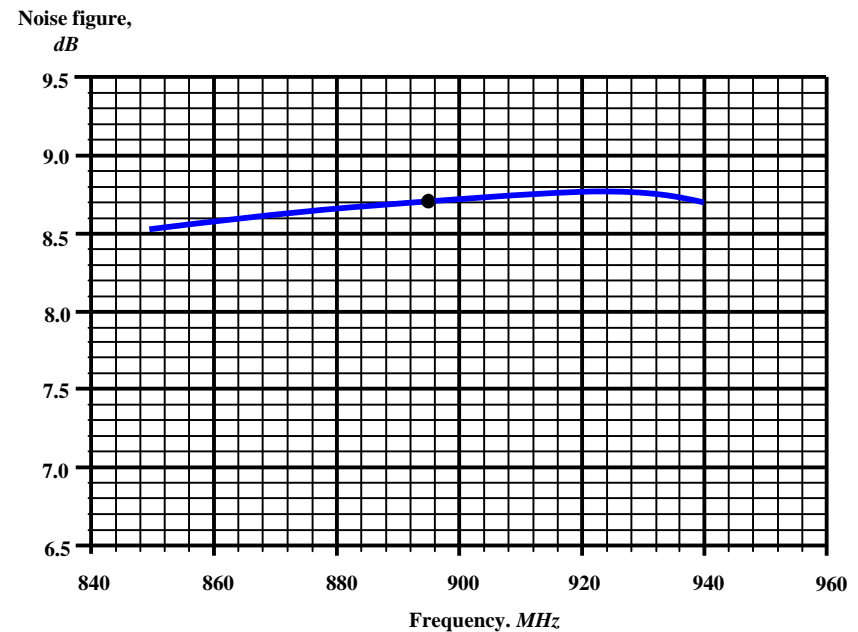
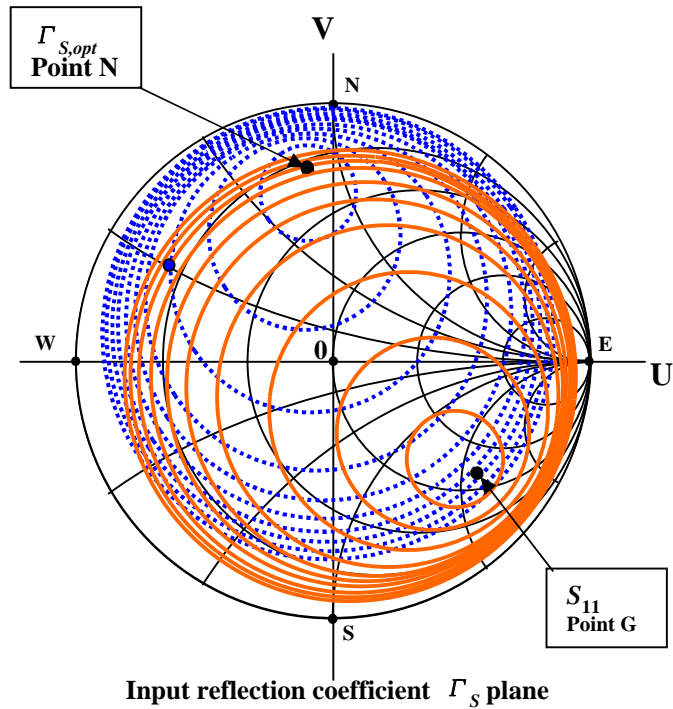


Figure 11.3 Noise Figure from 850 to 940 MHz,  $I_D = 2.6 \text{ mA}$ ,  $NF = 8.7 \text{ dB}$  when  $f = 895 \text{ MHz}$

Figure 11.3 Constant gain circles and constant noise figure circles when  $f = 895 \text{ MHz}$

- \* Gain circles:  $G_{max} = 3.0 \text{ dB}$  at point G, step =  $-1.0 \text{ dB}$ ,
- \* Noise figure circles:  $NF_{min} = 5 \text{ dB}$  at point N, step =  $0.5 \text{ dB}$ .

\* Impedance matching

Is it possible to pull the point G and N together after input impedance matching network is build?

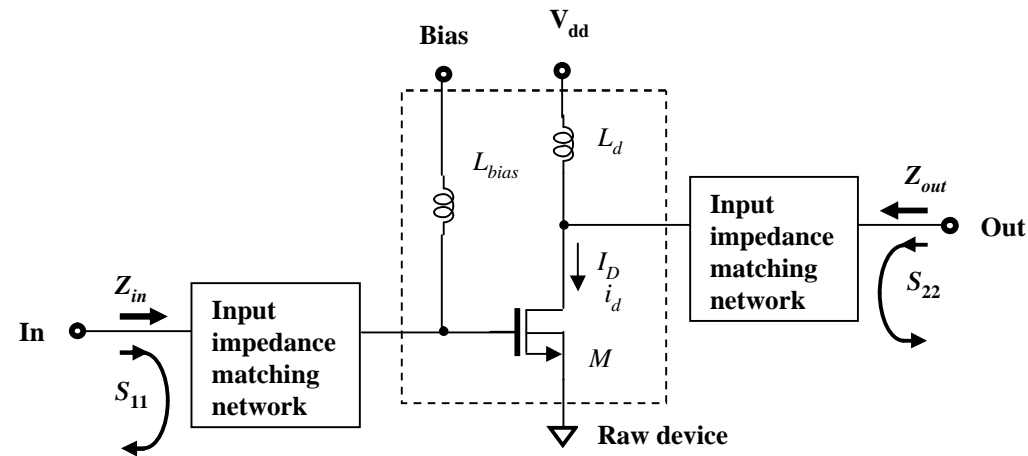



Figure 11.4 Input and output impedance matched networks are added to the raw device.

$f = 850$  to  $940$  MHz,  $I_D = 2.6$  mA  
 $C_{in}, C_{out}$  : “Zero” capacitor;  
 $L_{bias}, L_c, L_d$  : “Infinite” inductor.



\* The answer is

**Impedance matching is not a good assistant to the  $NF_{min}$ !  
Trade-off must be taken!**

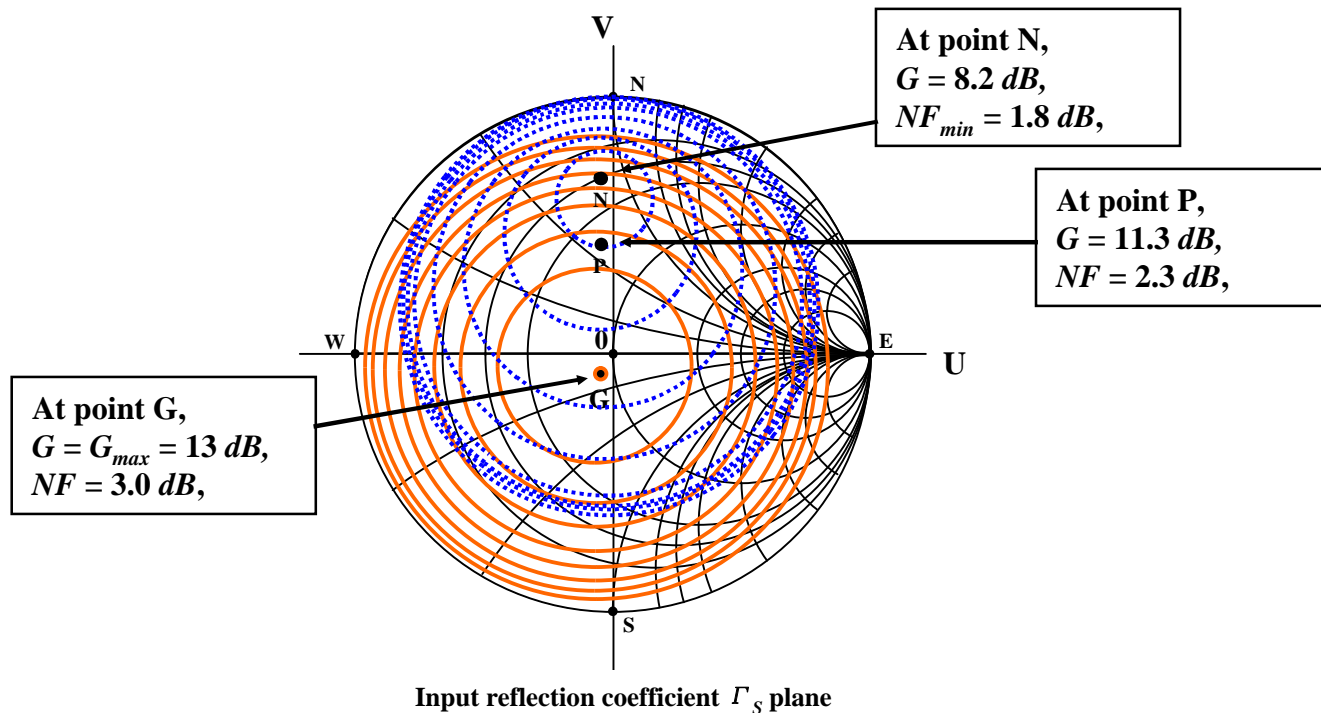

**Figure 11.5** Constant gain circles and constant noise figure circles when  $f = 895 \text{ MHz}$

- o Gain circles:  $G_{max} = 13 \text{ dB}$  at point G, step =  $1.0 \text{ dB}$ ,
- o Noise figure circles:  $NF_{min} = 1.8 \text{ dB}$  at point N, step =  $0.5 \text{ dB}$ ,

## o Challenge for a good LNA design

### \* Optimum of Source Reflection coefficient, $\Gamma_{opt}$

- In order to enable the raw device approaching to the minimum of noise figure,  $\Gamma_{S,opt}$  is a required optimum of source reflection coefficient,  $\Gamma_S$ , looked from the raw device toward the source.
- On the other hand, in order to enable the raw device approaching to the maximum of gain,  $G_{max}$ ,  $S_{11}^*$  is a required value of source reflection coefficient,  $\Gamma_S$ , looked from the raw device toward the source since the actual reflection coefficient looked from the source toward the raw device is  $S_{11}$ .

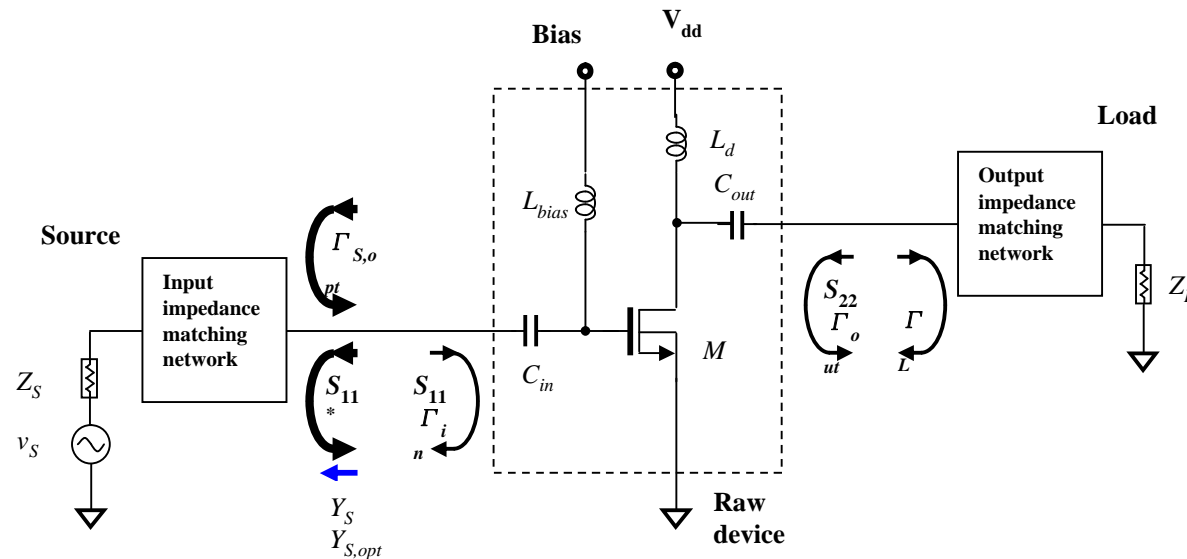


Figure 11.6 Directions of  $\Gamma_{S,opt}$ ,  $\Gamma_{in}$  and  $\Gamma_{out}$ ,  $S_{11}$  and  $S_{11}^*$  in the schematic for the raw device testing

\* **Key Issue**

$$\Gamma_{S,opt} = S_{11}^*$$

\* **Schemes to satisfy the condition:**  $\Gamma_{S,opt} = S_{11}^*$

1) **Increase or decrease of current drain,  $I_D$ ,**

The S parameters as well as the values of  $\Gamma_{S,opt}$  will be changed as the current drain is varied.  
The condition,  $\Gamma_{S,opt} = S_{11}^*$ , could be reached at an appropriate amount of current drain.

2) **Change of device size,**


The S parameters as well as the values of  $\Gamma_{S,opt}$  will be changed as the device size is varied.  
The condition,  $\Gamma_{S,opt} = S_{11}^*$ , could be reached at an appropriate device size.  
Of course, this scheme is only possible to the IC designer but not to the designer who implements the circuits by discrete parts.

3) **Addition of degeneration part,**

Up to the design experience in the practical design, this is an easy way to get success.

4) **And so on.**

\* **Addition of degeneration inductor**

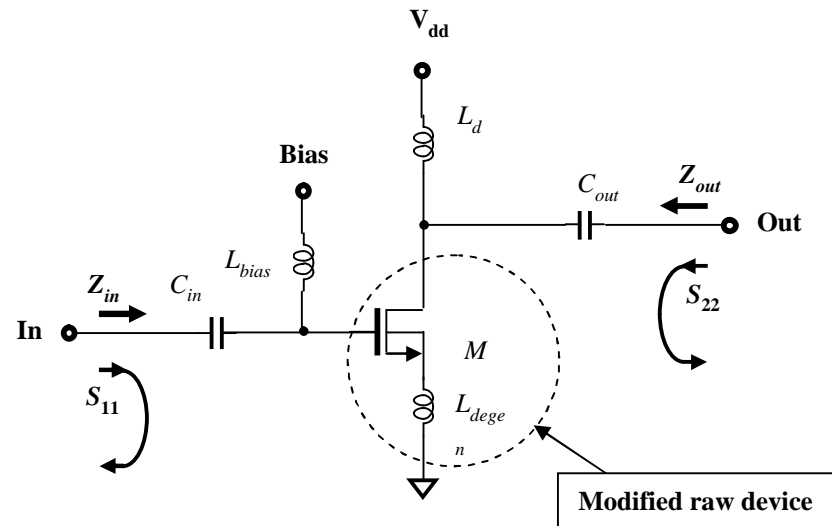


**Figure 11.7** Setup for modified raw device testing by adding of degeneration inductor

$L_{degen}$  : Degeneration inductor.

$C_{in}$ ,  $C_{out}$  : “Zero” capacitor;

$L_{bias}$ ,  $L_c$ ,  $L_d$  : “Infinite” inductor.

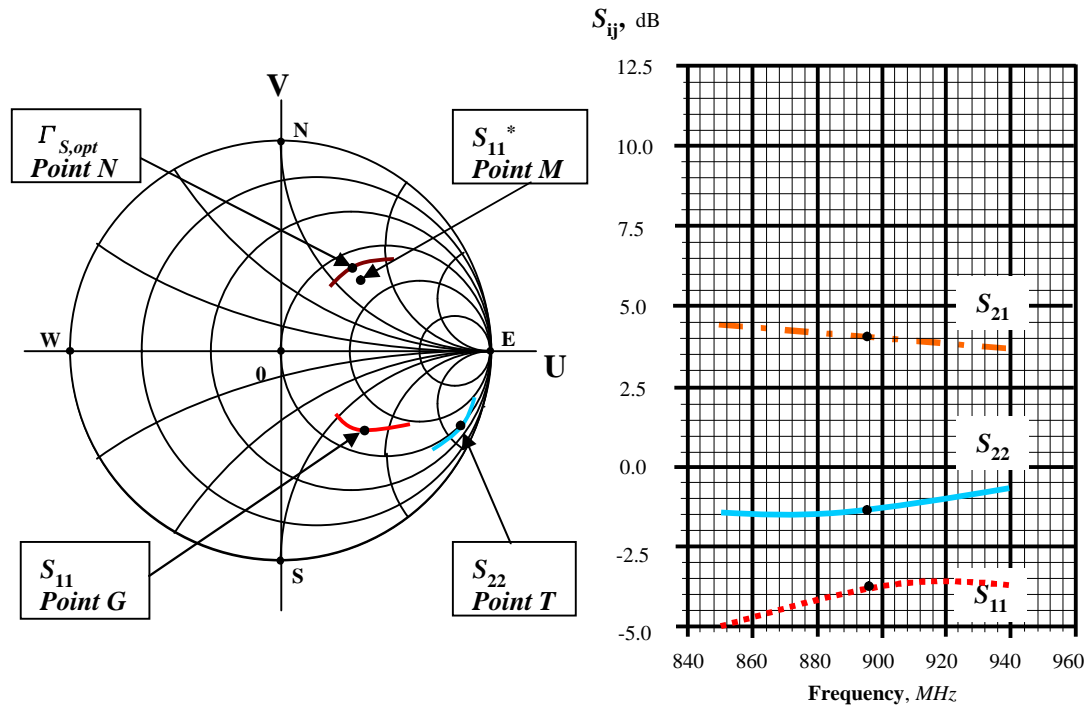\*  $S_{11}$  and  $\Gamma_{opt}$  adjusted by degeneration inductor



(a)  $S_{11}$ ,  $S_{22}$  and  $\Gamma_{S,opt}$  on Smith Chart

(b) Magnitude of  $S_{ij}$ , dB

Figure 11.8  $S$  parameters from modified raw device testing,  $f = 850 - 940$  MHz,  $I_D = 2.6$  mA (The intermediate frequency 895 MHz is marked with dot on each trace.)

\* **Variation of Input Impedance due to Degeneration Inductor**


**1) MOSFET**

$$v_{in} = i_{in} \left( jL_g W + \frac{1}{jC_{gs} W} \right) + (i_{in} + i_d) jL_{deg en} W = i_{in} j \left( L_g W - \frac{1}{C_{gs} W} \right) + (i_{in} + g_m V_{gs}) jL_{deg en} W$$


$$v_{in} = i_{in} j \left( L_g W - \frac{1}{C_{gs} W} \right) + \left( i_{in} + g_m i_{in} \frac{1}{jC_{gs} W} \right) jL_{deg en} W$$

$$Z_{in} = \frac{v_{in}}{i_{in}} = R_{in} + jX_{in}$$
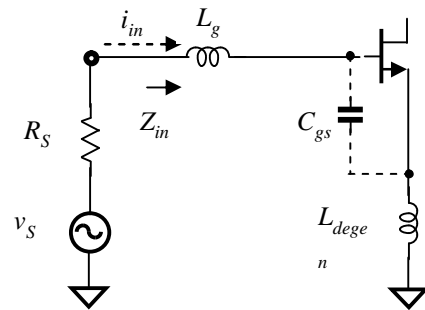
$$Z_{in} = j(L_g + L_{deg en})W + \frac{1}{jC_{gs} W} + \frac{g_m}{C_{gs}} L_{deg en} = j \left[ (L_g + L_{deg en})W - \frac{1}{C_{gs} W} \right] + L_{deg en} W_T$$



(a) Input stage

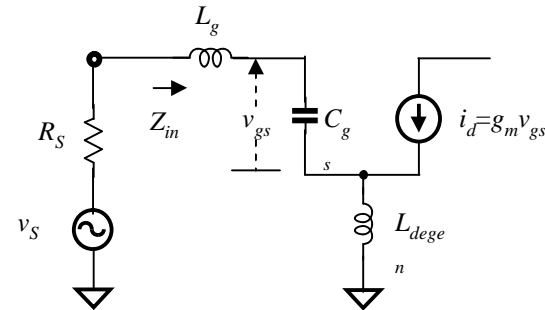

(b) Equivalent of input stage

**Figure 11.9** The input stage of MOSFET transistor with common source configuration


## 2) Bipolar

$$r_p \parallel C_p = \frac{r_p}{1 + jC_p \omega r_p} = \frac{r_p}{1 + (C_p \omega r_p)^2} - j \frac{C_p \omega r_p^2}{1 + (C_p \omega r_p)^2}$$


$$v_{in} = i_{in} (r_b + r_p \parallel C_p) + (i_{in} + i_c) L_{degen} \omega \quad i_c = g_m v_{be} = g_m i_{in} (r_p \parallel C_p)$$

$$Z_{in} = \frac{v_{in}}{i_{in}} = r_b + r_p \parallel C_p + j[1 + (r_p \parallel C_p) g_m] L_{degen} \omega$$
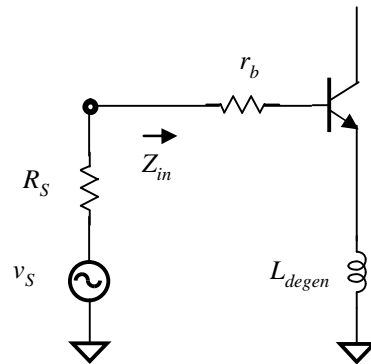
$$Z_{in} = r_b + r_p + \frac{L_{degen} C_p \omega^2 g_m r_p^2}{1 + (C_p \omega r_p)^2} + j \left[ 1 + \frac{\left( g_m - \frac{C_p}{L_{degen}} r_p \right) r_p}{1 + (C_p \omega r_p)^2} \right] L_{degen} \omega$$



(a) Schematic of input stage

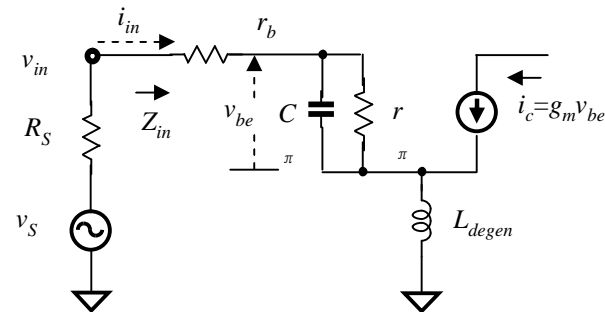


(b) Equivalent of input stage


Figure 11.10 The input stage of a bipolar transistor with a degeneration inductor



\* **Input and output impedance matching**

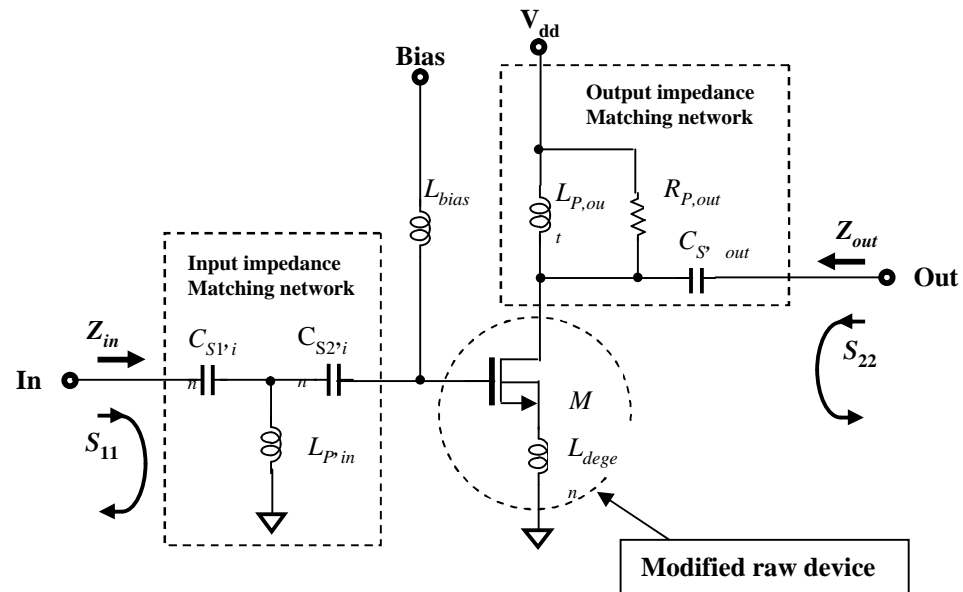

**Figure 11.11 Impedance matching of modified raw device by parts:**  
 At input :  $C_{S1,in} = 1 \text{ pF}$ ,  $L_{P,in} = 20 \text{ nH}$ ,  $C_{S2,in} = 39 \text{ pF}$ .  
 At output :  $L_{P,out} = 15 \text{ nH}$ ,  $R_{P,out} = 1500 \text{ } \Omega$ , and  $C_{S',out} = 1.6 \text{ pF}$

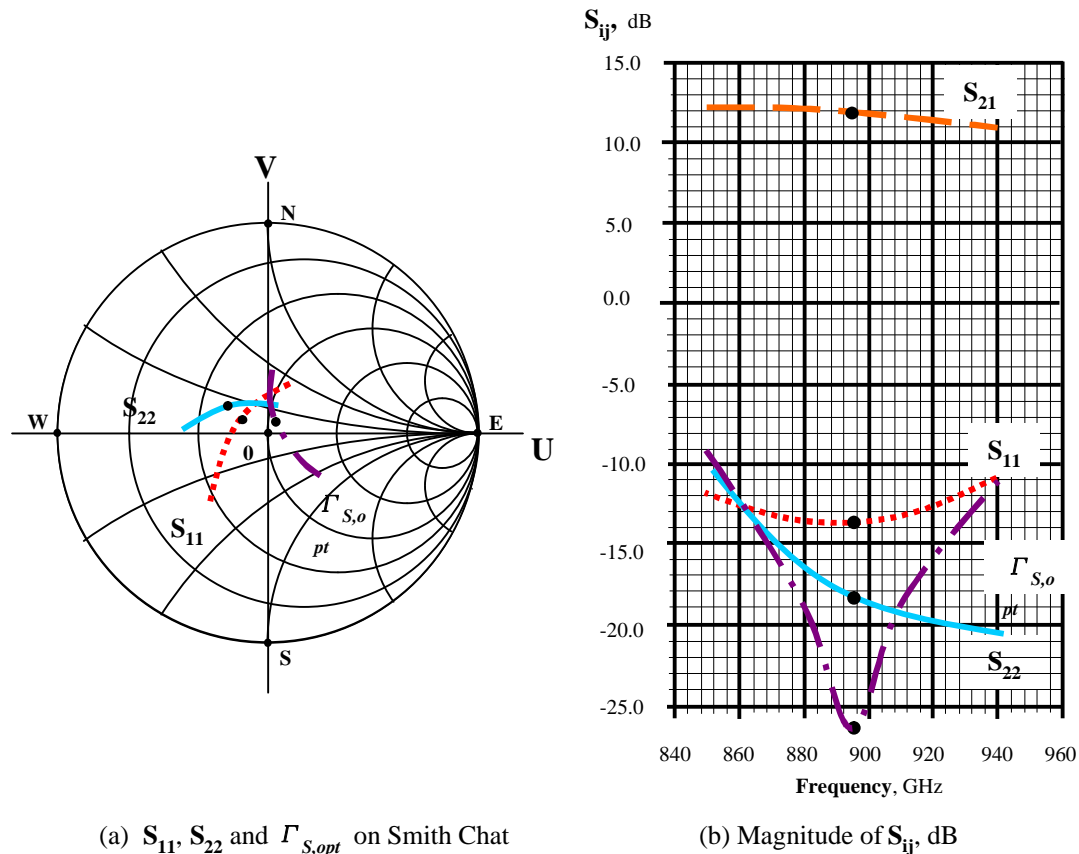


**Figure 11.12**  $S$  parameters of the design example,  $f=850$  - $940$  MHz,  $I_D=2.6$  mA  
 (The intermediate frequency 895MHz is marked with dot on each trace.)

The input and output impedances are matched by parts:


At input:  $C_{SP,in} = 1$  pF,  $L_{P,in} = 20$  nH,  $C_{S2,in} = 39$  pF.

At output:  $L_{P,out} = 15$  nH,  $R_{P,out} = 1500$   $\Omega$ ,  $C_{S,out} = 1.6$  pF

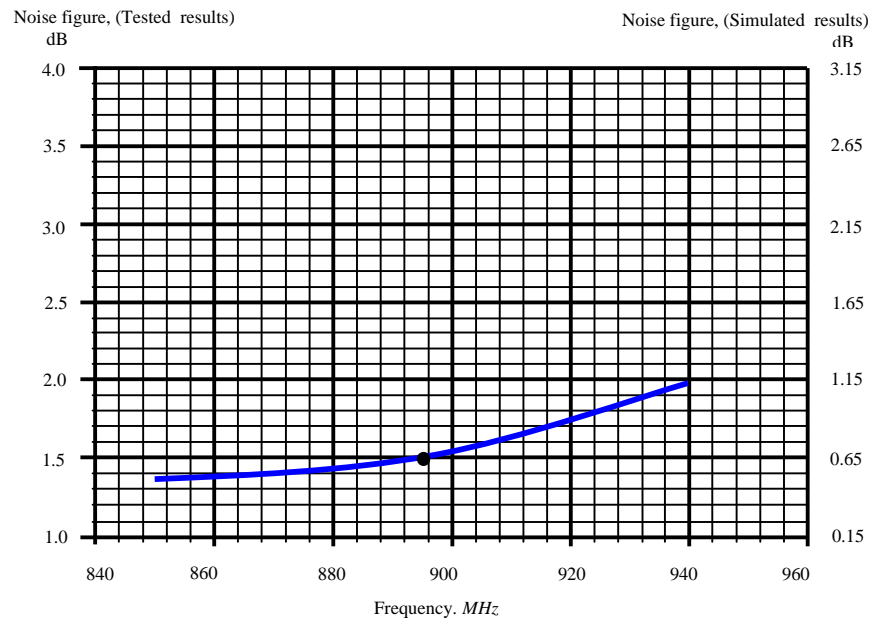

**Figure 11.13** Noise Figure of the design example,  
 $f = 850$  to  $940$  MHz,  $I_D = 2.6$  mA

$NF = 1.5$  dB when  $f = 895$  GHz

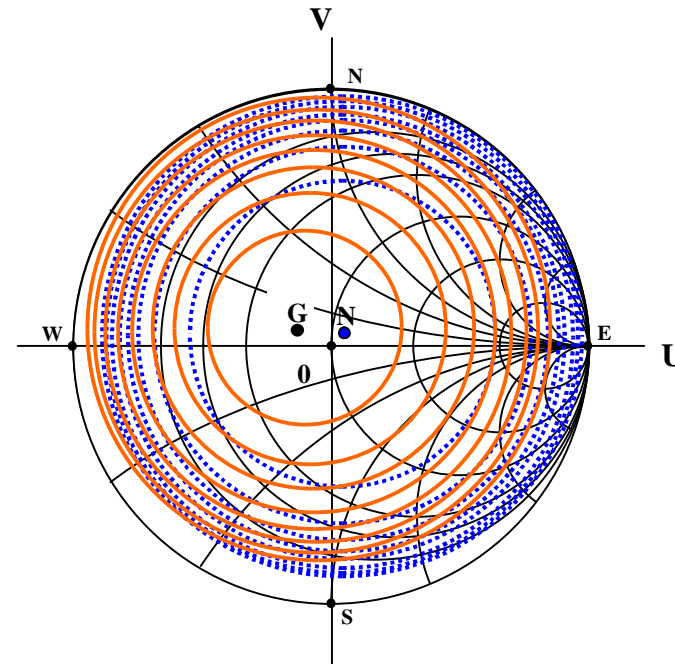

**Figure 11.14** Constant gain circles and constant noise figure circles

when  $f = 895$  MHz

Gain circles:  $G_{max} = 12$  dB at point G, step = 1.0 dB,

NF circles:  $NF_{min} = 1.5$  dB at point N, step = 0.5 dB.

$$\mu = 1.1 > 1$$

$$G = 12 \text{ dB}$$

$$NF = 1.5 \text{ dB}$$

## o Stability

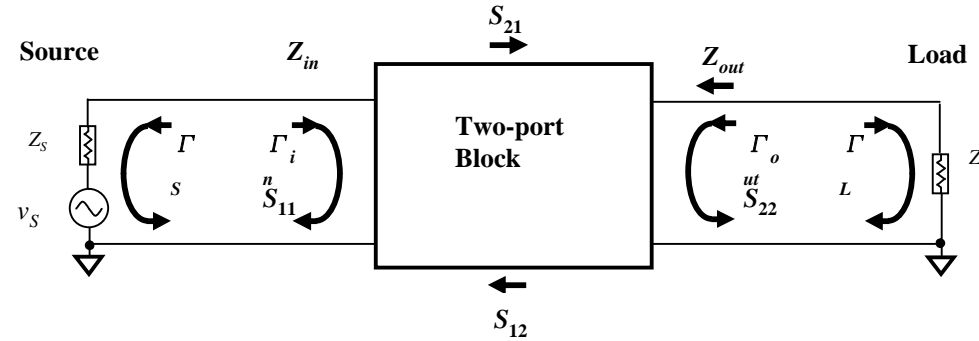


Figure 11.15 Different reflection coefficients and S parameters in a two-port block

$$\begin{aligned}
 |\Gamma_S| < 1 & \quad K = 1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2 \\
 |\Gamma_L| < 1 & \quad K > 1 \\
 |\Gamma_{in}| < 1 & \quad |\Delta| = |S_{11}S_{22} - S_{12}S_{21}| \\
 |\Gamma_{out}| < 1 & \quad |\Delta| < 1
 \end{aligned}$$

$$m = \frac{1 - [mag(S_{11})]^2}{mag[S_{22} - \Delta conj(S_{11})] + mag(S_{21}S_{12})}$$

$$m > 1$$


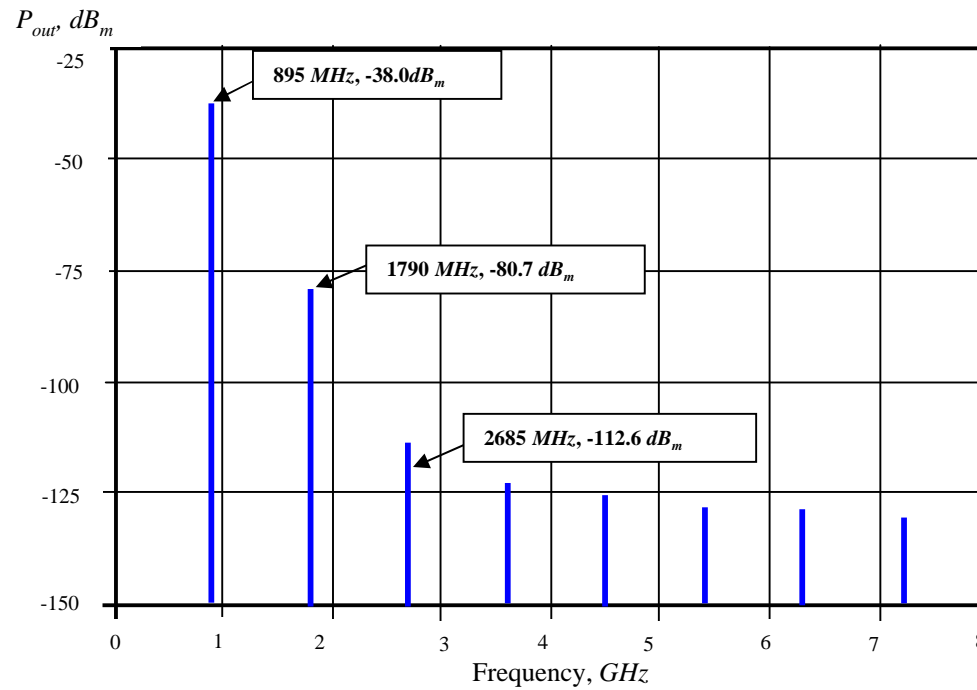


Figure 11.16 Spectrum at LNA output ,  $f_o = 895 \text{ MHz}$ ,  $P_{in} = -50 \text{ dB}_m$

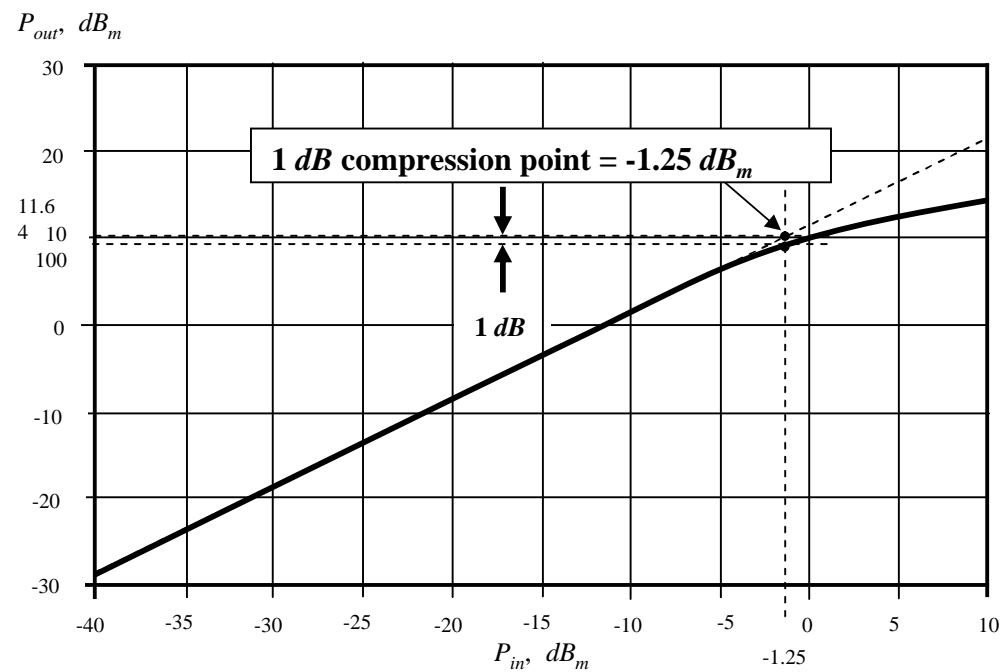

**Figure 11.17** 1dB compression point when  $f_o = 895$  MHz

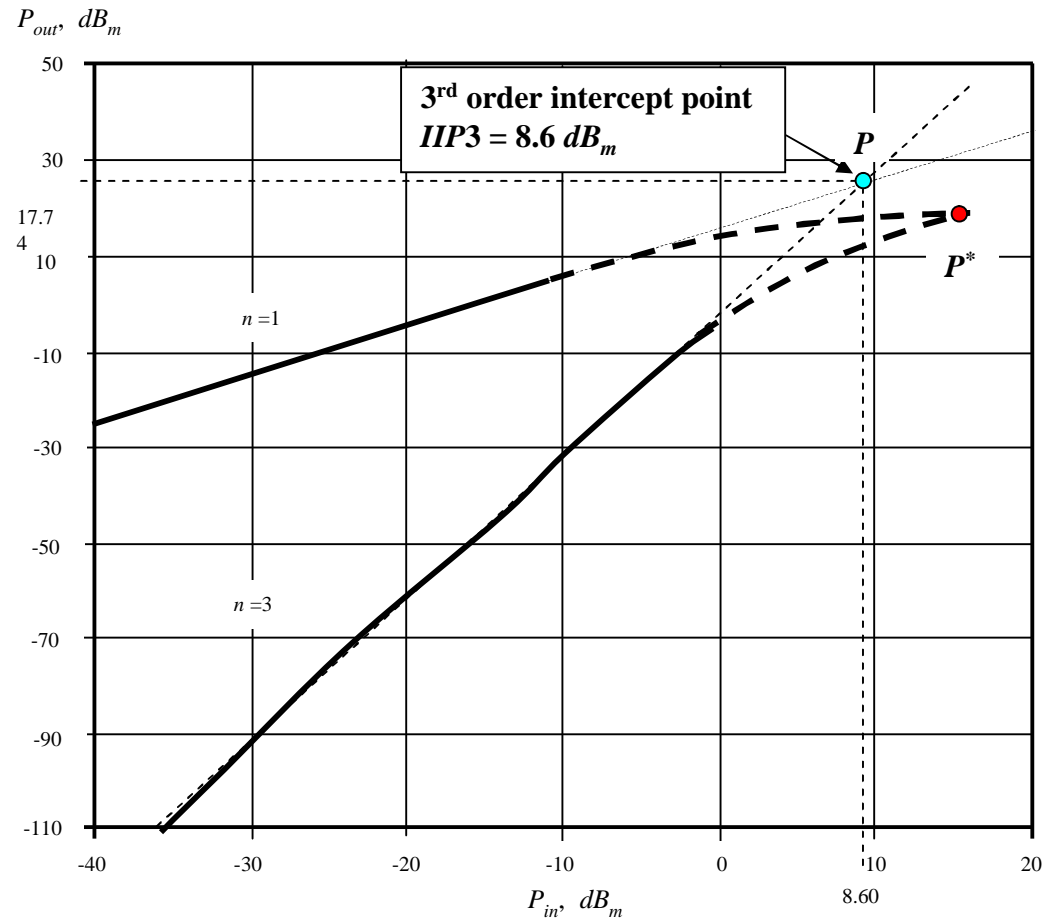


Figure 11.18 3<sup>rd</sup> order input intercept point when  $f_o = 895$  MHz



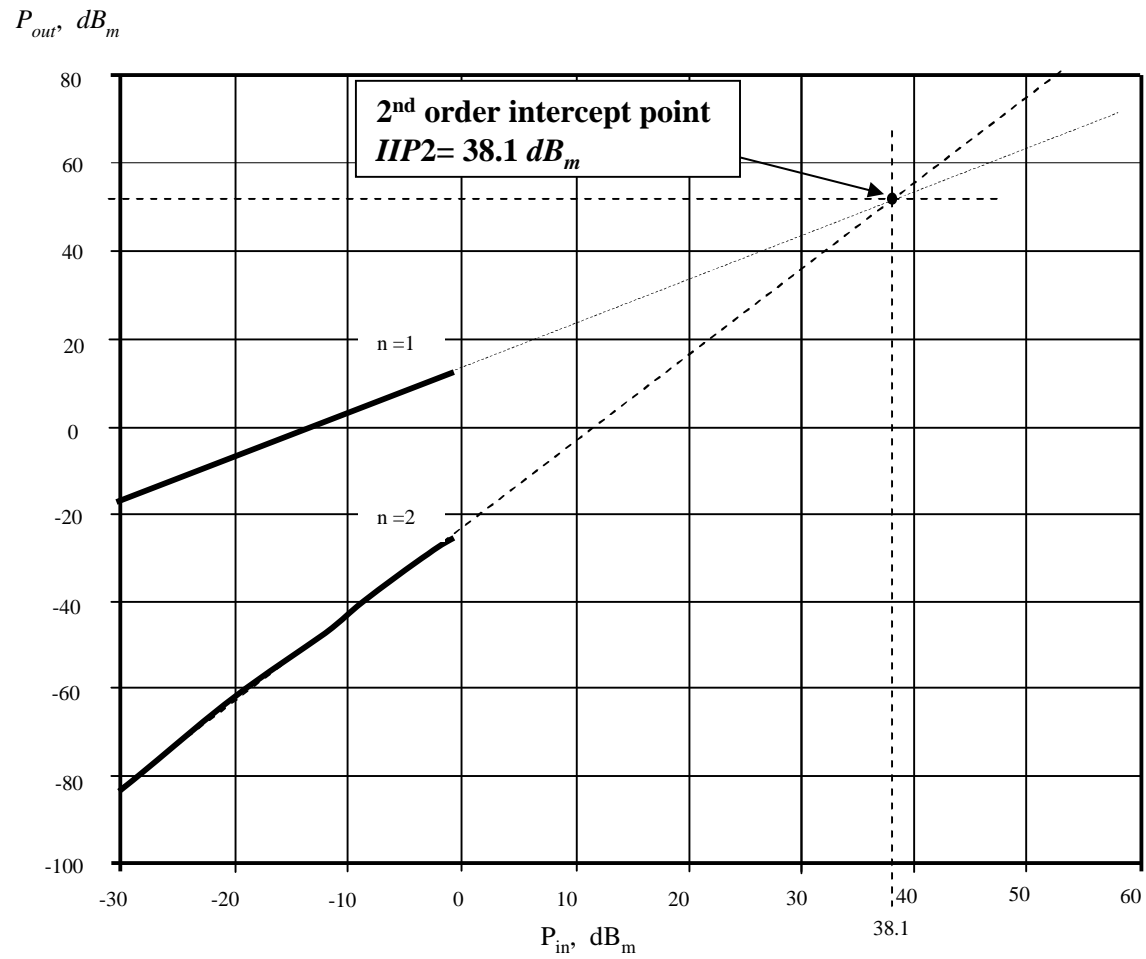


Figure 11.19 2<sup>nd</sup> order input intercept point when  $f_o = 895 \text{ MHz}$


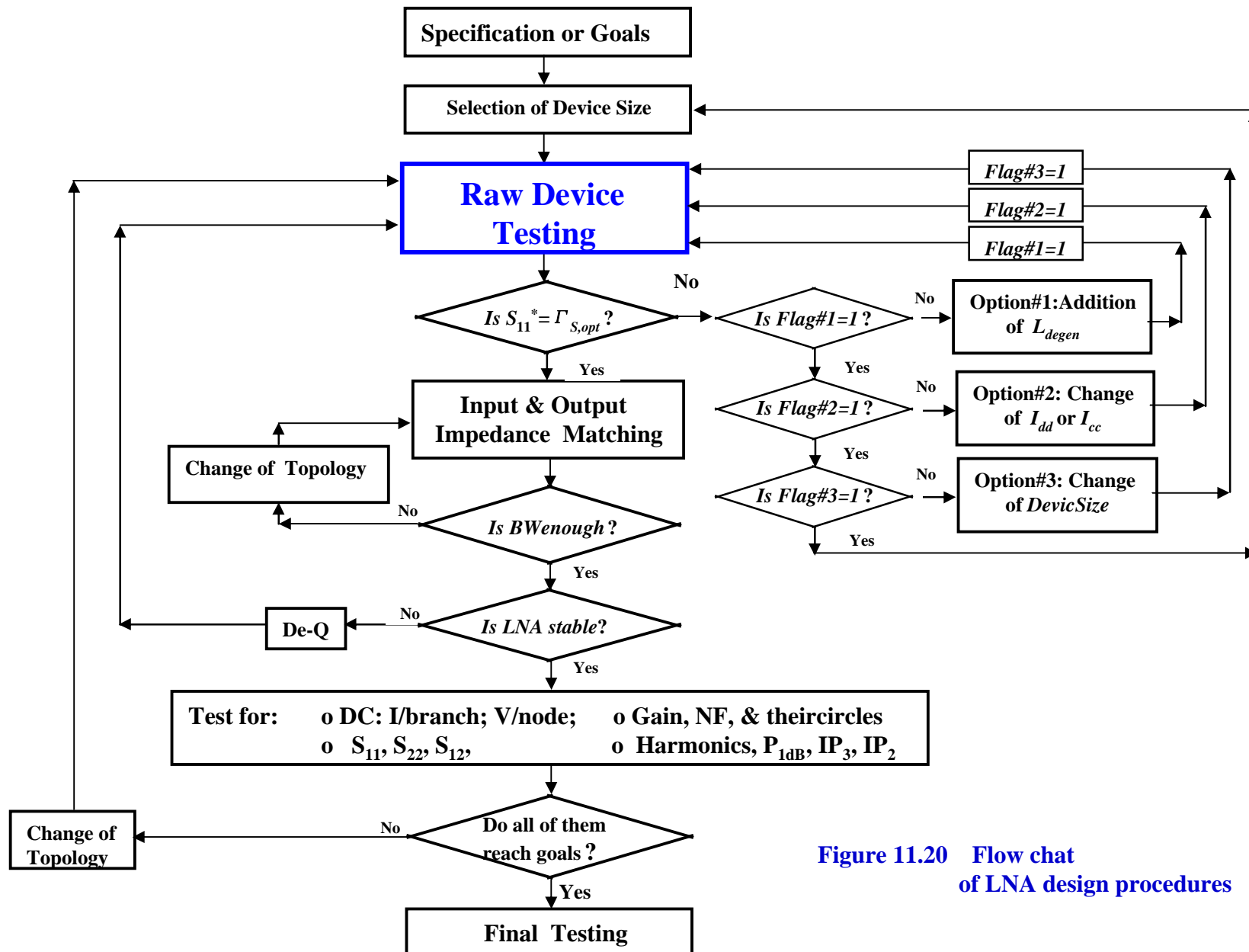


Figure 11.20 Flow chat of LNA design procedures

## o Other examples

### \* LNA Design for VHF radio


	<u>Specification</u>		<u>Final tested result</u>	
Frequency range	130 MHz to 180 MHz			
Device	BFQ67 (Manufactured by Siemens)			
DC power supply	3	V		
Current drain	< 4	mA	3.47	mA
Gain	> 10	dB	15.0	dB
Noise Figure	< 2	dB	1.75	dB
IIP3	> 0	dBm	2.5	dBm
Input return	< -10	dB	-40.0	dB
Output return	< -10	dB	-12.2	dB

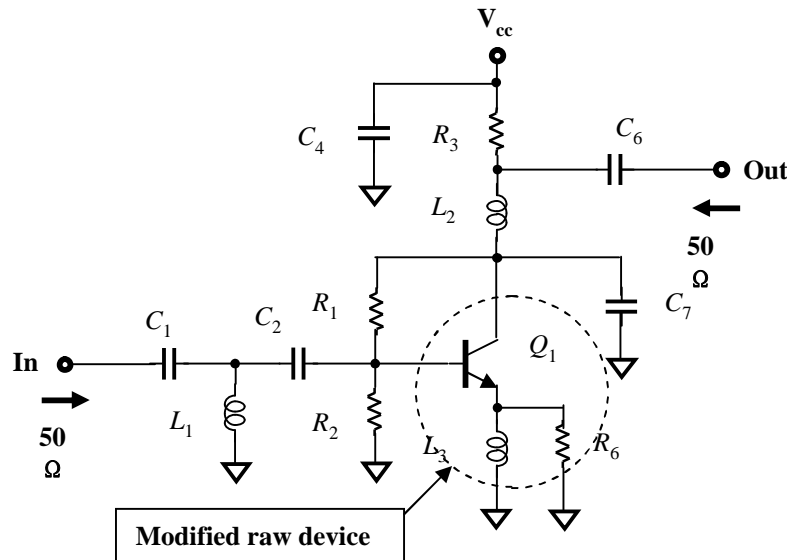

#### Part list (Purchased from MuRata)

$C_1$	13 pF
$C_2$	1500 pF
$C_4$	1500 pF
$C_6$	1500 pF
$C_7$	6.2 pF
$L_1$	92 nH
$L_2$	92 nH
$L_3$	33 nH
$R_1$	3.3 k $\Omega$
$R_2$	3.3 k $\Omega$
$R_3$	390 $\Omega$
$R_6$	100 $\Omega$
$Q_1$	BFQ67

Figure 11.21 LNA designed for VHF radio

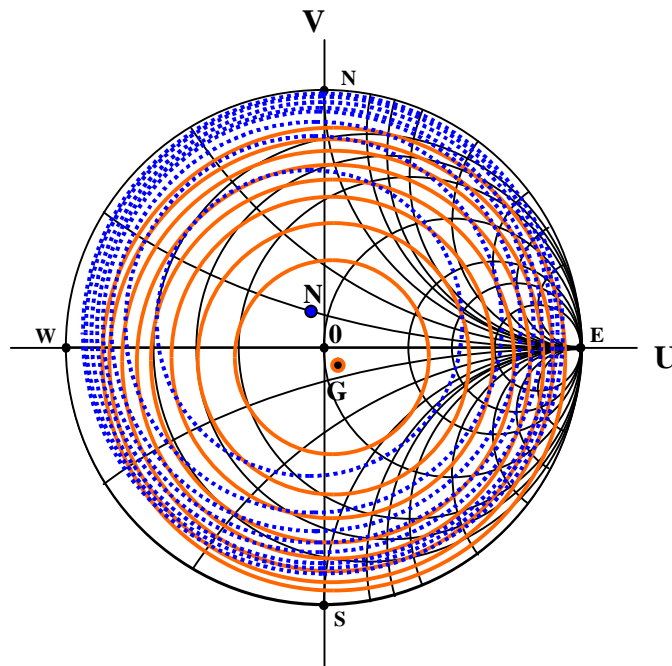


**Figure 11.22** Constant gain circles and constant noise figure circles when  $f = 150$  MHz

- o Gain circles:  $G_{\max} = 15$  dB at point G, step = 1.0 dB,
- o Noise figure circles:  $NF_{\min} = 1.75$  dB at point N, step = 0.25 dB,

## o Other examples

### \* LNA Design for UHF radio

	<u>Specification</u>		<u>Final tested result</u>	
Frequency range	400 MHz to 470 MHz			
Device	BFQ67 (Manufactured by Siemens)			
DC power supply	3	V		
Current drain	< 4	mA	3.43	mA
Gain	> 10	dB	12.0	dB
Noise Figure	< 2	dB	1.5	dB
IIP3	> 0	dBm	5.0	dBm
Input return	< -10	dB	-17.8	dB
Output return	< -10	dB	-16.0	dB

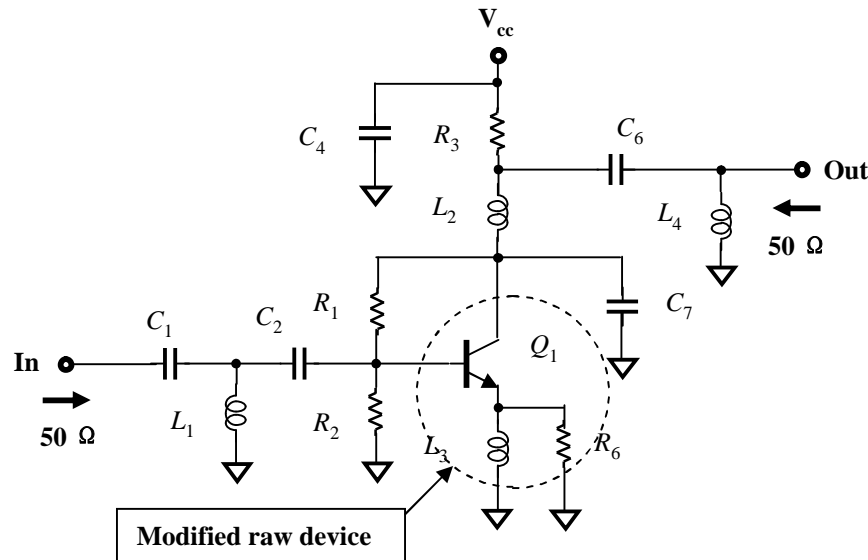


#### Part list

(Purchased from MuRata)

$C_1$	10 pF
$C_2$	150 pF
$C_4$	150 pF
$C_6$	150 pF
$C_7$	1.5 pF
$L_1$	33 nH
$L_2$	33 nH
$L_3$	5.6 nH
$L_4$	33 nH
$R_1$	3.3 k $\Omega$
$R_2$	3.3 k $\Omega$
$R_3$	390 $\Omega$
$R_6$	390 $\Omega$
$Q_1$	BFQ67

Figure 11.23 LNA designed for UHF radio

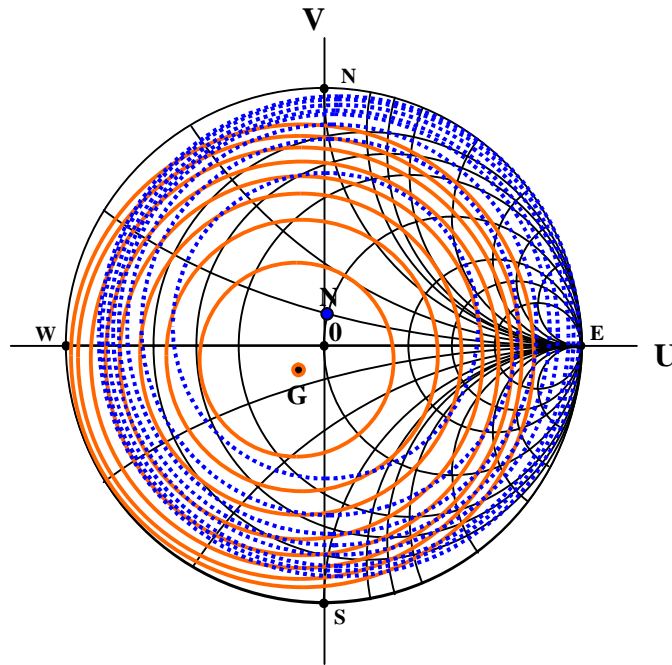


**Figure 11.24** Constant gain circles and constant noise figure circles when  $f = 450$  MHz

- o Gain circles:  $G_{\max} = 12$  dB at point G, step = 1.0 dB,
- o Noise figure circles:  $NF_{\min} = 1.5$  dB at point N, step = 0.25 dB,

## o Other examples

### \* LNA Design for 800/900 MHz radio

	<u>Specification</u>		<u>Final tested result</u>	
Frequency range	850 MHz to 940 MHz			
Device	BFQ67 (Manufactured by Siemens)			
DC power supply	3	V		
Current drain	< 4	mA	3.48	mA
Gain	> 10	dB	11.0	dB
Noise Figure	< 2	dB	1.8	dB
IIP3	> 0	dBm	8.6	dBm
Input return	< -10	dB	-11.7	dB
Output return	< -10	dB	-17.0	dB

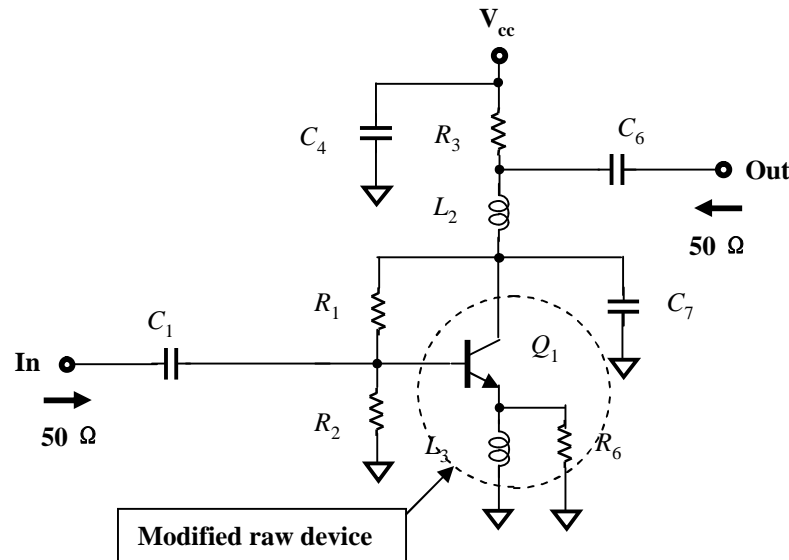


#### Part list

(Purchased from  
MuRata)

$C_1$	150 pF
$C_4$	39 pF
$C_6$	39 pF
$L_2$	33 nH
$L_3$	4.7 nH
$R_1$	3.3 k $\Omega$
$R_2$	3.3 k $\Omega$
$R_3$	390 $\Omega$
$R_6$	390 $\Omega$
$Q_1$	BFQ67

Figure 11.25 LNA designed for 800/900 MHz radio

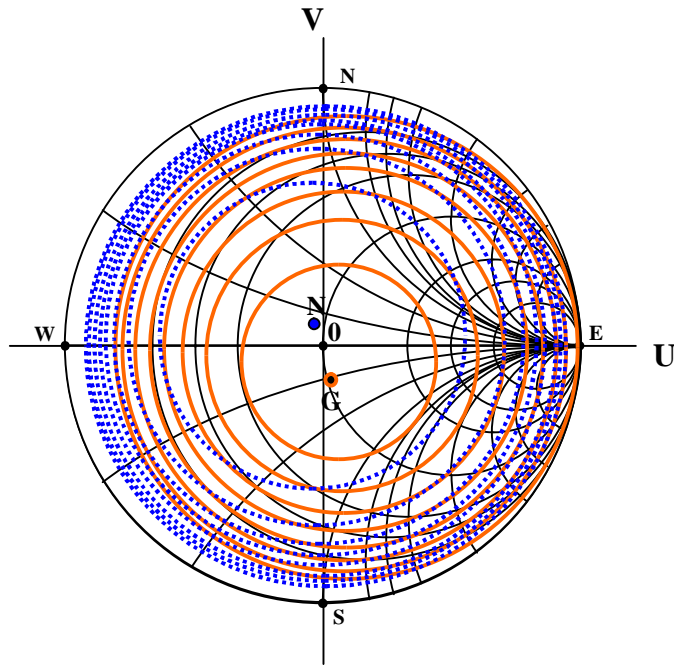

**Figure 11.26** Constant gain circles and constant noise figure circles when  $f = 850$  MHz

- Gain circles:  $G_{\max} = 11$  dB at point G, step = 1.0 dB,
- Noise figure circles:  $NF_{\min} = 1.8$  dB at point N, step = 0.25 dB.



## o Single-ended CascodeLNA

\* Bipolar CE-CB cascode devices

$$R_i = R_{i1} = r_{p1}$$

$$R_{i2} = r_{e2} = \frac{1}{g_{m2} + \frac{1}{r_{p2}}} = \frac{1}{1 + b_2} r_{p2} \approx \frac{r_{p2}}{b_2}$$

$$R_{o1} = r_{o1}$$

$$R_o = r_{o2} \left( 1 + \frac{g_{m2} r_{o1}}{1 + \frac{g_{m2} r_{o1}}{b_2}} \right) \quad R_o \approx b_2 r_{o2}$$

if  $g_{m2} r_{o1} \gg b_2 \gg 1$

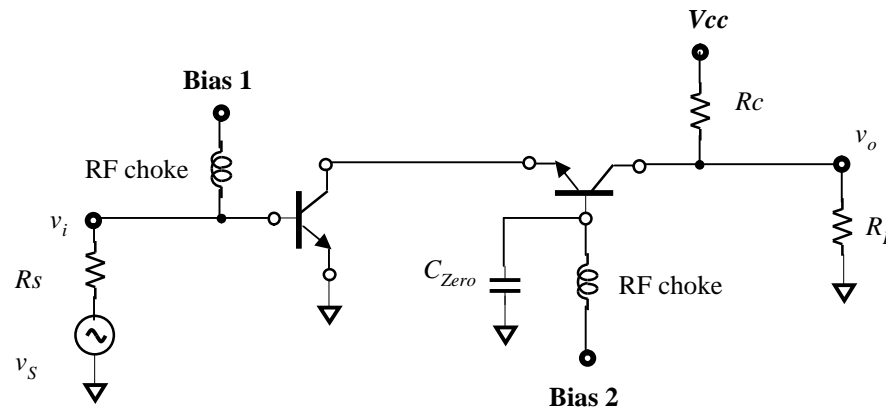


Figure 11.27 A bipolar cascode amplifier

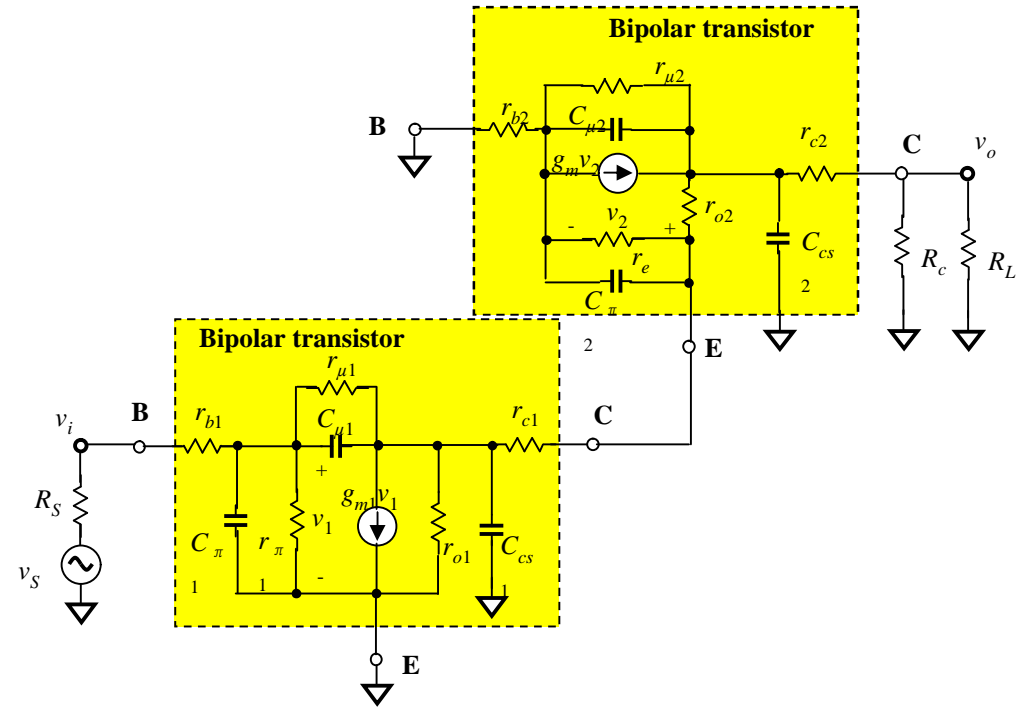


Figure 11.28 Equivalent circuit of bipolar cascode amplifier with CE-CB configuration

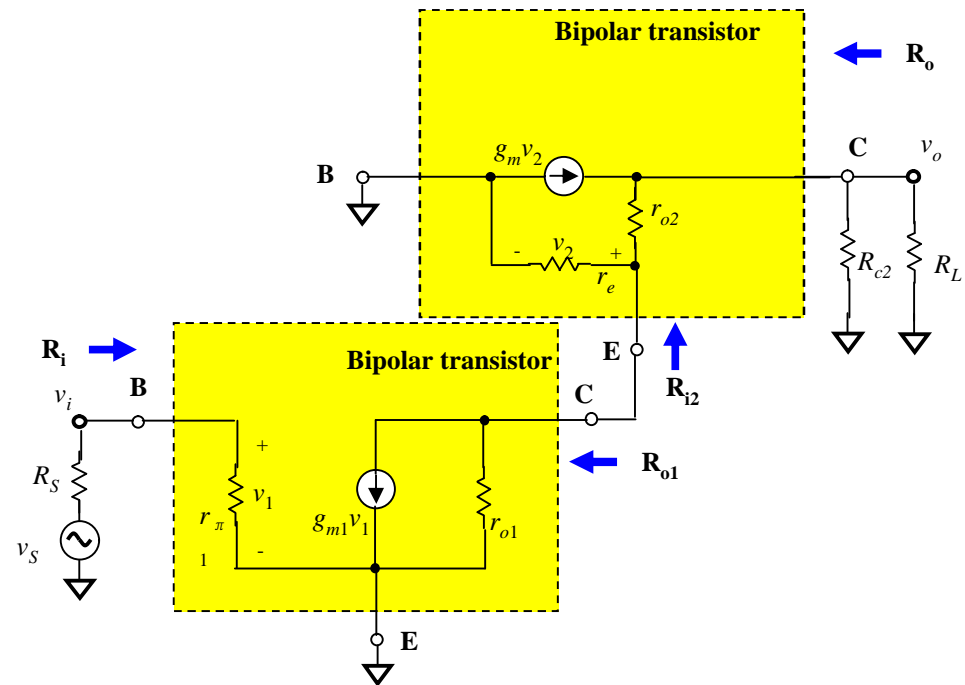


Figure 11.29 Equivalent circuit of bipolar cascode amplifier with CE-CB configuration at low frequencies and the resistors,  $r_b$ ,  $r_\mu$ , and  $r_c$ , are neglected

$$A_{v1} = -g_{m1}r_{o1} // R_{i2} \approx -g_{m1} \frac{r_{p2}}{b_2}$$

Assume that

$$g_{m1} = g_{m2}$$

$$r_{p1} = r_{p2}$$

$$b_1 = b_2$$

$$G_m = g_{m1}$$

Then,

$$A_{v1} = -1$$

$$A_v = \frac{v_o}{v_i} \approx -G_m R_o \approx -g_{m1} r_{o2} b_2$$

$$A_{i1} = b$$

$$A_{i2} \approx 1 \quad \text{because } i_{i2} \approx i_{o2}$$

$$A_i \approx A_{i1} A_{i2} \approx b$$

\* **MOSFET CS-CG cascode devices**


$$R_i \rightarrow \infty$$

$$R_{i2} = \frac{1}{(g_{m2} + g_{mb2})} + \frac{R_L'}{(g_{m2} + g_{mb2})r_{o2}} \quad R_L' = R_d // R_L = \frac{R_d}{R_D + R_L} R_L$$

$$R_{i2} \approx \frac{1}{(g_{m2} + g_{mb2})}$$

$$G_m \approx g_{m1}$$

$$R_o = r_{o1} + r_{o1} + (g_{m2} + g_{mb2})r_{o1}r_{o2} \approx (g_{m2} + g_{mb2})r_{o1}r_{o2}$$

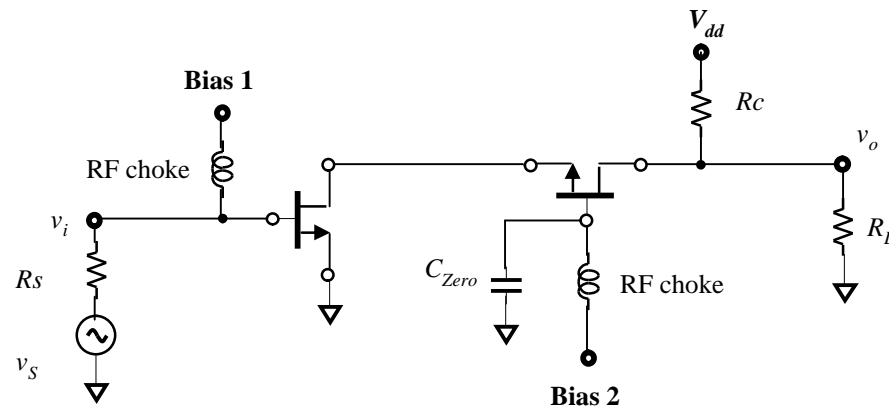

**Figure 11.30** A MOSFET cascode amplifier

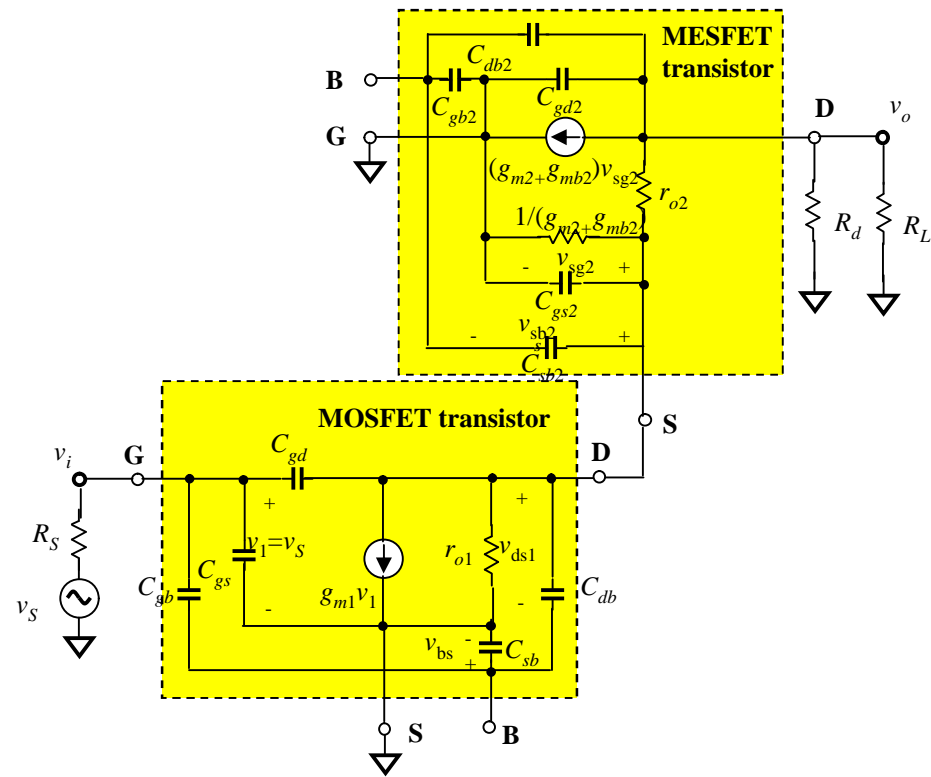


Figure 11.31 Equivalent circuit of MOSFET cascode amplifier with CS-CG configuration

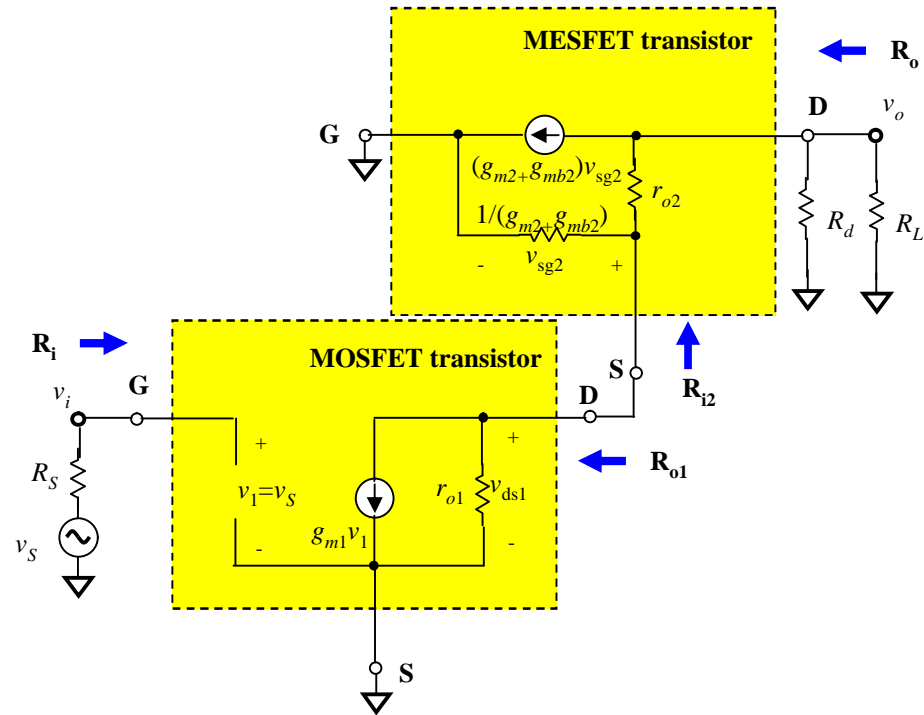


Figure 11.32 Equivalent circuit of MOSFET cascode amplifier with CS-CG configuration at low frequencies.

$$A_{v1} = -g_{m1} r_{o1} // R_{i2} \approx -g_{m1} R_{i2} \approx -\frac{g_{m1}}{g_{m2} + g_{mb2}}$$

$$g_{m1} = g_{m2}$$

$$A_{v1} \approx -1$$

$$A_{i1} \rightarrow \infty$$

$$A_{i2} \approx 1$$

$$A_v = \frac{v_o}{v_i} \approx -G_m R_o \approx -g_{m1} (g_{m2} + g_{mb2}) r_{o1} r_{o2}$$



## o Why Cascode

**1) It increases the output impedance,**

**2) It alleviates the Miller effect on a voltage amplifier.**

$$A_{v1} = -g_{m1} R_{L1}' // R_{i2} = -g_{m1} R_{L1}' // \frac{r_{p2}}{b_2} \approx -g_{m1} \frac{r_{p2}}{b_2} \approx 1$$

$$g_{m1} = g_{m2}$$

$$C_{i,miller} = C_m (1 + g_m R_L') \approx C_m$$

$$W_{T1} = \frac{g_{m1}}{C_{p1} + C_{m1} (1 + g_{m1} R_{L1}')} \quad \rightarrow \quad W_{T1} = \frac{g_{m1}}{C_{p1} + C_{m1}}$$

$$W_{T2} = \frac{g_{m2}}{C_{m2}}$$

**3) Better isolation**

**4) It could magnify the signal not only voltage but also the power of signal as well.**

## o Example


This is an LNA RFIC design example, which is designed for group #1, Band #2 of UWB

DC power supply:  $V_{dd} = 1.2\text{ V}$ ,  
Current drain:  $I_{total} < 5\text{ mA}$ ,  
Operating frequency range:  $f = 3.696\text{ to }4.4224\text{ GHz}$ ,  
Gain:  $G > 12\text{ dB}$ ,  
Input return loss:  $S_{11} < -10\text{ dB}$ ,  
Output return loss:  $S_{22} < -10\text{ dB}$ ,  
Noise figure:  $NF < 2.5\text{ dB}$   
3rd order input intercept point:  $IIP3 > 5\text{ dBm}$ ,  
2nd order input intercept point:  $IIP2 > 35\text{ dBm}$ .


$$BW = \frac{\Delta f}{f} = \frac{4224 - 3696}{(4224 + 3696)/2} = \frac{528}{3960} = 13.3\%$$

$L = 130\text{ nm}$   
 $W = 1.25\text{ }\mu\text{m}$   
 $W_{total} = 10\text{ }\mu\text{m}$   
Fingers = 8  
Multiplier = 32  
 $M_{total} = 256$

\* Raw device testing

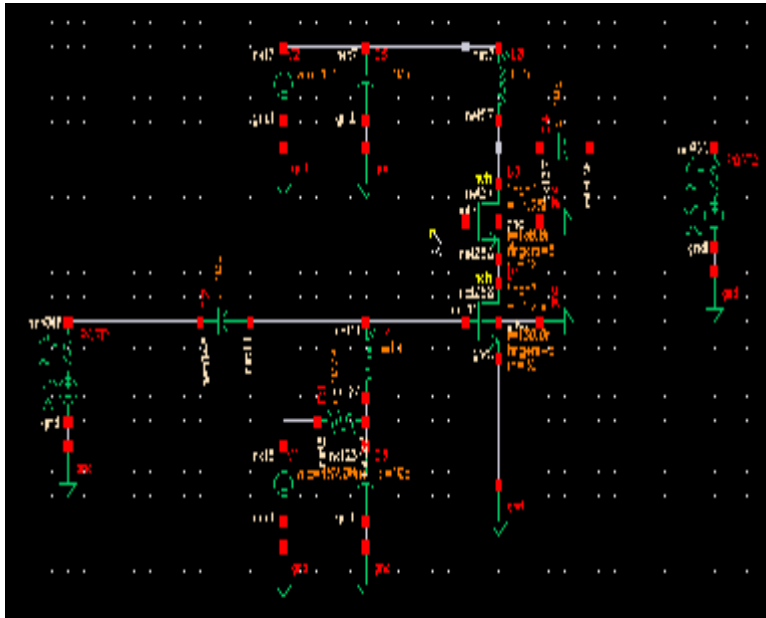

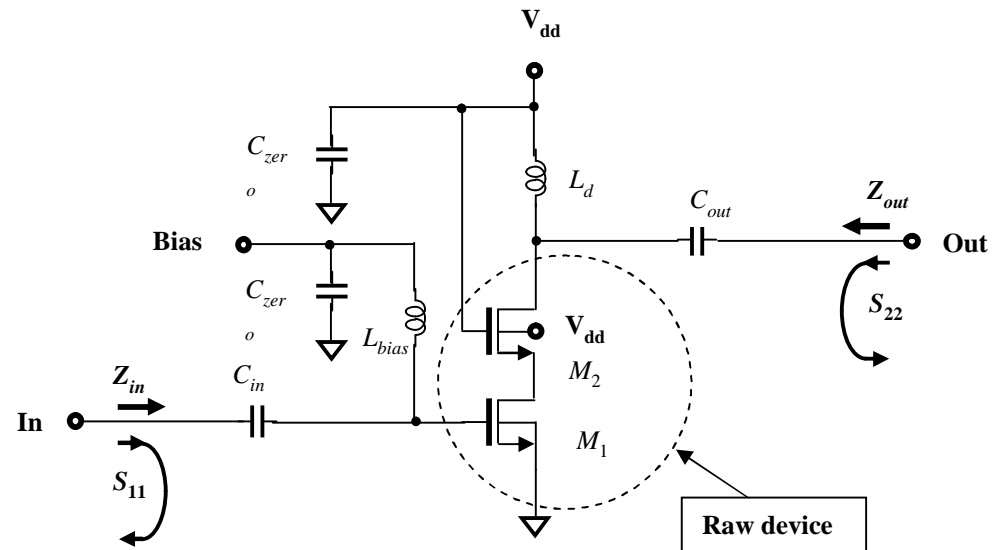
(a) Photo of setup for raw device testing taken from simulation screen



(b) Schematic of set-up for raw device testing re-drawn from the screen photo.

- o  $C_{in}$ ,  $C_{out}$ ,  $C_{zero}$ : "Zero" capacitor;
- o  $L_{bias}$ ,  $L_d$ : "Infinite" inductor.

Figure 11.33 Setup for raw device testing  $I_{dd} = 4.54 \text{ mA}$  (Bias = 0.482 V)

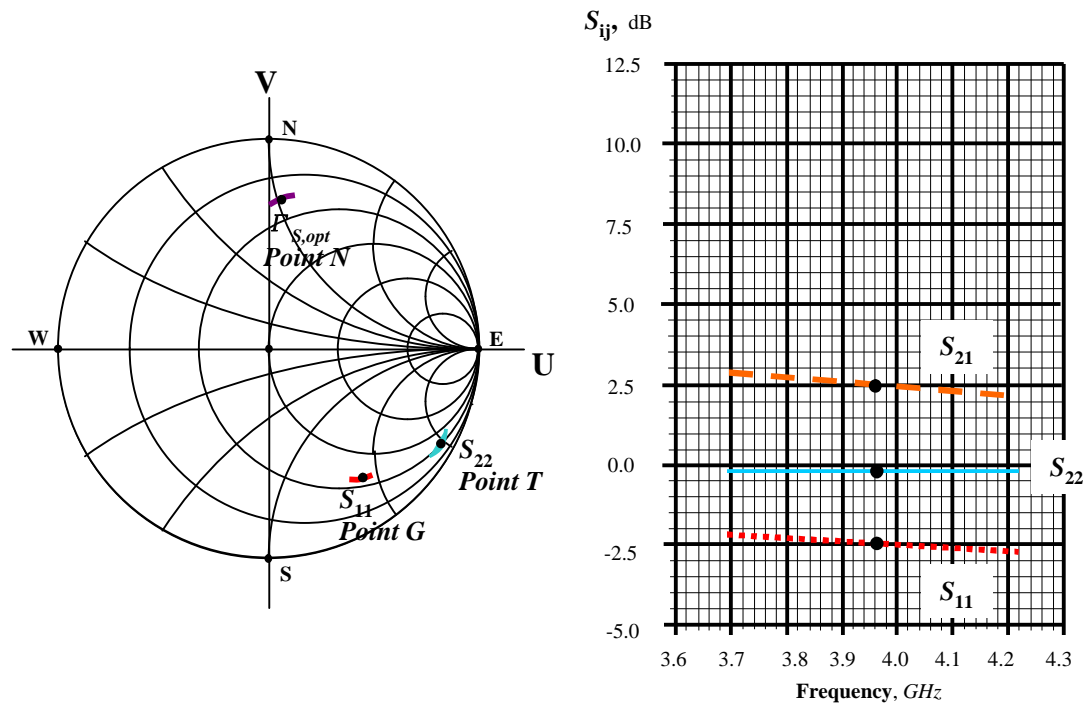


(a)  $S_{11}$  and  $S_{22}$  on Smith Chart

(b) Magnitude of  $S_{ij}$ , dB

Figure 11.34  $S$  parameters from raw device testing  
(The intermediate frequency  $f=3.96$  GHz is marked by a dot on each trace.)

f, GHz	3.696	3.960	4.224
$S_{21}$ , dB	2.45	2.50	2.58
$S_{11}$ , dB	-2.75	-2.50	-2.20
$S_{22}$ , dB	-0.19	-0.18	-0.17

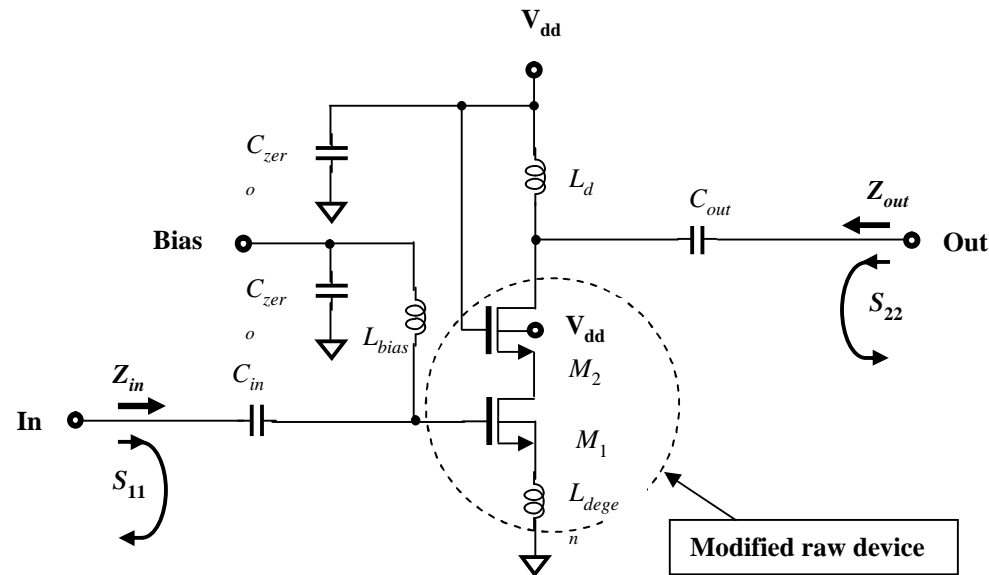

**Figure 11.35** Schematic of set-up for modified raw device testing

- $C_{in}$ ,  $C_{out}$ ,  $C_{zero}$  : “Zero” capacitor;
- $L_{bias}$ ,  $L_d$  : “Infinite” inductor.

$L_{\text{deg en}} = 0.45 \text{ nH}$ , which satisfies the condition of  $\Gamma_{S,\text{opt}} = S_{11}^*$   
 But  $m = 0.95 < 1$

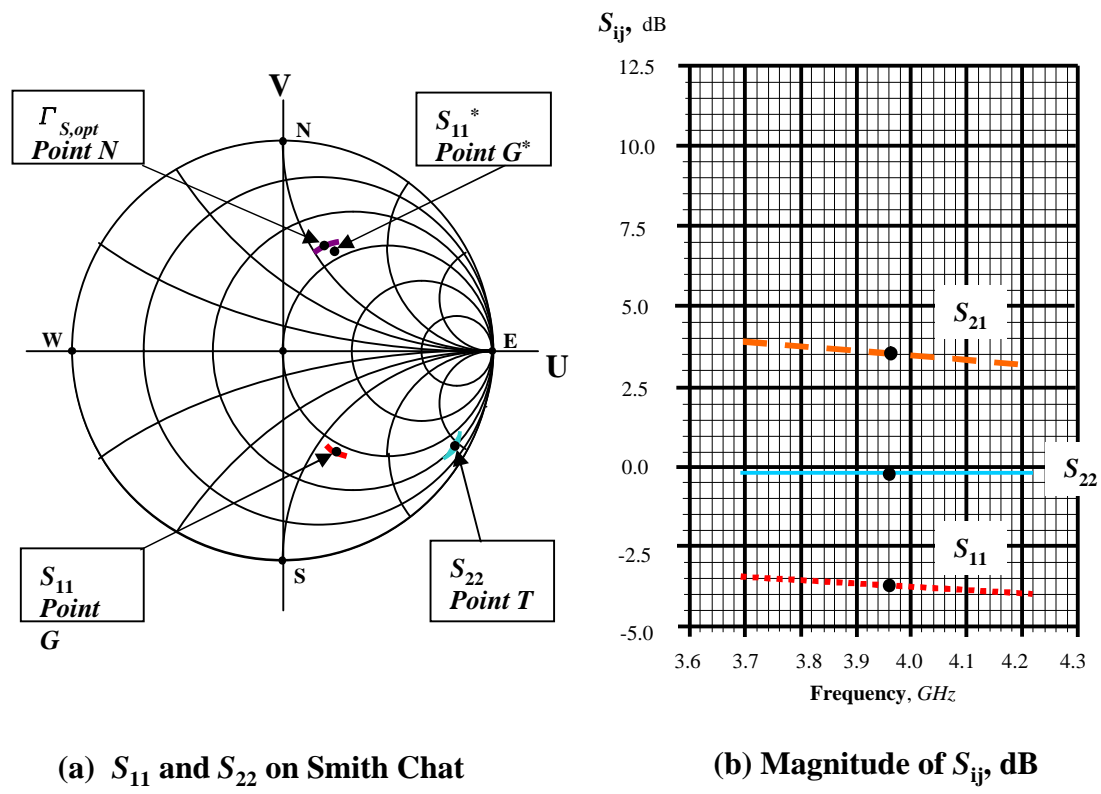


Figure 11.36  $S$  parameters from modified raw device testing  
 (The intermediate frequency  $f = 3.96 \text{ GHz}$  is marked by a dot on each trace.)

\* **Gain and Bandwidth**

- **The 1<sup>st</sup> try of the impedance matching work**

**In input impedance network:  $L_{S,in} = 4 \text{ nH}$ ,  $C_{S,in} = 10 \text{ pF}$ ,**

**In output impedance network:  $L_{P,out} = 10 \text{ nH}$ ,  $R_{P,out} = 50 \ \Omega$ ,  
 $C_{S,out} = 1 \text{ pF}$ .**

- The 1<sup>st</sup> try to implement impedance matching networks

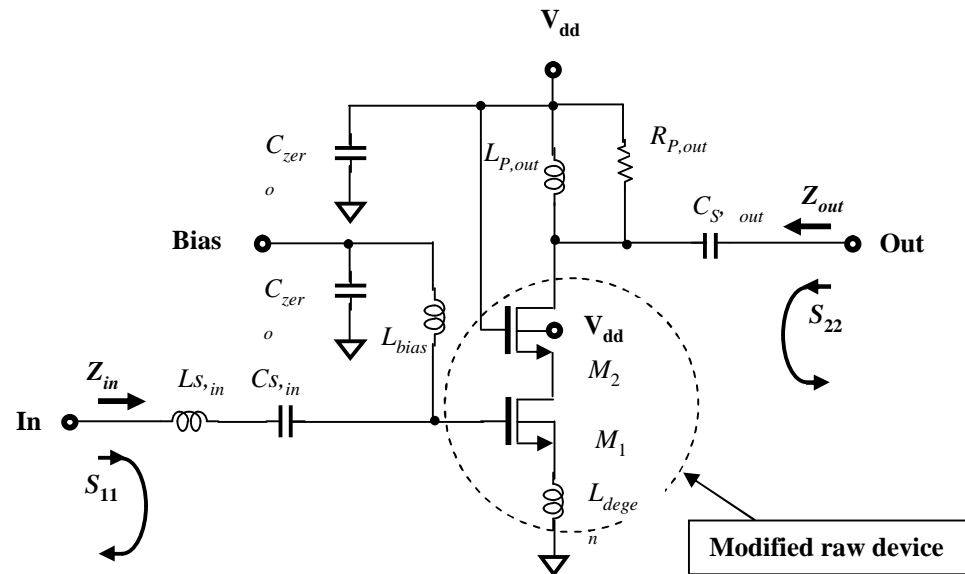


Figure 11. 37 Impedance matching by parts:


At input :  $L_{S,in} = 4 \text{ nH}$ ,  $C_{S,in} = 10 \text{ pF}$ .

At output :  $L_{P,out} = 10 \text{ nH}$ ,  $R_{P,out} = 500 \text{ } \Omega$ , and  $C_{S,out} = 1 \text{ pF}$



$\mu = 1.23 > 1$ , it is stable!

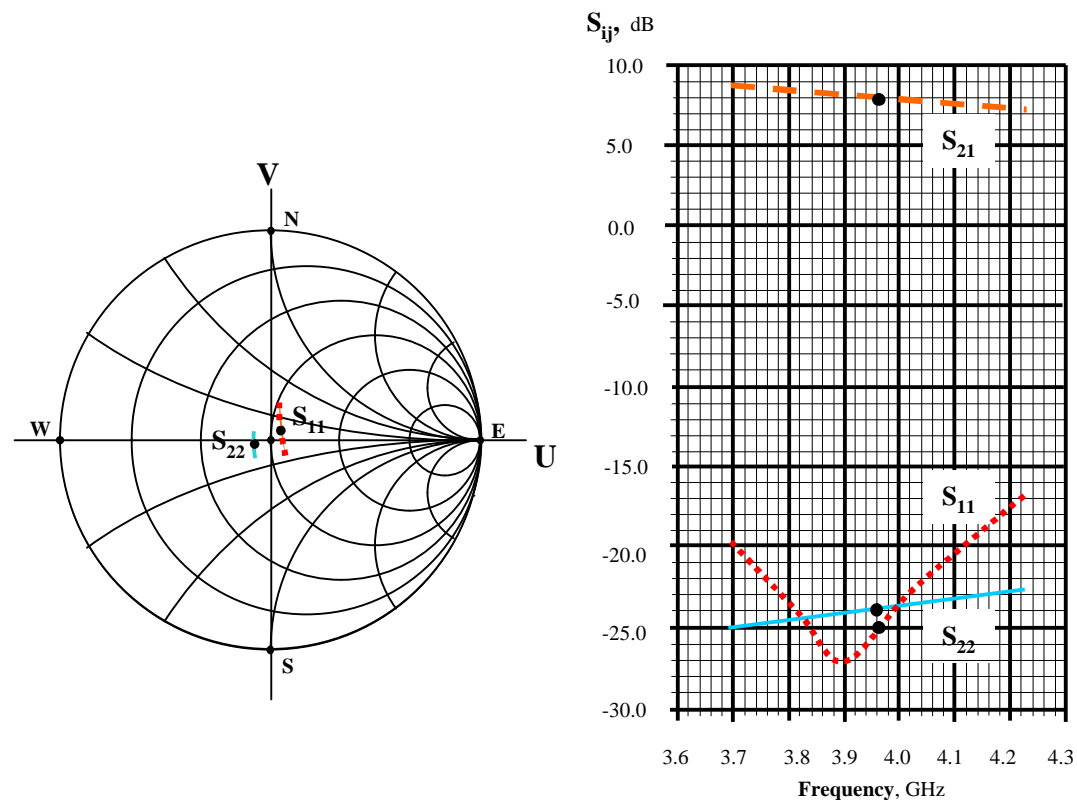However,  $G = 8.0 \text{ dB}$ , at  $f = 3.960 \text{ GHz}$ . The gain is too low!



(a)  $S_{11}$  and  $S_{22}$  on Smith Chart

(b) Magnitude of  $S_{ij}$ , dB

**Figure 11.38** S parameters after input and output impedances are matched by parts:  
(The intermediate frequency  $f = 3.96 \text{ GHz}$  is marked by a dot on each trace.)

At input:  $L_{S,in} = 4 \text{ nH}$ ,  $C_{S,in} = 10 \text{ pF}$ .

At output:  $L_{P,out} = 10 \text{ nH}$  and  $R_{P,out} = 500 \Omega$ ,  $C_{S,out} = 1 \text{ pF}$

- The 2<sup>nd</sup> try to re-build impedance matching networks


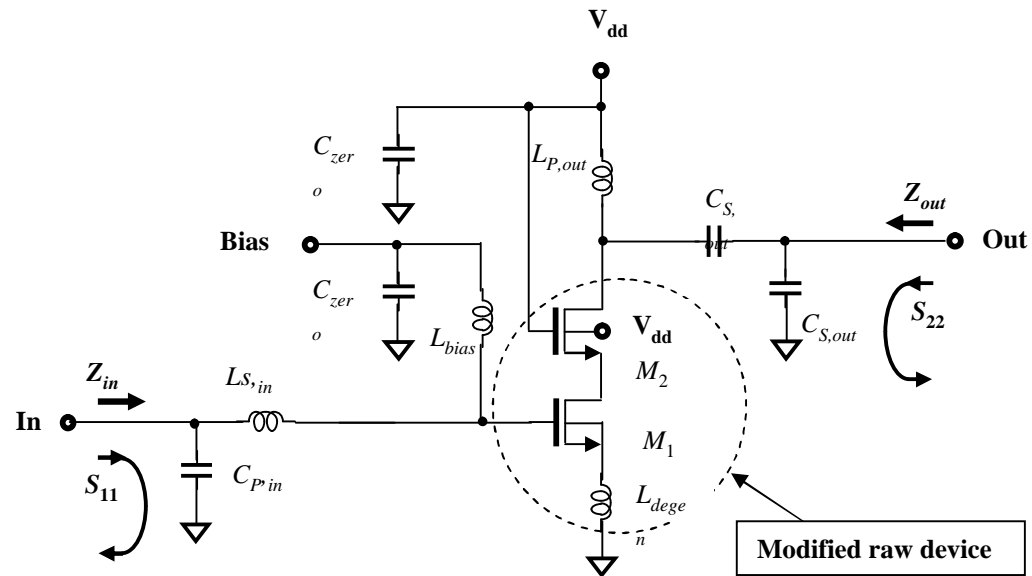


Figure 11.39 Modified impedance matching by parts:

At input :  $C_{P,in} = 0.3 \text{ pF}$ ,  $L_{S,in} = 3.3 \text{ nH}$ .

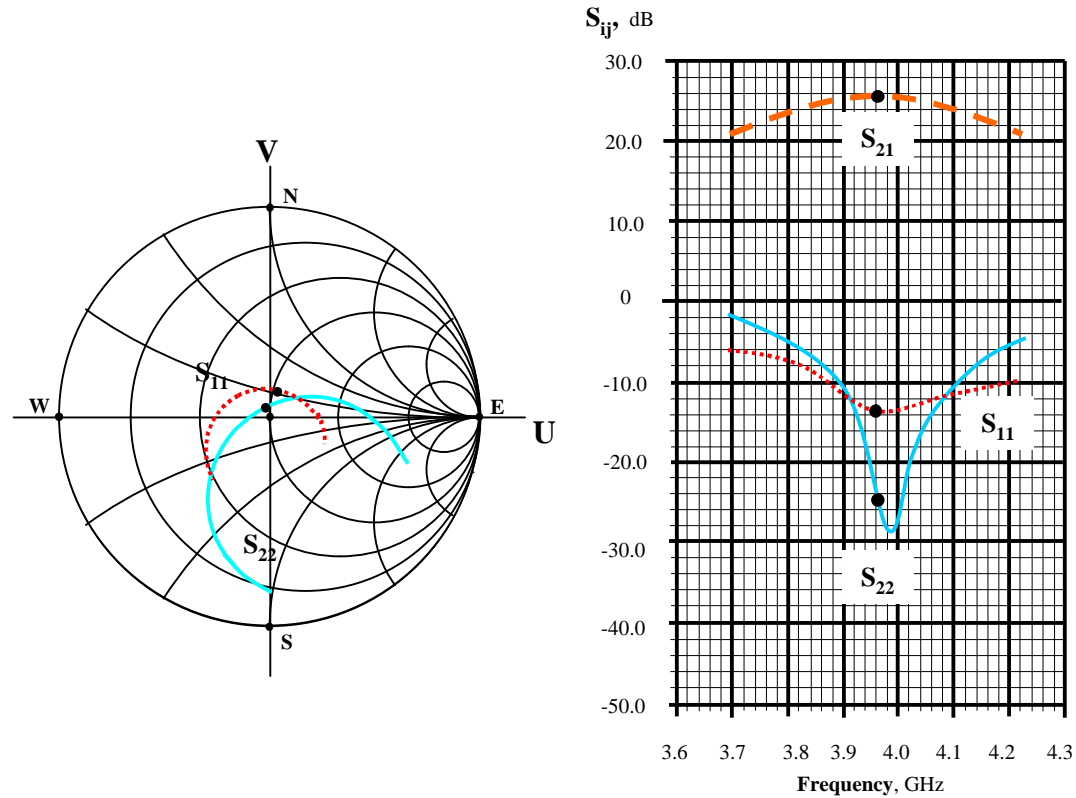At output :  $L_{P,out} = 5 \text{ nH}$ ,  $C_{S,out} = 0.13 \text{ pF}$ ,  
 $C_{P,out} = 0.3 \text{ pF}$



(a)  $S_{11}$  and  $S_{22}$  on Smith Chart

(b) Magnitude of  $S_{ij}$ , dB

**Figure 11.40** S parameters after input and output impedances are matched by parts:  
 (The intermediate frequency  $f = 3.96$  GHz is marked by a dot on each trace.)


**At input :**  $C_{P,in} = 0.3$  pF,  $L_{S,in} = 3.3$  nH.

**At output :**  $L_{P,out} = 5$  nH,  $C_{S,out} = 0.13$  pF, and  $C_{P,out} = 0.3$  pF


<b>f, GHz</b>	<b>3.696</b>	<b>3.960</b>	<b>4.224</b>
<b>S<sub>21</sub>, dB</b>	<b>20.8</b>	<b>25.5</b>	<b>25.5</b>
<b>S<sub>11</sub>, dB</b>	<b>-13.8</b>	<b>-13.6</b>	<b>-6.2</b>
<b>S<sub>22</sub>, dB</b>	<b>-28.8</b>	<b>-25.0</b>	<b>-1.8</b>

**In the entire frequency range, the gain,  $S_{21} > 20.8$  dB, is satisfied!**  
**Unfortunately, the bandwidth becomes narrow and is unable to cover the desired frequency range:  $3.696 \text{ GHz} < f < 4.224 \text{ GHz}$ !**


- The 3<sup>rd</sup> try to modify impedance matching networks

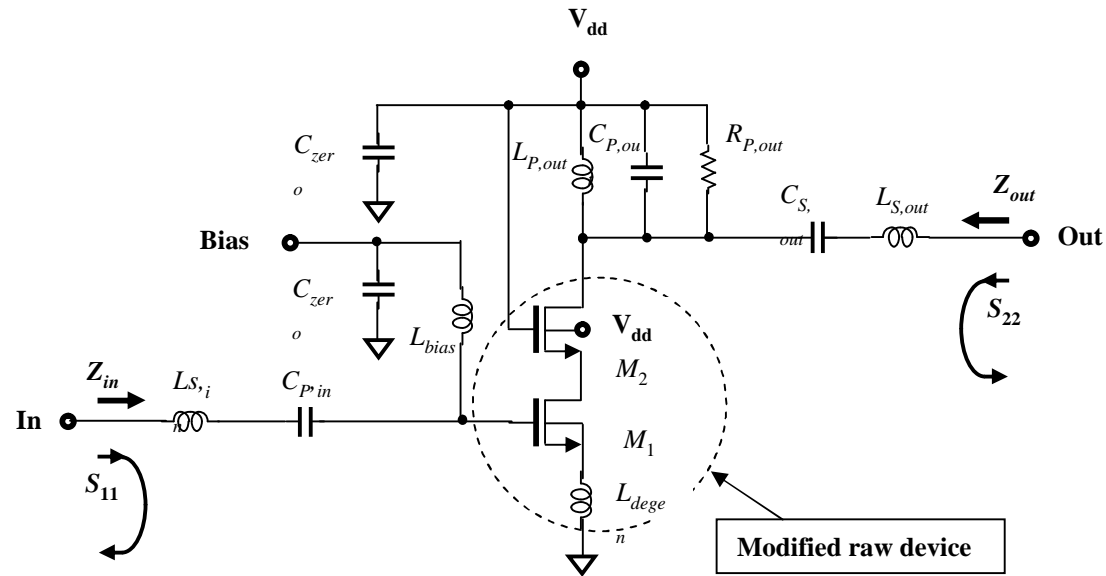

**Figure 4.41 Re-Modified impedance matching by parts:**  
**At input :**  $L_{S,in} = 3.8 \text{ nH}$ ,  $C_{S,in} = 5 \text{ pF}$ ,  
**At output :**  $R_{P,out} = 200 \Omega$ ,  $L_{P,out} = 2 \text{ nH}$ ,  $C_{P,out} = 0.97 \text{ pF}$ ,  
 $C_{S,out} = 10 \text{ pF}$ ,  $L_{S,out} = 3.3 \text{ nH}$

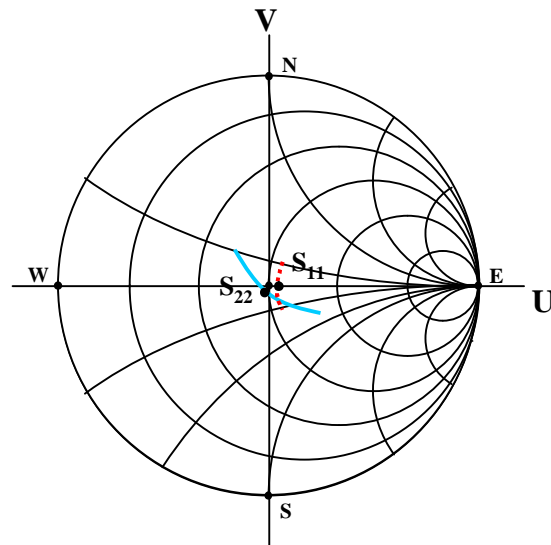

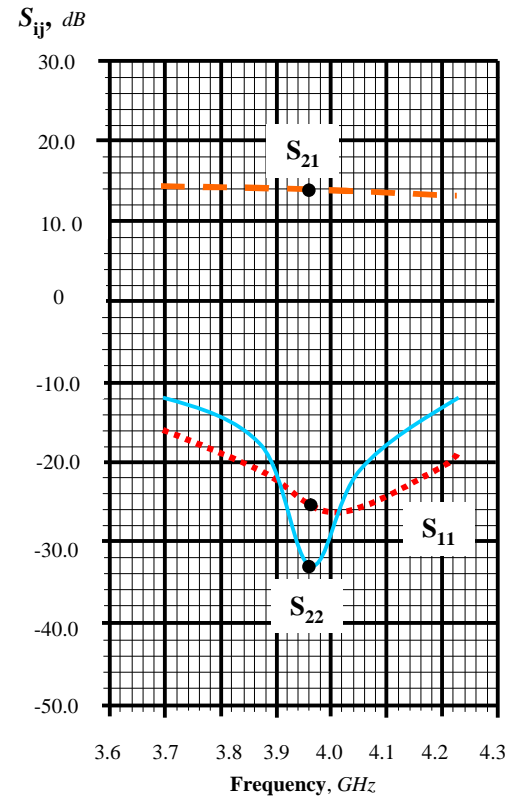(a)  $S_{11}$  and  $S_{22}$  on Smith Chart



(b) Magnitude of  $S_{ij}$ , dB

**Figure 4.42** S parameters after input and output impedances are matched by parts:  
 (The intermediate frequency  $f=3.96$  GHz is marked by a dot on each trace.)

**At input :**  $L_{S,in} = 3.8$  nH,  $C_{S,in} = 5$  pF,


**At output :**  $R_{P,out} = 200$   $\Omega$ ,  $L_{P,out} = 2$  nH,  $C_{P,out} = 0.97$  pF,

$C_{S,out} = 10$  pF,  $L_{S,out} = 3.3$  nH.


<b>f, GHz</b>	<b>3.696</b>	<b>3.960</b>	<b>4.224</b>
<b>S<sub>21</sub>, dB</b>	<b>13.0</b>	<b>14.0</b>	<b>14.3</b>
<b>S<sub>11</sub>, dB</b>	<b>-26.2</b>	<b>-25.5</b>	<b>-15.9</b>
<b>S<sub>22</sub>, dB</b>	<b>-33.2</b>	<b>-33.1</b>	<b>-11.9</b>

**In the entire frequency range, the gain,  $S_{21} > 13.0$  dB, is satisfied!  
And the bandwidth becomes wide and is able to cover the  
desired bandwidth:  $3.696 \text{ GHz} < f < 4.224 \text{ GHz}$ !**

\* Noise

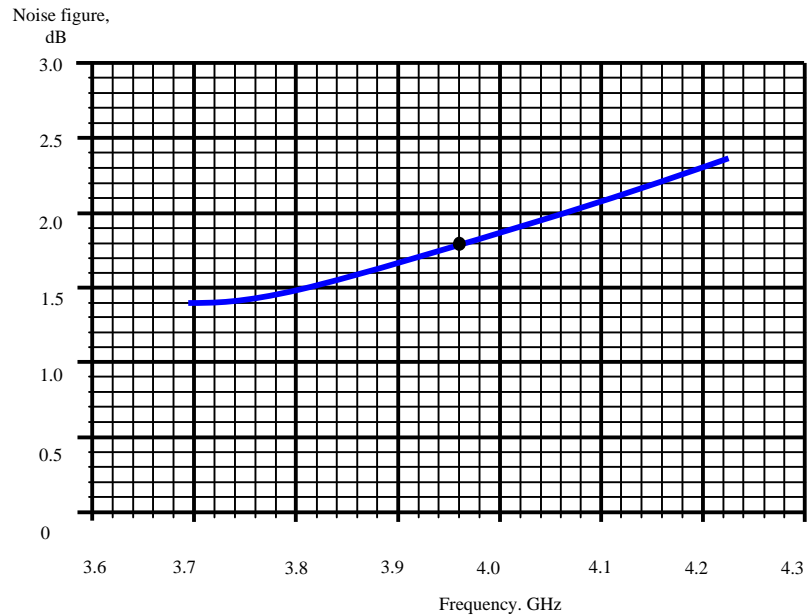

**Figure 11.43** Noise Figure from 3.696 to 4.224 GHz.  
 $NF = 1.8 \text{ dB}$  when  $f = 3.960 \text{ GHz}$

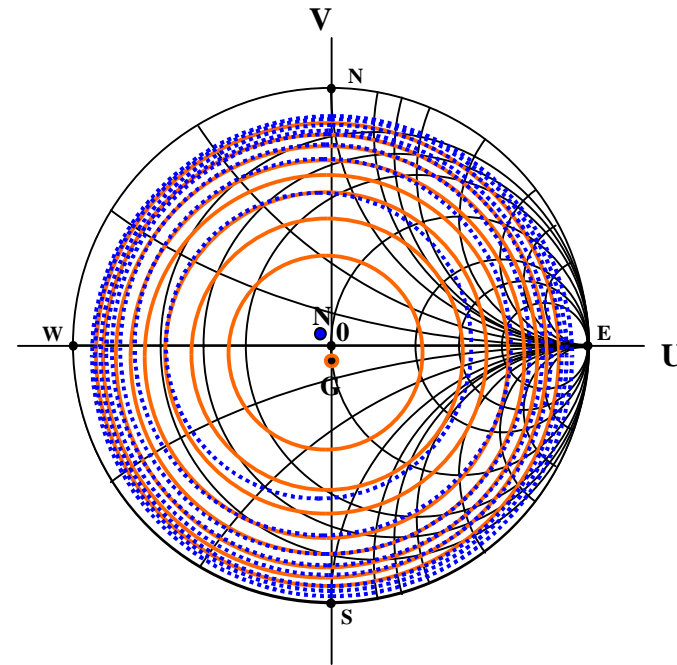

**Figure 4.44** Constant gain circles and constant noise figure circles when  $f = 3.96 \text{ GHz}$

- o Gain circles:  $G_{\max} = 14 \text{ dB}$  at point G, step = 1.0 dB,
- o Noise figure circles:  $NF_{\min} = 1.8 \text{ dB}$  at point N, step = 0.5 dB,



\* **Non-Linearity**

• **Output Spectrum**

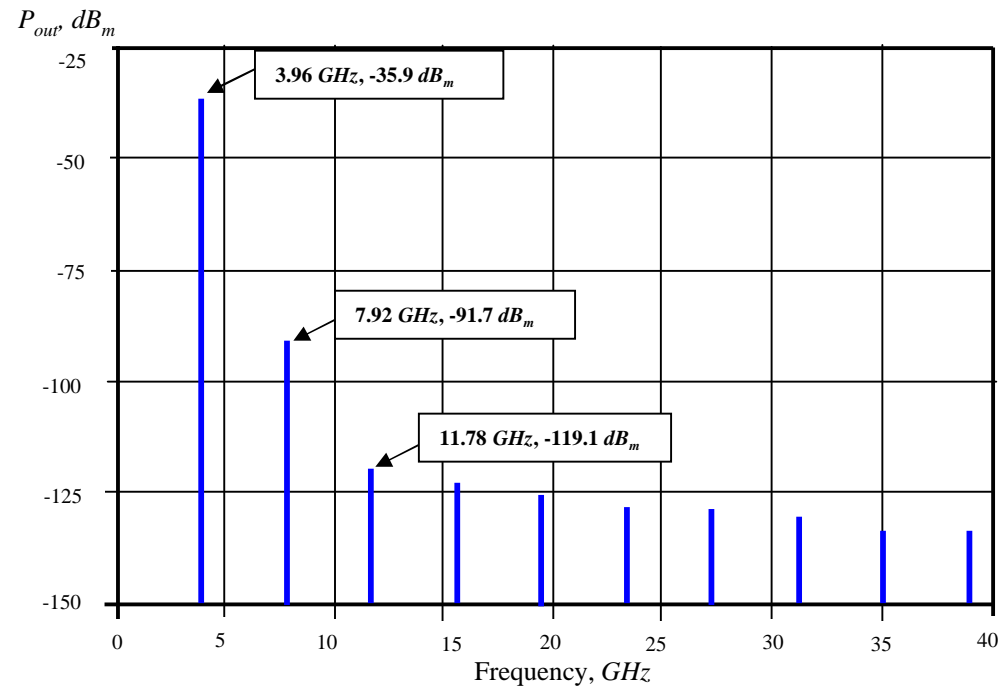


Figure 11.45 Spectrum at LNA output ,  $f_o = 3.96\text{GHz}$ ,  $P_{in} = -50 \text{ dB}_m$

- 1 dB Compression Point


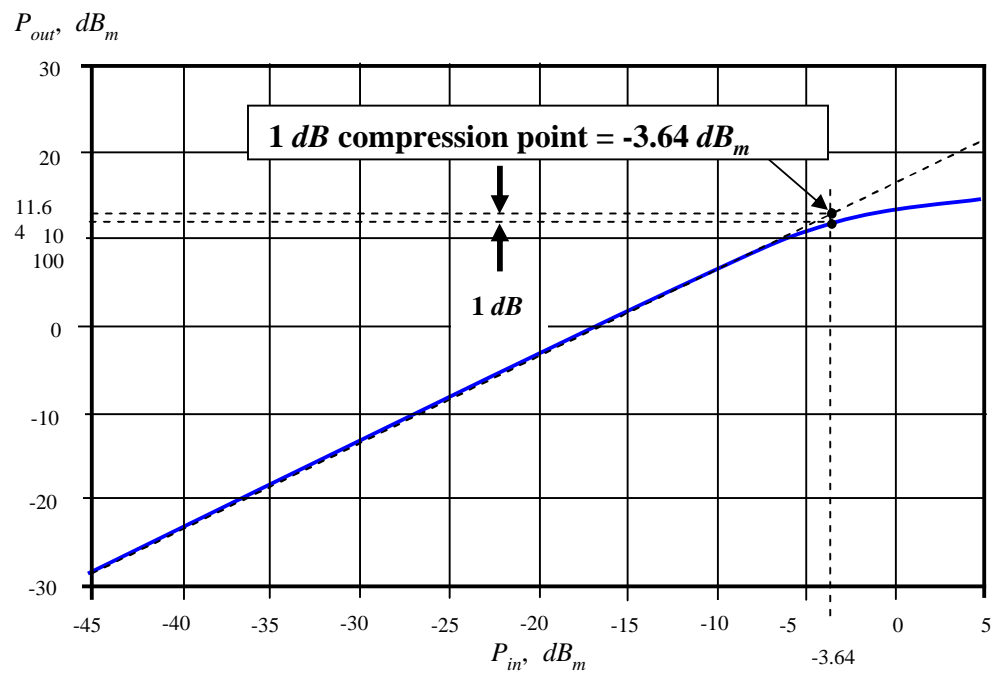



Figure 11.46 1dB compression point when  $f_o = 3.96$  GHz

- **3<sup>rd</sup> order Intercept Point**

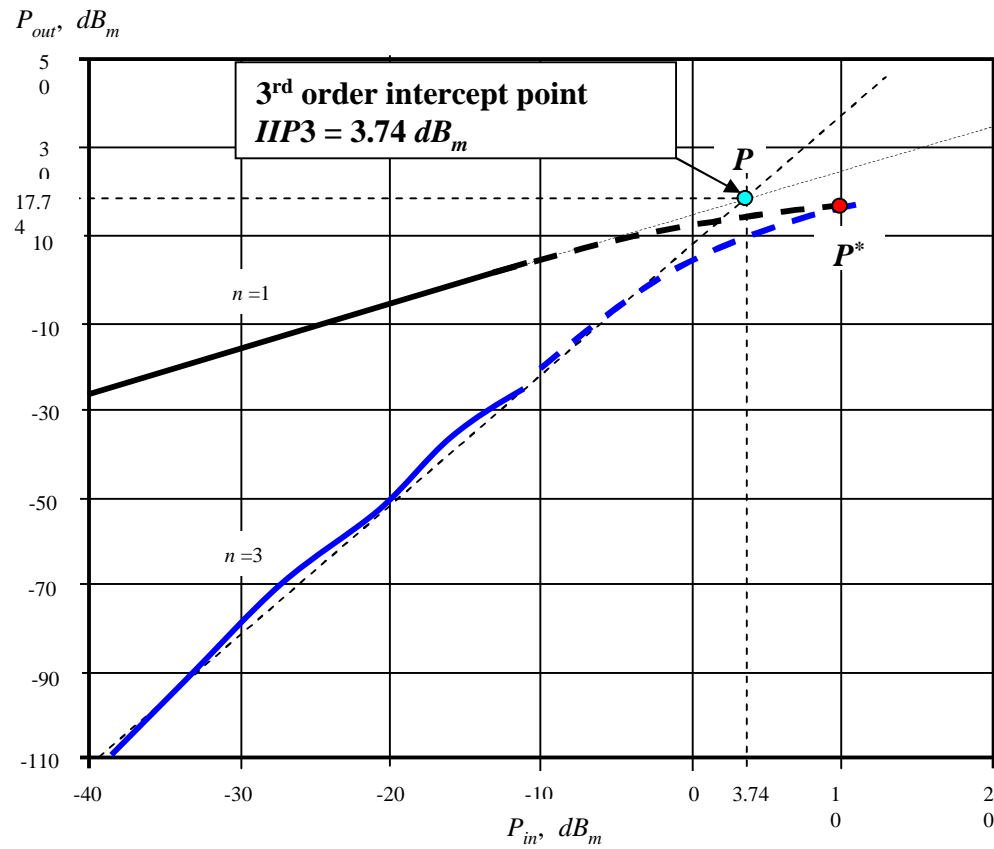

**Figure 11.47** 3<sup>rd</sup> order input intercept point when  $f_o = 3.96 \text{ GHz}$

- **2<sup>nd</sup> order Intercept Point**

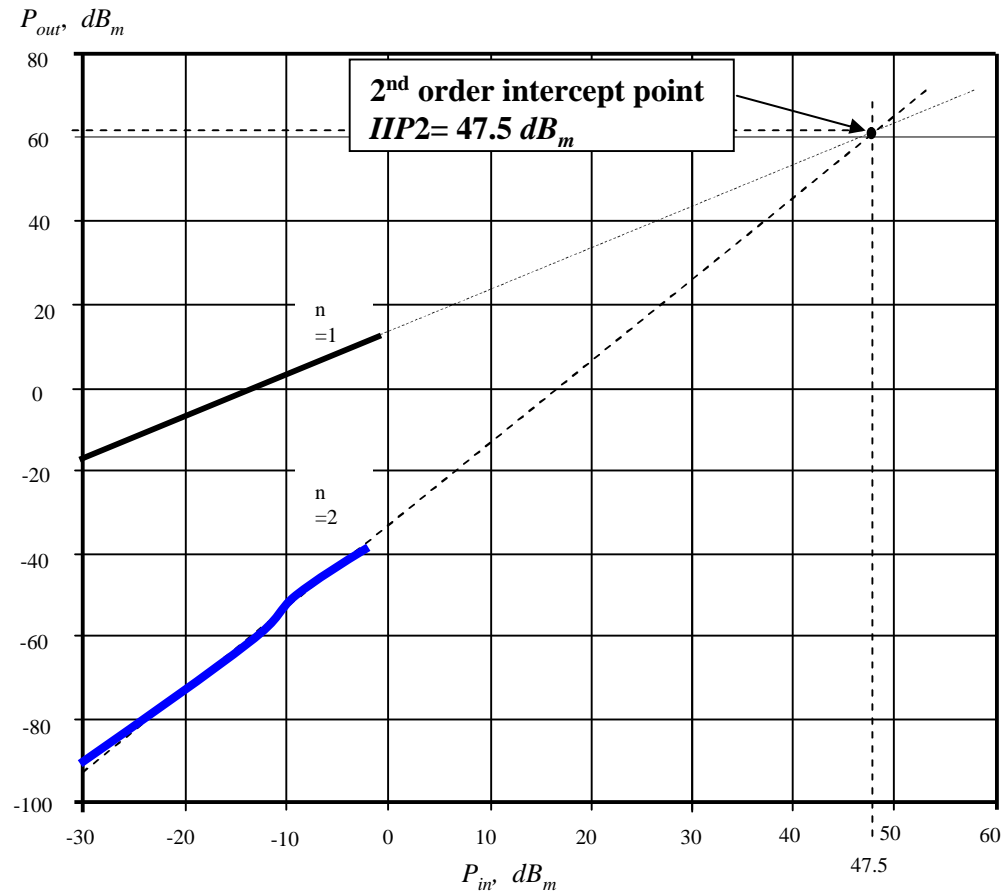

**Figure 4.48** 2<sup>nd</sup> order input intercept point when  $f_o = 3.96$  GHz

## o LNA with AGC (Automatic Gain Control)

### \* Variation of Field Strength around Antenna

- Q: What does the 90 dB variation of the field strength around the antenna mean?
- A: It means that the field strength is varied so many times, that is,

$$2^{\frac{90}{3}} = 1,073,741,824 \quad !$$

\* Implication of AGC

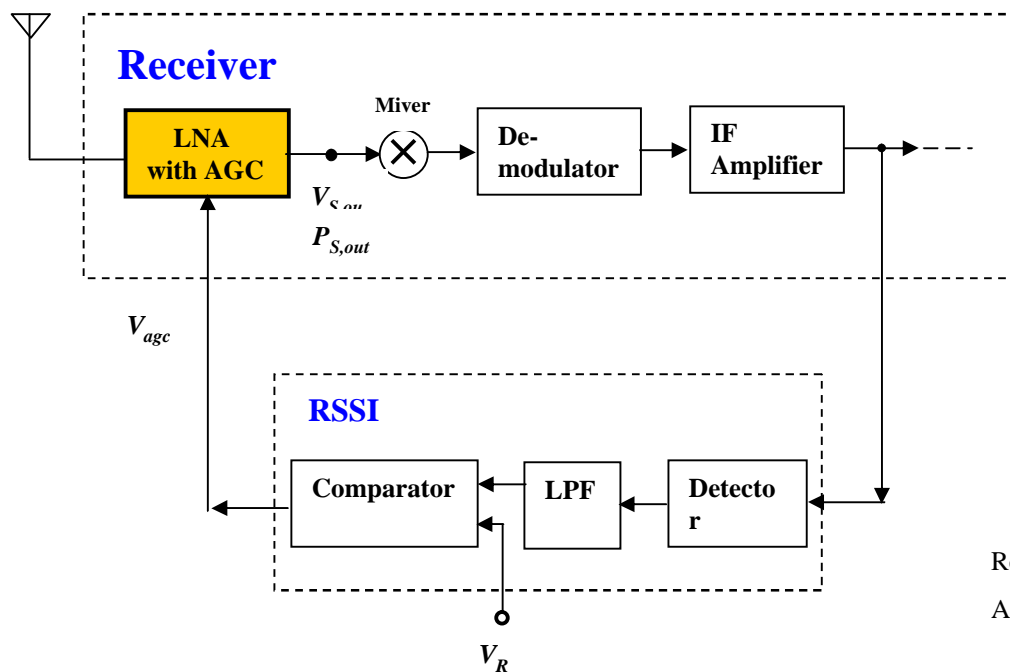


Figure 11.49 An AGC control loop in the receiver of a communication system

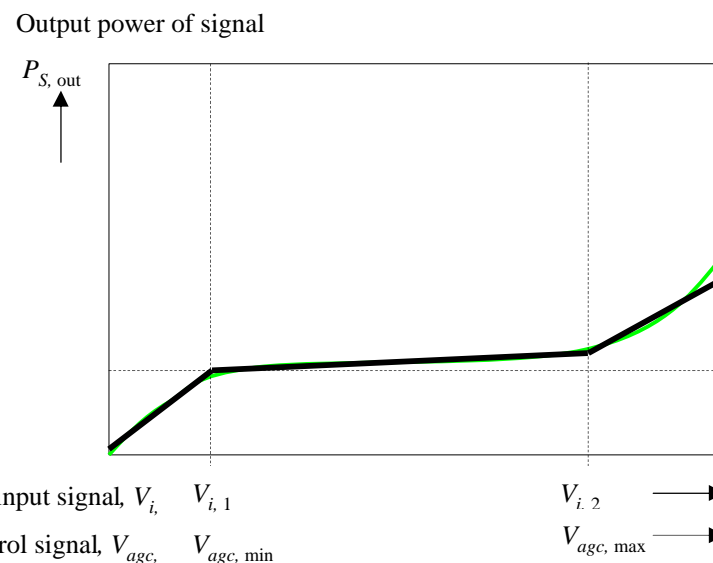


Figure 11.50 Expected Characteristics of AGC control  
 — Ideal  
 — Actual performance

\* **Traditional LNA with AGC**


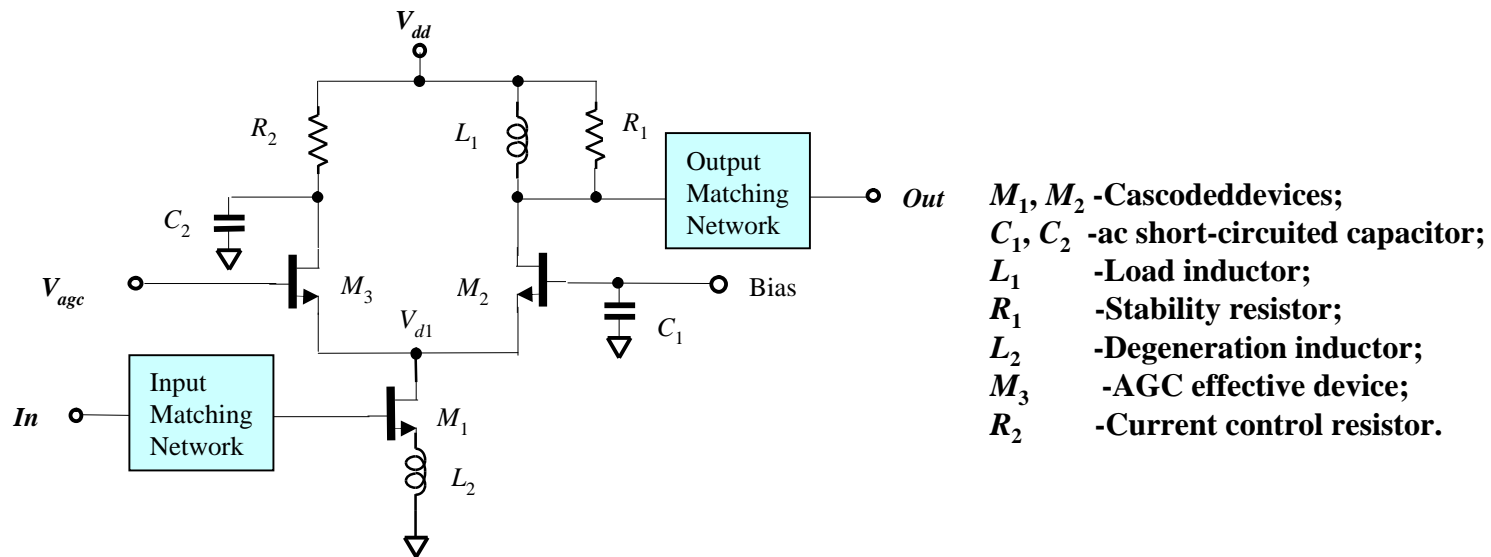


Figure 11.51 Traditional LNA with AGC

\* **Increase of AGC Dynamic Range**

- **Diode Clamping**

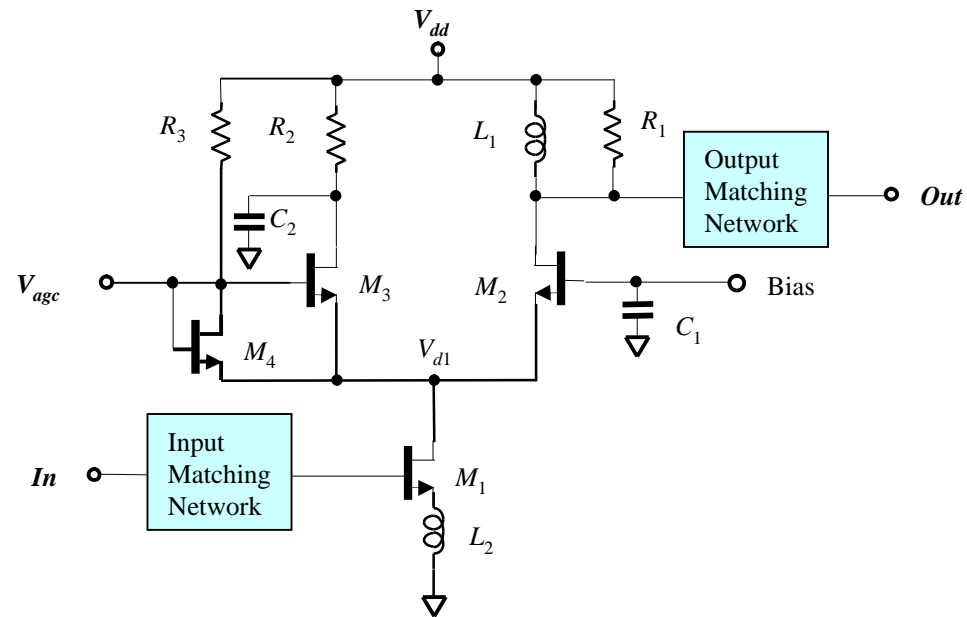

**Figure 11.52** LNA with large dynamic range of AGC



- **To avoid RSSI operated as a current sink or source**

## **Addition of $R_3$ and $M_4$**

- Selection of big device  $M_3$

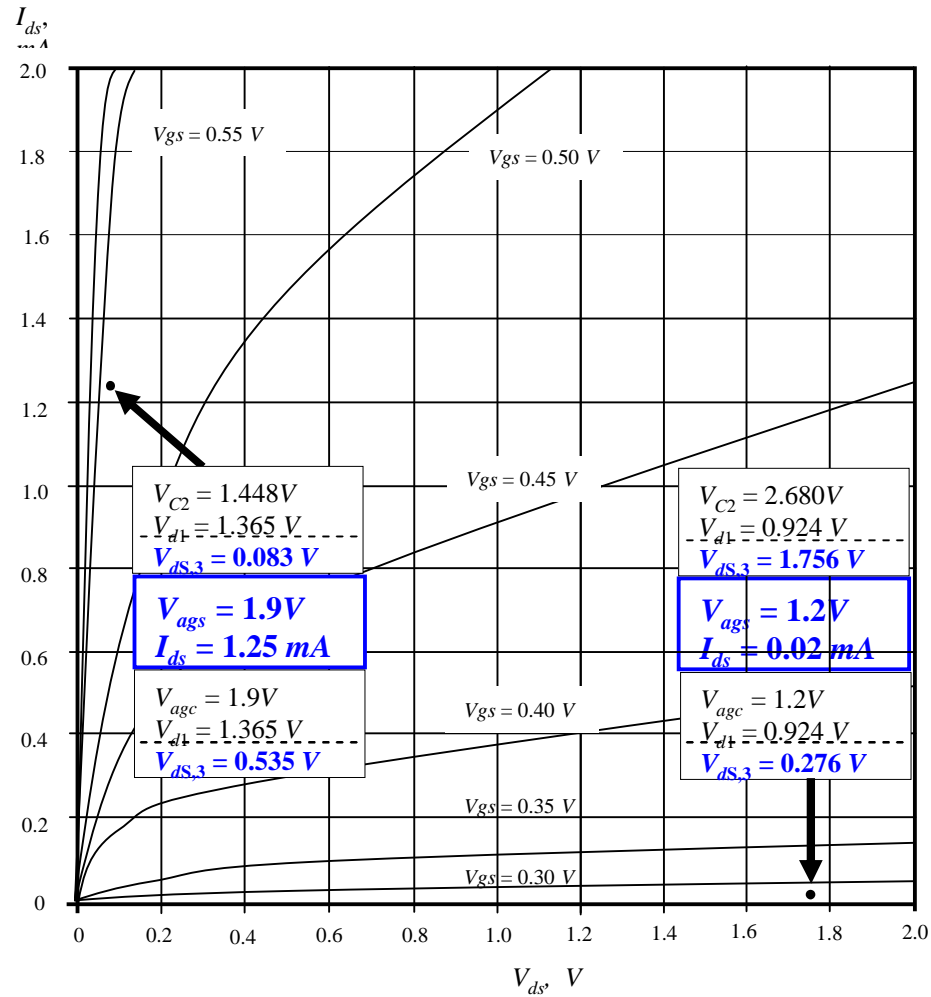


Figure 11.53 DC characteristics of transistor  $M_3$

**Table 11.2 Part list of LNA with AGC**

<b><u>Part</u></b>	<b><u>Value</u></b>	
$M_1$	Fingers = 8	$W_{total} = 128 \mu m$
$M_2$	Fingers = 16	$W_{total} = 256 \mu m$
$M_3$	Fingers = 100	$W_{total} = 1600 \mu m$
$M_4$	Fingers = 16	$W_{total} = 1256 \mu m$
$R_1$	700 $\Omega$	
$R_2$	1 k $\Omega$	
$R_3$	10 k $\Omega$	
$C_1$	20 pF	
$C_2$	40 pF	
$L_1$	50 nH	
$L_2$	30 nH	

**Table 11.3 Goals, simulation, and performance of a LNA with AGC**

	<u>Goal</u>		<u>Simulation</u>	<u>Performance</u>
DC power supply, $V$	3.0	3.0	3.0 $V$	
Frequency, $f$	460 to 470		460 to 470	460 to 470 $MHz$
RSSI Control voltage, $V_{agc}$	1.2 to 1.9		1.2 to 1.9	1.2 to 1.9 $V$
AGC dynamic range, $DR_{agc}$	0.00 to -40		0.00 to -43.7	0.0 to -42 $dB$
Current drain, $I_{ds}$	2.0 to *		1.87 to 1.48	2.0 to 1.4 $mA$
Gain, $G$		12.0 to -28	12.6 to -31.1	15.0 to -27.0 $dB$
Noise Figure, $NF$	2.0 to *		1.26 to 29.4	2.7 to * $dB$
3rd order intercept point, $IIP3$	-15.0 to *		-10.2 to -7.5	-10.5 to -8.0 $dBm$
Input Return Loss, $S_{11}$	* to *		-15.3 to -10.4	* to * $dB$
Output Return Loss, $S_{22}$	* to *		-23.2 to -11.7	* to * $dB$

## Discussion

- o Key points to approach  $G_{\max}$  and  $NF_{\min}$ .
- o Advantages and disadvantages of CS-CG or CE-CB cascodeLNA
- o Why AGC?
- o Why differential?

## 射频和天线设计培训课程推荐

易迪拓培训([www.edatop.com](http://www.edatop.com))由数名来自于研发第一线的资深工程师发起成立,致力并专注于微波、射频、天线设计研发人才的培养;我们于 2006 年整合合并微波 EDA 网([www.mweda.com](http://www.mweda.com)),现已发展成为国内最大的微波射频和天线设计人才培养基地,成功推出多套微波射频以及天线设计经典培训课程和 ADS、HFSS 等专业软件使用培训课程,广受客户好评;并先后与人民邮电出版社、电子工业出版社合作出版了多本专业图书,帮助数万名工程师提升了专业技术能力。客户遍布中兴通讯、研通高频、埃威航电、国人通信等多家国内知名公司,以及台湾工业技术研究院、永业科技、全一电子等多家台湾地区企业。

易迪拓培训课程列表: <http://www.edatop.com/peixun/rfe/129.html>



### 射频工程师养成培训课程套装

该套装精选了射频专业基础培训课程、射频仿真设计培训课程和射频电路测量培训课程三个类别共 30 门视频培训课程和 3 本图书教材;旨在引领学员全面学习一个射频工程师需要熟悉、理解和掌握的专业知识和研发设计能力。通过套装的学习,能够让学员完全达到和胜任一个合格的射频工程师的要求...

课程网址: <http://www.edatop.com/peixun/rfe/110.html>

### ADS 学习培训课程套装

该套装是迄今国内最全面、最权威的 ADS 培训教程,共包含 10 门 ADS 学习培训课程。课程是由具有多年 ADS 使用经验的微波射频与通信系统设计领域资深专家讲解,并多结合设计实例,由浅入深、详细而又全面地讲解了 ADS 在微波射频电路设计、通信系统设计和电磁仿真设计方面的内容。能让您在最短的时间内学会使用 ADS,迅速提升个人技术能力,把 ADS 真正应用到实际研发工作中去,成为 ADS 设计专家...



课程网址: <http://www.edatop.com/peixun/ads/13.html>



### HFSS 学习培训课程套装

该套课程套装包含了本站全部 HFSS 培训课程,是迄今国内最全面、最专业的 HFSS 培训教程套装,可以帮助您从零开始,全面深入学习 HFSS 的各项功能和在多个方面的工程应用。购买套装,更可超值赠送 3 个月免费学习答疑,随时解答您学习过程中遇到的棘手问题,让您的 HFSS 学习更加轻松顺畅...

课程网址: <http://www.edatop.com/peixun/hfss/11.html>

## CST 学习培训课程套装

该培训套装由易迪拓培训联合微波 EDA 网共同推出,是最全面、系统、专业的 CST 微波工作室培训课程套装,所有课程都由经验丰富的专家授课,视频教学,可以帮助您从零开始,全面系统地学习 CST 微波工作的各项功能及其在微波射频、天线设计等领域的设计应用。且购买该套装,还可超值赠送 3 个月免费学习答疑...

课程网址: <http://www.edatop.com/peixun/cst/24.html>



## HFSS 天线设计培训课程套装

套装包含 6 门视频课程和 1 本图书,课程从基础讲起,内容由浅入深,理论介绍和实际操作讲解相结合,全面系统的讲解了 HFSS 天线设计的全过程。是国内最全面、最专业的 HFSS 天线设计课程,可以帮助您快速学习掌握如何使用 HFSS 设计天线,让天线设计不再难...

课程网址: <http://www.edatop.com/peixun/hfss/122.html>

## 13.56MHz NFC/RFID 线圈天线设计培训课程套装

套装包含 4 门视频培训课程,培训将 13.56MHz 线圈天线设计原理和仿真设计实践相结合,全面系统地讲解了 13.56MHz 线圈天线的工作原理、设计方法、设计考量以及使用 HFSS 和 CST 仿真分析线圈天线的具体操作,同时还介绍了 13.56MHz 线圈天线匹配电路的设计和调试。通过该套课程的学习,可以帮助您快速学习掌握 13.56MHz 线圈天线及其匹配电路的原理、设计和调试...

详情浏览: <http://www.edatop.com/peixun/antenna/116.html>



### 我们的课程优势:

- ※ 成立于 2004 年,10 多年丰富的行业经验,
- ※ 一直致力并专注于微波射频和天线设计工程师的培养,更了解该行业对人才的要求
- ※ 经验丰富的一线资深工程师讲授,结合实际工程案例,直观、实用、易学

### 联系我们:

- ※ 易迪拓培训官网: <http://www.edatop.com>
- ※ 微波 EDA 网: <http://www.mweda.com>
- ※ 官方淘宝店: <http://shop36920890.taobao.com>

专注于微波、射频、天线设计人才的培养

官方网址: <http://www.edatop.com>

淘宝网: <http://shop36920890.taobao.com>