

# Lecture #4 : Impedance Measurement

1. Introduction
  - o Voltage Measurement at One Point
  - o Measurement by S Parameter is Better than by Others
2. Impedance measured directly by Network Analyzer
  - o Theoretical Background of Impedance Measurement
  - o Smith Chart
  - o Calibration of Network Analyzer
  - o Relationship between the Impedance in Series and in Parallel
3. Impedance measured alternatively by network analyzer
  - o Accuracy of Smith Chart
  - o Low and high impedance measurement
4. Impedance measured by means of circulator
5. Impedance matching and matching of a mixer



# 1. Introduction

## o Voltage Measurement at One Point

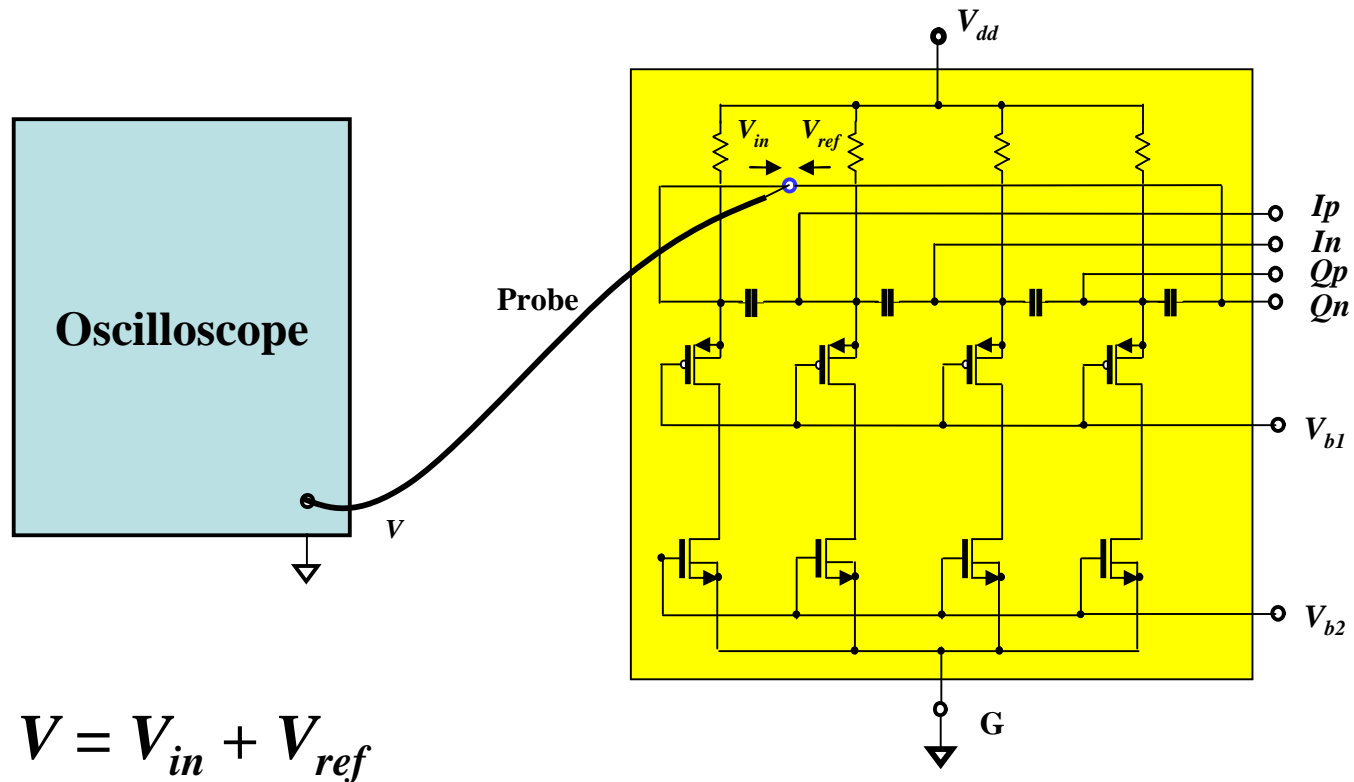


Figure 4.1 Voltage measured at one point is a resultant entity of incident and reflected voltage

o Measurement by S parameters is better than by others

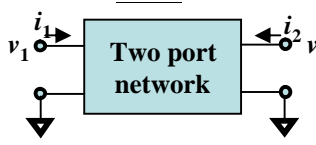
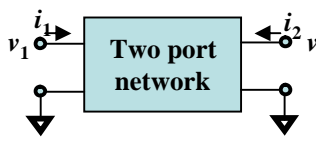
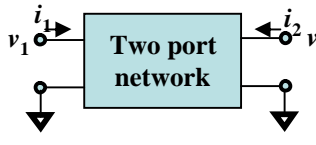
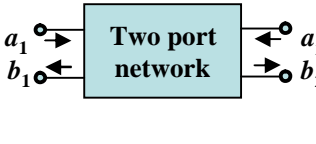
Parameters	Matrix	Coefficients	Block
$\underline{Z}$	$v_1 = z_{11}i_1 + z_{12}i_2$ $v_2 = z_{21}i_1 + z_{22}i_2$	$z_{11} = v_1 / i_1 / i_2=0$ ...	
$\underline{Y}$	$i_1 = y_{11}v_1 + y_{12}v_2$ $i_2 = y_{21}v_1 + y_{22}v_2$	$y_{11} = i_1 / v_1 / v_2=0$ ...	
$\underline{h}$	$v_1 = h_{11}i_1 + h_{12}v_2$ $i_2 = h_{21}i_1 + h_{22}v_2$	$h_{11} = v_1 / i_1 / v_2=0$ $h_{12} = v_1 / v_2 / i_1=0$ ...	
S	$b_1 = s_{11}a_1 + s_{12}a_2$ $b_2 = s_{21}a_1 + s_{22}a_2$	$s_{11} = b_1 / a_1 / a_2=0$ ...	

Figure 4.2 The various parameters to characterize a two port network.

## 2. Impedance Measured Directly by Network Analyzer

o Theoretical background of impedance measurement by parameters,  $S_{11}$ ,  $S_{22}$

$$\Gamma_{in} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$

$$\Gamma_{out} = S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S}$$

When  $\Gamma_S = \Gamma_L = 0$ ,

Or,  $S_{12} = 0$ ,

Or,  $S_{21} = 0$ ,

$$\Gamma_{in} = S_{11}$$

$$\Gamma_{out} = S_{22}$$

$$Z_{in} = \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = \frac{1 + S_{11}}{1 - S_{11}}$$

$$Z_{out} = \frac{1 + \Gamma_{out}}{1 - \Gamma_{out}} = \frac{1 + S_{22}}{1 - S_{22}}$$

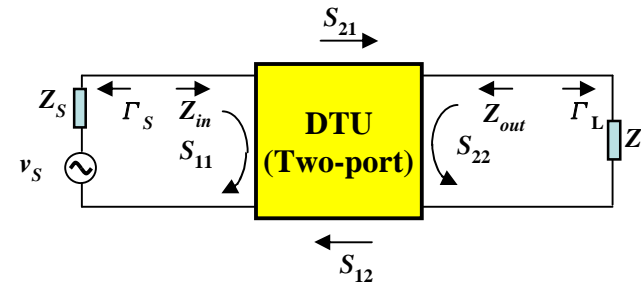


Figure 4.3 Relationship between  $S_{ij}$  and  $\Gamma_k$

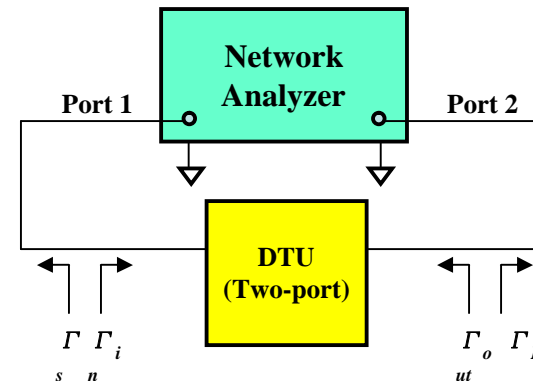


Figure 4.4 Impedance measured by network analyzer



## o Smith Chart

### \* Impedance coordination

$$\Gamma = U + jV$$

$$\Gamma = \frac{Z - Z_o}{Z + Z_o} = \frac{z - 1}{z + 1}$$

$$z = \frac{Z}{Z_o} = r + jx$$

$$z = \frac{1 + \Gamma}{1 - \Gamma}$$

$$\Gamma = U + jV = \frac{(r - 1) + jx}{(r + 1) + jx}$$

$$U = \frac{r^2 - 1 + x^2}{(r + 1)^2 + x^2}$$

$$V = \frac{2x}{(r + 1)^2 + x^2}$$

$$[U - r / (r + 1)]^2 + V^2 = \frac{1}{(r + 1)^2}$$

$$(U - 1)^2 + (V - 1/x)^2 = \frac{1}{x^2}$$

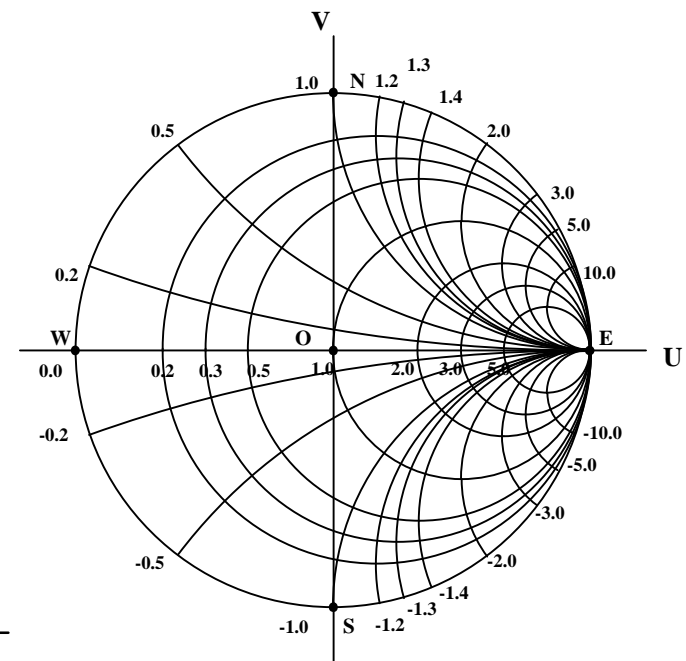


Figure 4.5 Impedance coordination of Smith Chart

\* Admittance coordination

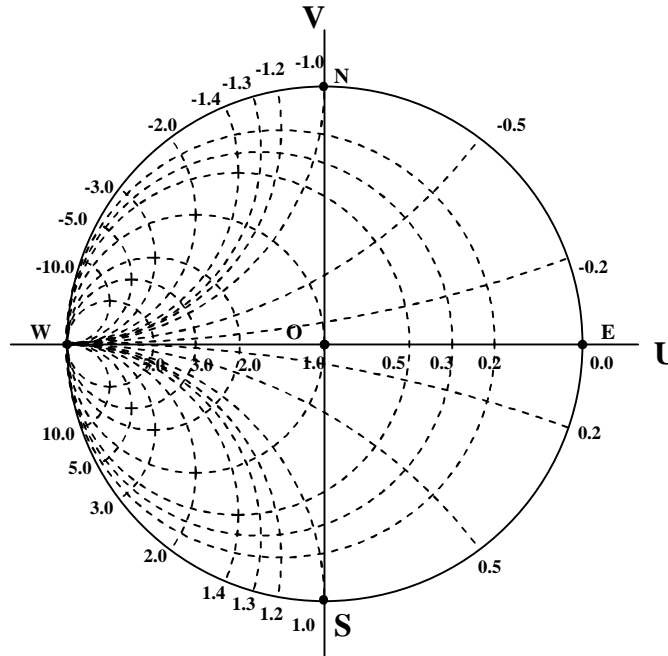


Figure 4.6 Admittance coordination of the Smith Chart

$$y = g + jb$$

$$y = \frac{1}{z} = \frac{1 - \Gamma}{1 + \Gamma}$$

The y curve can be obtained by rotating of z curve with 180° because

$$y = \frac{1}{z} = \frac{1 - \Gamma}{1 + \Gamma} = \frac{1 + \Gamma e^{jP}}{1 - \Gamma e^{jP}}$$

\* Impedance and admittance coordination together

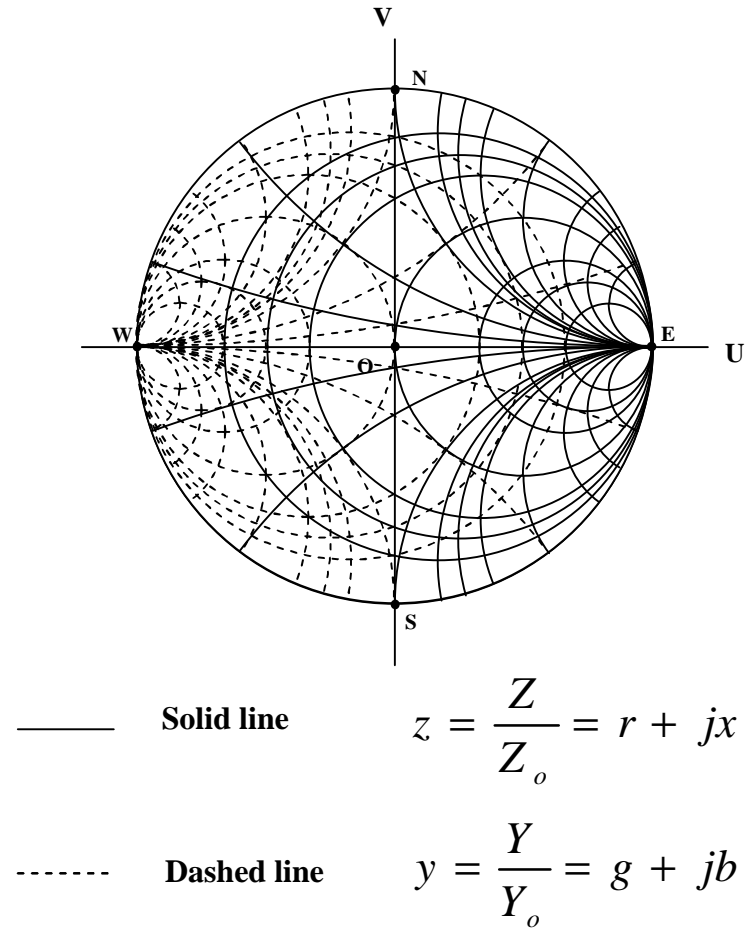


Figure 4.7 Impedance and admittance coordination of Smith Chart

**\* Scales on Smith chart**

**Some scaled parameters are attached below the Smith Chart :**

- \* Reflection coefficient of power,  $G^2$ ,**
- \* Return loss in dB,  $-10\log(G^2)$ ,**
- \* Reflection loss in dB,  $-10\log(1-G^2)$ ,**
- \* VSWR (Voltage Standing Wave Ratio),  $(1+|G|)/(1-|G|)$ ,**
- \* VSWR in dB,  $20\log(1+|G|)/(1-|G|)$ ,**
- \* Transmission loss coefficient,  $(1+|G|^2)/(1-|G|^2)$ .**



o Calibration of network analyzer

\* A test PCB










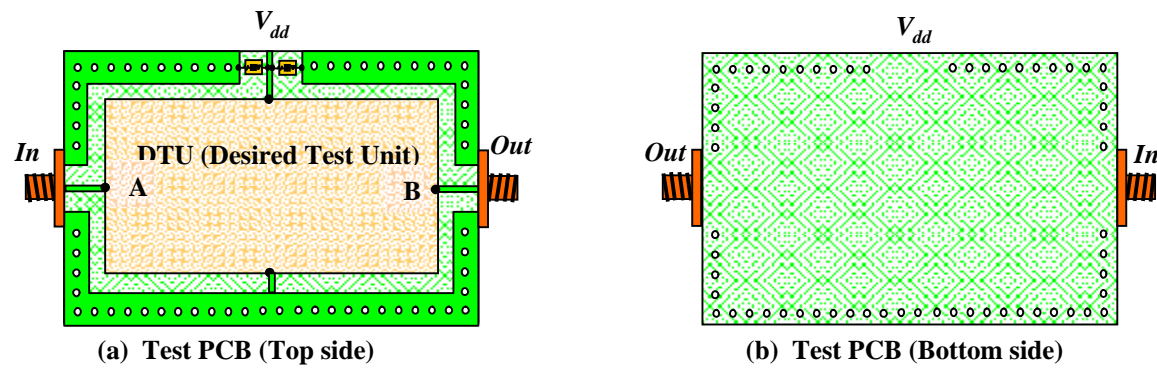
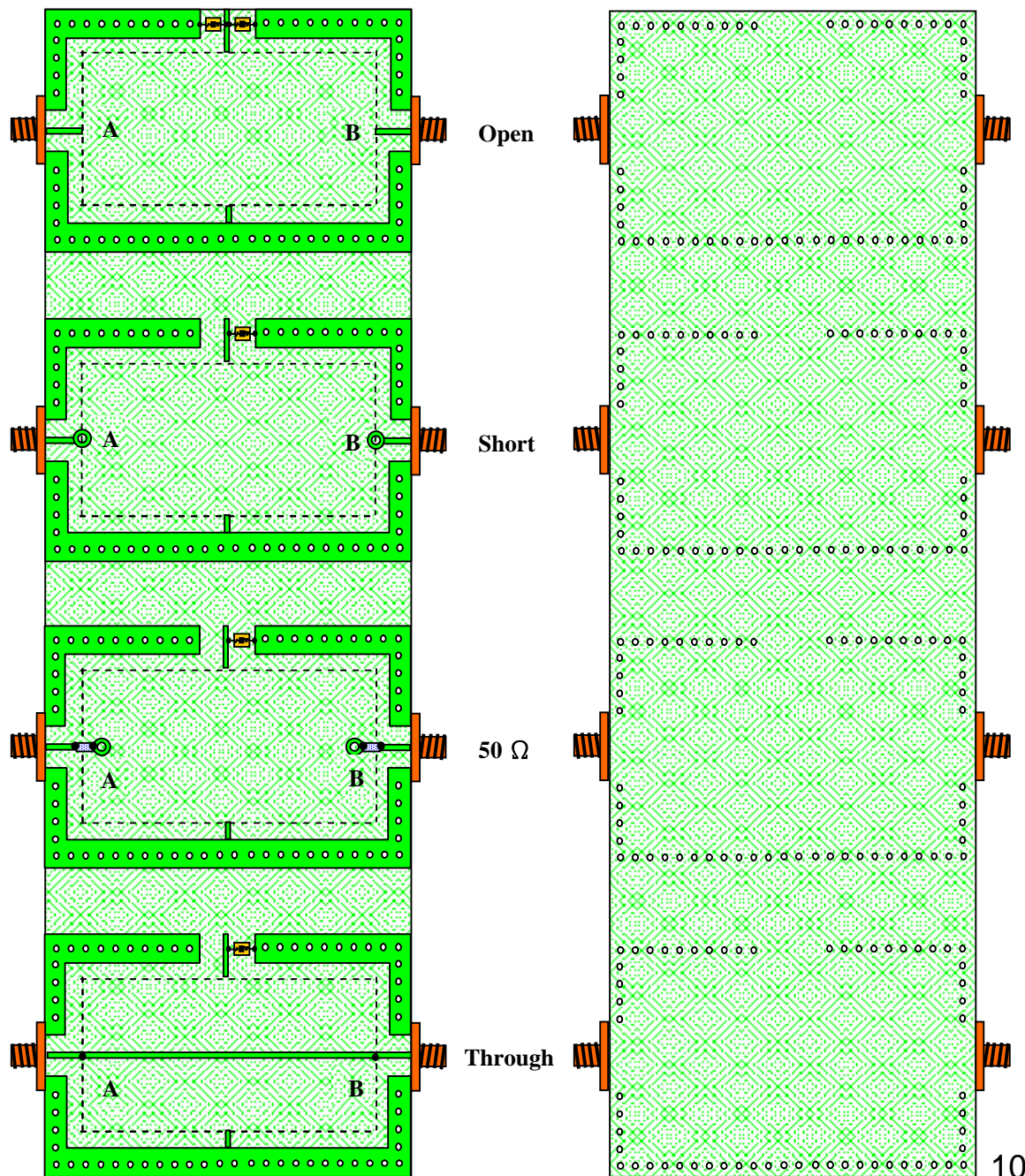
Figure 4.8 Layout of test PCB



\* Calibration Board  
for Network Analyzer

Figure 4.9 Layout of a self-supporting calibration kit

-  Top metallic area;
-  Bottom metallic area;
-  Conductive via from top to bottom
-  "Zero" capacitor
-  50  $\Omega$  resistor
-  Runner,  $Z_0 = 50 \Omega$ .
-  SMA connector



(a) Calibration kit (Top side)

(b) Calibration (Bottom side)

o Transformation of impedance between in series and in parallel

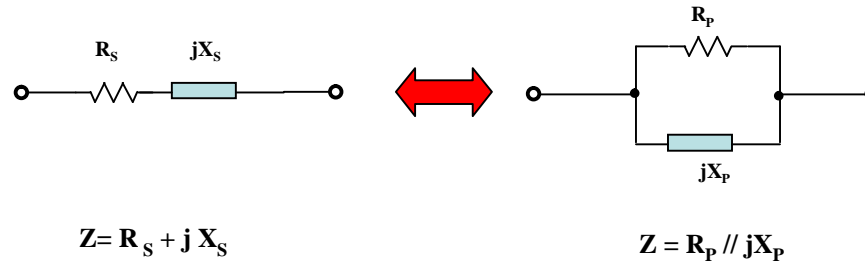


Figure 4.10 Transformation of impedance between in series and in parallel


$$R_s + jX_s = R_p // jX_p = \frac{X_p^2 R_p + jX_p R_p^2}{R_p^2 + X_p^2}$$

$$X_p = X_s \frac{Q^2 + 1}{Q^2} \cong X_s$$

$$R_p = R_s (Q^2 + 1) \cong \frac{X_s^2}{R_s}$$

$$Q = \frac{|X_s|}{R_s} = \frac{R_p}{|X_p|}$$

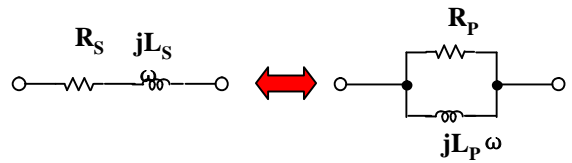Note :  $X_s$  and  $X_p$  could be either inductors or capacitors.




$$Z_S = R_S + jL_S \omega \quad Z_P = R_P // jL_P \omega$$

(a) When  $X_S$  and  $X_P$  are impedance of inductors

$$X_S = X_{LS} = L_S \omega$$

$$X_P = X_{LP} = L_P \omega$$

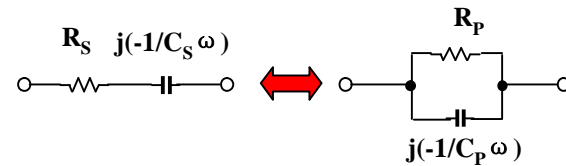

$$Z_S = R_S + j(-1/C_S \omega) \quad Z_P = R_P // j(-1/C_P \omega)$$

(b) When  $X_S$  and  $X_P$  are impedance of capacitors

$$X_S = X_{CS} = -\frac{1}{C_S \omega}$$

$$X_P = X_{CP} = -\frac{1}{C_P \omega}$$

Figure 4.11 Transformation of impedance between in series and in parallel

$$R_S + jL_S \omega = R_P // jL_P \omega = \frac{L_P^2 \omega^2 R_P + jL_P \omega R_P^2}{R_P^2 + L_P^2 \omega^2}$$

$$L_P = L_S \frac{Q^2 + 1}{Q^2}$$

$$R_P = R_S (Q^2 + 1)$$

$$Q = \frac{L_S \omega}{R_S} = \frac{R_P}{L_P \omega}$$

$$R_S + j\left(\frac{-1}{C_S \omega}\right) = R_P // j\left(\frac{-1}{C_P \omega}\right) = \frac{R_P - jR_P^2 C_P \omega}{R_P^2 C_P^2 \omega^2 + 1}$$

$$C_P = C_S \frac{Q^2}{Q^2 + 1}$$

$$R_P = R_S (Q^2 + 1)$$

$$Q = \frac{1}{R_S C_S \omega} = R_P C_P \omega$$

### 3. Impedance measured alternatively by network analyzer

#### o Accurate and inaccurate area of Smith Chart

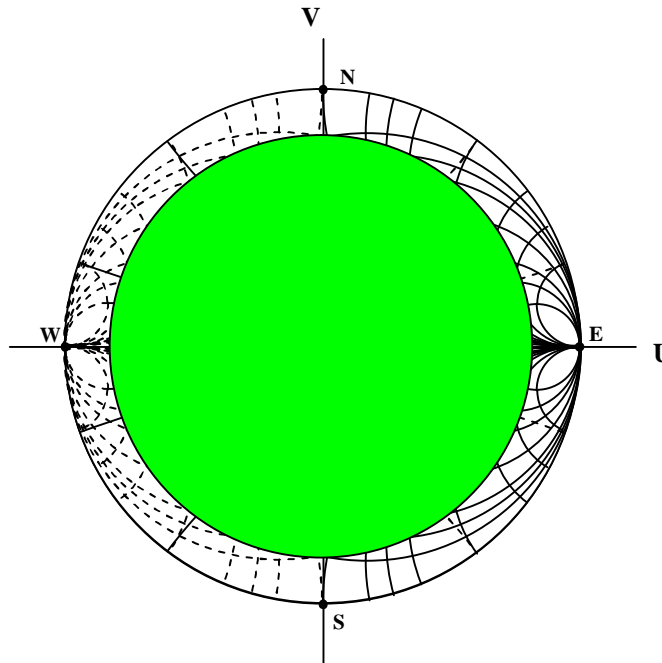

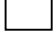


Figure 4.12 Accurate and inaccurate area in Smith Chart

 Relatively accurate area  
 Relatively inaccurate area



o Impedance measured by an alternative way

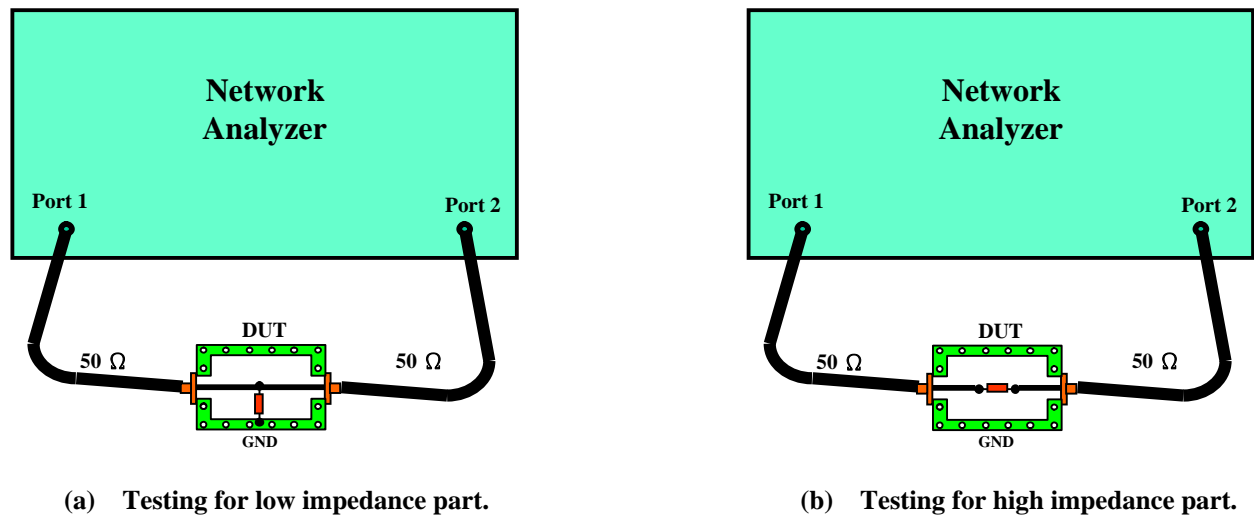


Figure 4.13 Testing setup for parts with low and high impedance  
●■● DTU (Desired Test Unit)

o Impedance measured by means of circulator

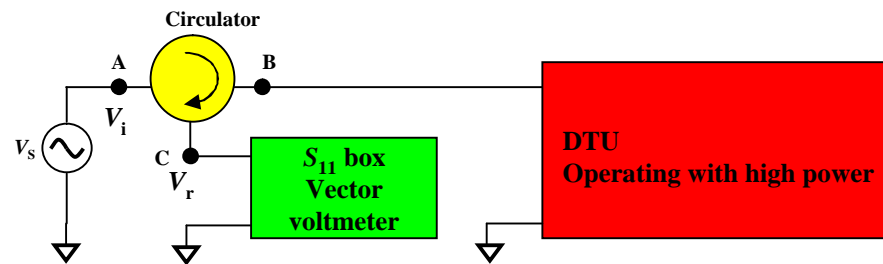


Figure 4.14 Impedance measurement by means of circulator.

$$\Gamma = \frac{V_r}{V_i}$$

$$z = \frac{1 + \Gamma}{1 - \Gamma}$$

o Impedance measuring and matching of a mixer :

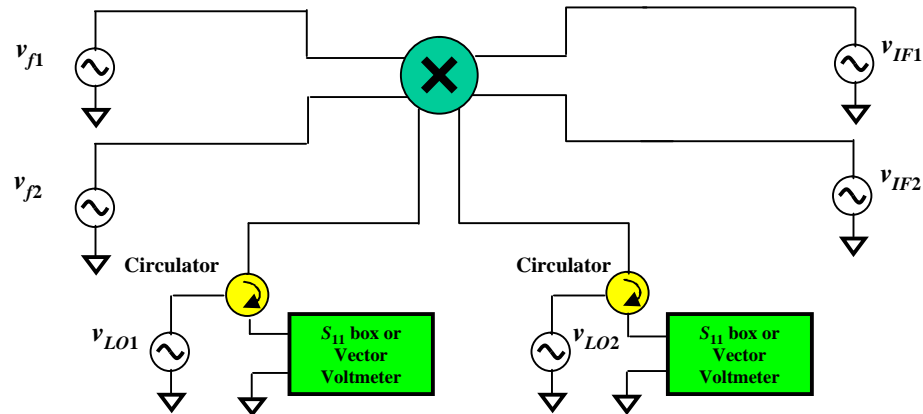


Figure 4.15 Impedance measurement and matching for a differential mixer by means of circulator.

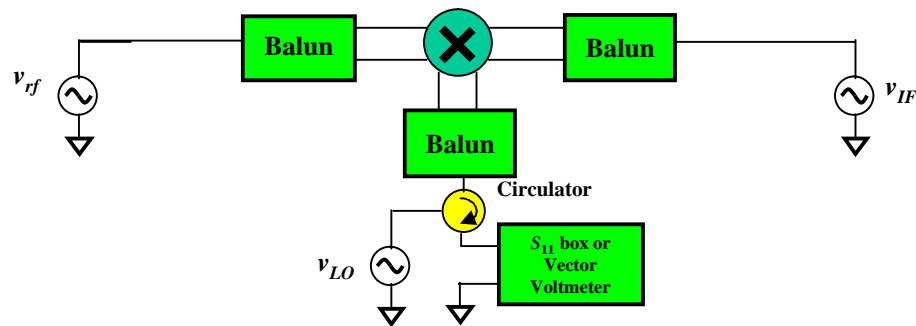


Figure 4.16 Change of impedance measurement and matching for a differential mixer by means of Balun.



## 射频和天线设计培训课程推荐

易迪拓培训([www.edatop.com](http://www.edatop.com))由数名来自于研发第一线的资深工程师发起成立,致力并专注于微波、射频、天线设计研发人才的培养;我们于 2006 年整合合并微波 EDA 网([www.mweda.com](http://www.mweda.com)),现已发展成为国内最大的微波射频和天线设计人才培养基地,成功推出多套微波射频以及天线设计经典培训课程和 ADS、HFSS 等专业软件使用培训课程,广受客户好评;并先后与人民邮电出版社、电子工业出版社合作出版了多本专业图书,帮助数万名工程师提升了专业技术能力。客户遍布中兴通讯、研通高频、埃威航电、国人通信等多家国内知名公司,以及台湾工业技术研究院、永业科技、全一电子等多家台湾地区企业。

易迪拓培训课程列表: <http://www.edatop.com/peixun/rfe/129.html>




### 射频工程师养成培训课程套装

该套装精选了射频专业基础培训课程、射频仿真设计培训课程和射频电路测量培训课程三个类别共 30 门视频培训课程和 3 本图书教材;旨在引领学员全面学习一个射频工程师需要熟悉、理解和掌握的专业知识和研发设计能力。通过套装的学习,能够让学员完全达到和胜任一个合格的射频工程师的要求...

课程网址: <http://www.edatop.com/peixun/rfe/110.html>
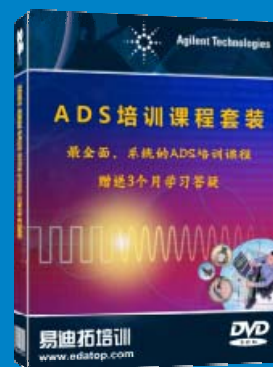
### ADS 学习培训课程套装

该套装是迄今国内最全面、最权威的 ADS 培训教程,共包含 10 门 ADS 学习培训课程。课程是由具有多年 ADS 使用经验的微波射频与通信系统设计领域资深专家讲解,并多结合设计实例,由浅入深、详细而又全面地讲解了 ADS 在微波射频电路设计、通信系统设计和电磁仿真设计方面的内容。能让您在最短的时间内学会使用 ADS,迅速提升个人技术能力,把 ADS 真正应用到实际研发工作中去,成为 ADS 设计专家...



课程网址: <http://www.edatop.com/peixun/ads/13.html>



### HFSS 学习培训课程套装

该套课程套装包含了本站全部 HFSS 培训课程,是迄今国内最全面、最专业的 HFSS 培训教程套装,可以帮助您从零开始,全面深入学习 HFSS 的各项功能和在多个方面的工程应用。购买套装,更可超值赠送 3 个月免费学习答疑,随时解答您学习过程中遇到的棘手问题,让您的 HFSS 学习更加轻松顺畅...

课程网址: <http://www.edatop.com/peixun/hfss/11.html>

## CST 学习培训课程套装

该培训套装由易迪拓培训联合微波 EDA 网共同推出,是最全面、系统、专业的 CST 微波工作室培训课程套装,所有课程都由经验丰富的专家授课,视频教学,可以帮助您从零开始,全面系统地学习 CST 微波工作的各项功能及其在微波射频、天线设计等领域的设计应用。且购买该套装,还可超值赠送 3 个月免费学习答疑...

课程网址: <http://www.edatop.com/peixun/cst/24.html>



## HFSS 天线设计培训课程套装

套装包含 6 门视频课程和 1 本图书,课程从基础讲起,内容由浅入深,理论介绍和实际操作讲解相结合,全面系统的讲解了 HFSS 天线设计的全过程。是国内最全面、最专业的 HFSS 天线设计课程,可以帮助您快速学习掌握如何使用 HFSS 设计天线,让天线设计不再难...

课程网址: <http://www.edatop.com/peixun/hfss/122.html>

## 13.56MHz NFC/RFID 线圈天线设计培训课程套装

套装包含 4 门视频培训课程,培训将 13.56MHz 线圈天线设计原理和仿真设计实践相结合,全面系统地讲解了 13.56MHz 线圈天线的工作原理、设计方法、设计考量以及使用 HFSS 和 CST 仿真分析线圈天线的具体操作,同时还介绍了 13.56MHz 线圈天线匹配电路的设计和调试。通过该套课程的学习,可以帮助您快速学习掌握 13.56MHz 线圈天线及其匹配电路的原理、设计和调试...

详情浏览: <http://www.edatop.com/peixun/antenna/116.html>



### 我们的课程优势:

- ※ 成立于 2004 年,10 多年丰富的行业经验,
- ※ 一直致力并专注于微波射频和天线设计工程师的培养,更了解该行业对人才的要求
- ※ 经验丰富的一线资深工程师讲授,结合实际工程案例,直观、实用、易学

### 联系我们:

- ※ 易迪拓培训官网: <http://www.edatop.com>
- ※ 微波 EDA 网: <http://www.mweda.com>
- ※ 官方淘宝店: <http://shop36920890.taobao.com>