

Lecture #6 : Single-ended stage and differential pair

1. Single-ended stage

- o General description
- o Small-signal model of a bipolar transistor
- o Small-signal model of a MOSFET transistor

2. Differential pair

- o DC transfer characteristic
- o Small signal characteristic
- o Improvement of CMRR
- o Increase of voltage swing
- o Interference cancellation
- o Increase of noise

3. Apparent difference between single ended stage and differential pair

4. DC offset

- o DC offset in a single ended device
- o Zero DC offset in a pseudo differential pair
- o Why “zero” IF or direct conversion
- o DC offset cancellation



1. Single-ended stage

o General description

* Voltage gain and current gain of a device in low frequency

Table 6.1 Voltage gain and current gain of a bipolar and CMOS device in low frequency. ($Z_{L,A}$ =Actual load impedance)

Configuration	Voltage gain	Current gain	Z_L _____.
CE	$-g_m(r_o // z_L)$	b_o	$Z_L = R_C // z_{L,A}$
CB	$g_m z_L$	a_o	$Z_L = R_C // z_{L,A}$
CC	$\frac{(b_o + 1) \frac{r_o z_L}{r_o + z_L}}{r_b + r_p + (b_o + 1) \frac{r_o z_L}{r_o + z_L}} \rightarrow 1$	$(1 + g_m r_p) \frac{r_o}{r_o + z_L} \rightarrow (1 + b_o)$	$Z_L = R_E // z_{L,A}$
CS	$-g_m(r_d // z_L)$	$\rightarrow \infty$	$Z_L = R_d // z_{L,A}$
CG	$(g_m + g_{mb})z_L$	$\rightarrow 1$	$Z_L = R_d // z_{L,A}$
CD	$\frac{g_m r_d}{1 + (g_m + g_{mb})r_d + \frac{r_d}{z_L}}$	$\rightarrow \infty$	$Z_L = R_S // z_{L,A}$

o General description (Continued)

- * **In the cases when the RF circuit is operating in RF frequency range or the digital circuit is operating with high data rate,**
 - *Either voltage or current gain is less important than power gain. Power transportation must be considered as the first priority.*
 - *The power gain is mainly determined by the performance of input and output impedance matching. The designers very concern the input and output impedances in a variety of configurations,*
 - *A basic single ended amplifier can be demarcated into 3 portions.*

It is therefore concluded that the study of input and output impedances of a device, Z_{in} and Z_{out} , with different configuration becomes prerequisite.

 


Figure 6.1 A basic single ended amplifier can be demarcated into 3 portions.

- *Example #1: a LNA*
 - a) Input impedance matching*
 - b) Output impedance matching*
 - c) Low noise*
 - d) Power gain*

- *Example #2: a buffer after VCO*
 - a) High input impedance , unmatched*
 - b) With power gain*
 - c) Output impedance matching*
 - d) Load pulling test*

o Small-signal model of a bipolar transistor

 


Figure 6.2 Small-signal equivalent circuit model of a bipolar transistor

$$I_c = I_s \left(1 + \frac{V_{ce}}{V_A} \right) \exp \left(\frac{V_{be}}{V_T} \right) = I_s \left(1 + \frac{V_{ce}}{V_A} \right) \exp \left(\frac{qV_{be}}{kT} \right)$$

$$g_m = \frac{\partial I_c}{\partial V_{be}} = I_s \left(1 + \frac{V_{ce}}{V_A} \right) \frac{q}{kT} \exp \left(\frac{qV_{be}}{kT} \right) = \frac{qI_c}{kT}$$

$$C_p = C_b + C_{je} \qquad r_p = \frac{b_o}{g_m}$$

$$C_b = t_F g_m \qquad r_o = \frac{V_A}{I_c}$$

$$C_{je} = \frac{C_{jeo}}{\sqrt[3]{1 - \frac{V_D}{y_o}}} \qquad r_m = (1 \rightarrow 10) b_o r_o$$

$$C_m = \frac{C_{mo}}{\left(1 - \frac{V}{y_o} \right)^n}$$

 


Figure 6.3 Small-signal equivalent circuit model of a bipolar transistor in the high frequency.

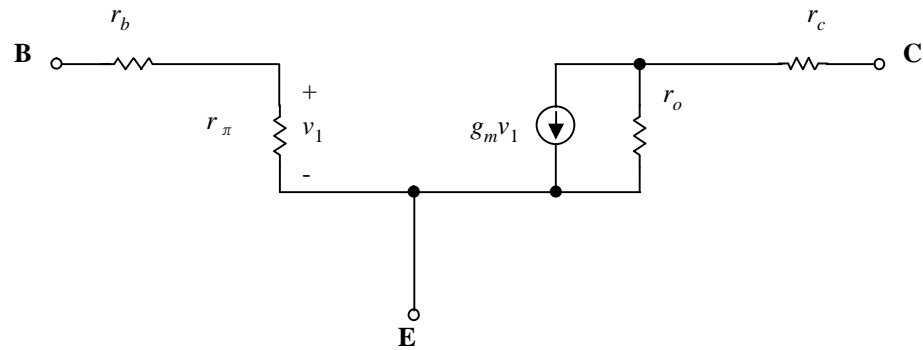


Figure 6.4 Small-signal equivalent circuit model of a bipolar transistor in the low frequency

* Impedance of a CE (common emitter) device

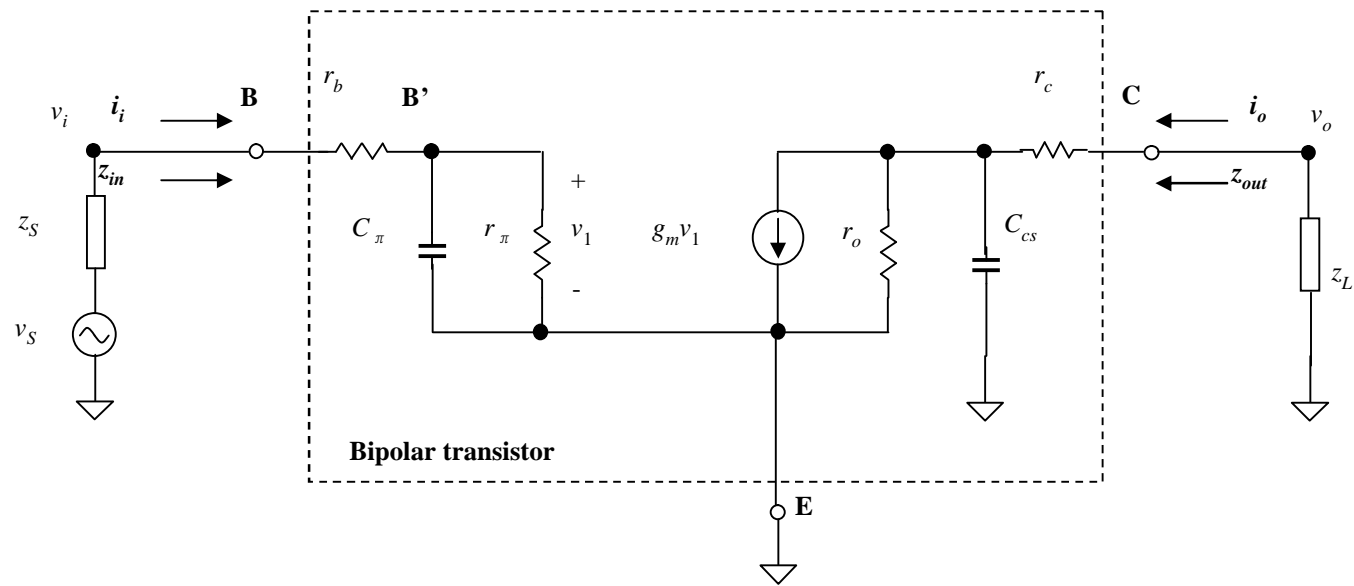


Figure 6.5 Small-signal equivalent circuit model of a CE (common emitter) device

$$z_{in} = r_b + \frac{1}{jC_p \omega} // r_p$$

$$Q = \frac{1}{r_s C_s \omega} = r_p C_p \omega \quad r_s = \frac{r_p}{(Q^2 + 1)} = \frac{r_p}{(r_p C_p \omega)^2 + 1}$$

$$C_s = C_p \frac{Q^2 + 1}{Q^2} = C_p \frac{(r_p C_p \omega)^2 + 1}{(r_p C_p \omega)^2}$$

$$z_{in} = \left[r_b + \frac{r_p}{(r_p C_p \omega)^2 + 1} \right] - j \frac{(r_p C_p \omega)^2}{C_p \omega [(r_p C_p \omega)^2 + 1]}$$

$$z_{out} = r_c + r_o // \frac{1}{jC_{cs} \omega}$$

$$z_{out} = \left[r_c + \frac{r_o}{(r_o C_{cs} \omega)^2 + 1} \right] - j \frac{(r_o C_{cs} \omega)^2}{C_{cs} \omega [(r_o C_{cs} \omega)^2 + 1]}$$

In the low-and mid-frequency, the capacitors, C_π and C_{cs} , are negligible, thus

$$z_{in} = r_b + r_p$$

$$z_{out} = r_c + r_o$$

* Impedance of a CB (common base) device

Approximations :

$$r_b \ll r_p$$

$$r_p \ll r_o$$

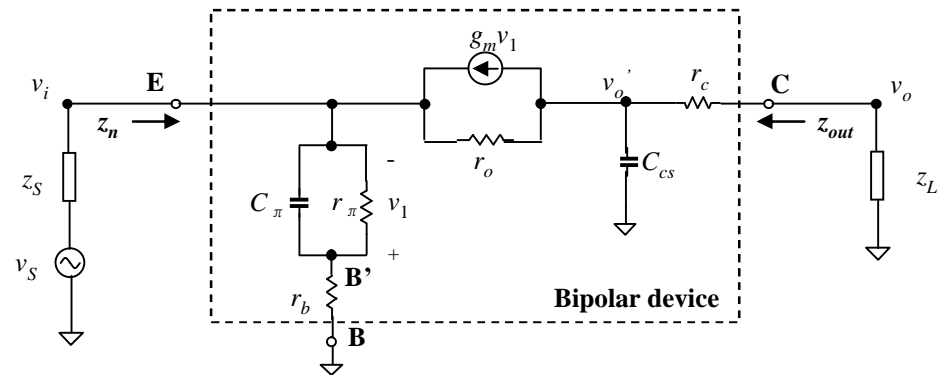


Figure 6.6 Small-signal equivalent circuit model of a CB (common base) device

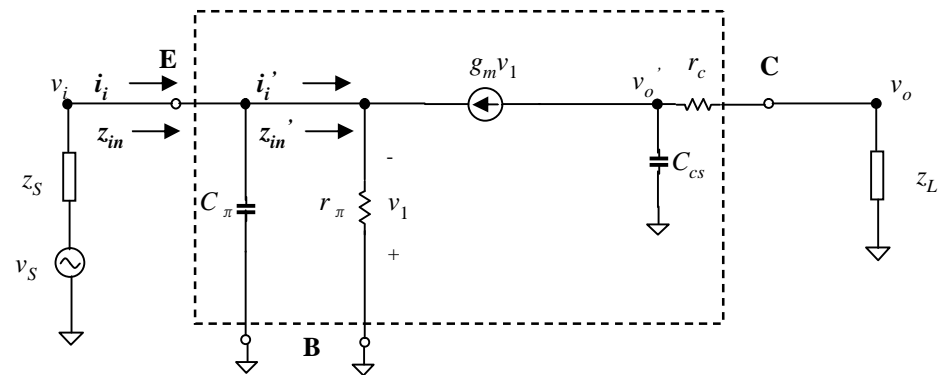


Figure 6.7 Small-signal equivalent circuit model of a CB (common base) device for input impedance discussion

$$v_i = -v_1$$

$$z_{in}' = \frac{v_i}{i_i'} = \frac{v_i}{\frac{v_i}{r_p} - g_m v_1} = \frac{v_i}{\frac{v_i}{r_p} + g_m v_i} = \frac{r_p}{1 + g_m r_p} \approx \frac{1}{g_m}$$

$$z_{in} = \frac{1}{jC_p W} // z_{in}' = \frac{r_p}{1 + r_p (g_m + jC_p W)} \approx \frac{1}{g_m + jC_p W}$$

However for higher accuracy when r_o is taken into account, the input impedance is dependent of the load, z_L . It would be modified to

$$z_{in} = \frac{r_p}{1 + r_p (g_m + jC_p W)} \left(1 + \frac{r_c + z_L}{r_o} \right)$$

At low-and mid-frequency,

$$z_{in} = \frac{r_p}{1 + r_p g_m} \left(1 + \frac{r_c + z_L}{r_o} \right)$$

For higher accuracy, the resistor r_b is taken into account,

$$z_{in} = \frac{r_p + r_b}{1 + (r_p + r_b)g_m} \left(1 + \frac{r_c + z_L}{r_o} \right)$$

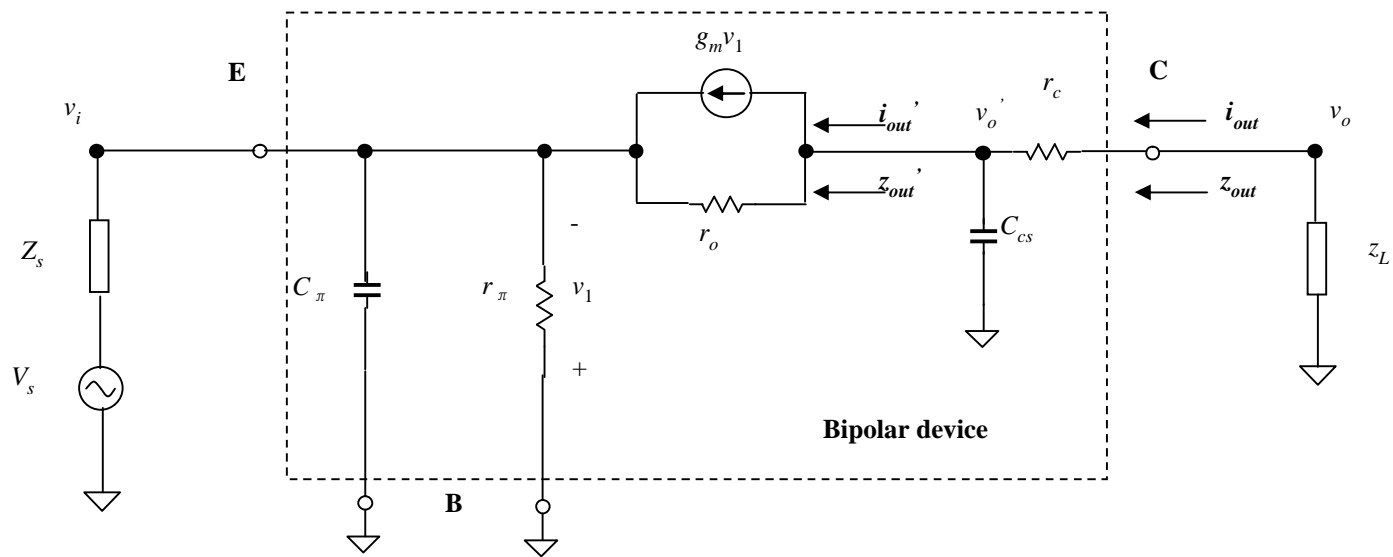


Figure 6.8 Small-signal equivalent circuit model of a CB (common base) device for output impedance discussion

$$i_{out}' = g_m v_1 + \frac{v_o' - v_i}{r_o} = -g_m v_i + \frac{v_o' - v_i}{r_o}$$

$$i_{out} = i_{out}' + \frac{v_o'}{jC_{CS}W} = \frac{v_o'}{r_o + R(1 + g_m r_o)} + v_o' jC_{CS}W = \left[\frac{1}{r_o + R(1 + g_m r_o)} + jC_{CS}W \right] v_o'$$

$$-\frac{v_i}{z_s // r_p // C_p} + \frac{v_o' - v_i}{r_o} + g_m(-v_i) = 0$$

$$v_i = \frac{1}{r_o \left(\frac{1}{R} + \frac{1}{r_o} + g_m \right)} v_o'$$

$$v_o = i_{out} r_c + v_o'$$

$$z_{out}' = \frac{v_o'}{i_{out}'} = r_o + R(1 + g_m r_o)$$

$$z_{out} = \frac{v_o}{i_{out}} = r_c + r_o + R(1 + g_m r_o)$$

$$z_{out} = \frac{v_o}{i_{out}} = r_c + \frac{1}{\frac{1}{r_o + R(1 + g_m r_o)} + jC_{CS}W}$$

$$R = z_s // r_p // C_p = \frac{z_s r_p \frac{1}{jC_p W}}{z_s r_p + r_p \frac{1}{jC_p W} + z_s \frac{1}{jC_p W}}$$

$$R = \frac{z_s r_p}{z_s + r_p + jC_p W z_s r_p}$$

$$R = \frac{z_s r_p}{z_s + r_p}$$

* Impedance of a CC (common collector) device

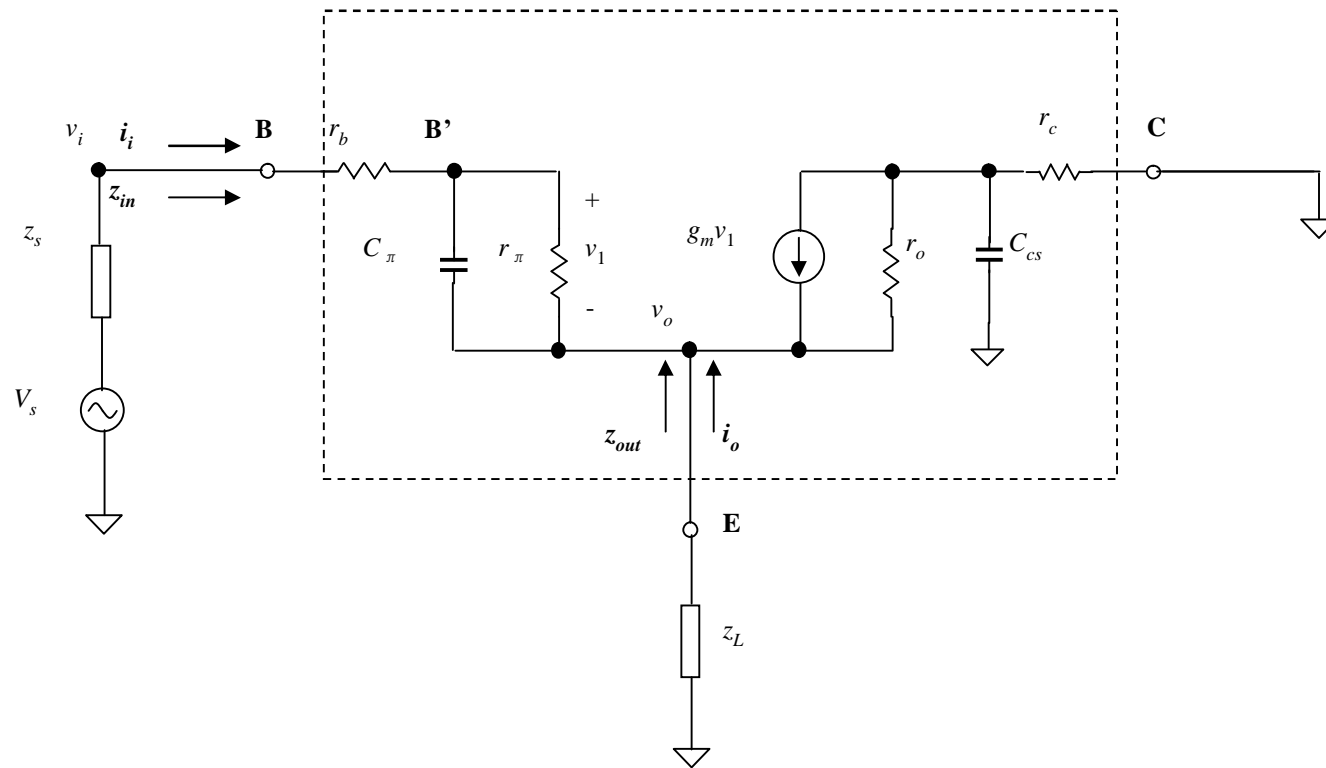


Figure 6.9 Small-signal equivalent circuit model of a CC (common collector) device

$$v_o = (i_i + g_m v_1) [z_L // (r_o + r_c // C_{cs})]$$

$$v_o = i_i [1 + g_m (r_p // C_p)] [z_L // (r_o + r_c // C_{cs})]$$

$$v_i = i_i (r_b + r_p // C_p) + i_i [1 + g_m (r_p // C_p)] [z_L // (r_o + r_c // C_{cs})]$$

$$z_{in} = \frac{v_i}{i_i} = (r_b + r_p // C_p) + [1 + g_m (r_p // C_p)] [z_L // (r_o + r_c // C_{cs})]$$

$$r_p // C_p = \frac{1}{1 + jC_p \omega r_p} r_p$$

$$r_b + r_p // C_p = \frac{r_b + r_p + jC_p \omega r_b r_p}{1 + jC_p \omega r_p}$$

$$r_o + r_c // C_{cs} = \frac{r_o + r_c + jC_{cs} \omega r_o r_c}{1 + jC_{cs} \omega r_c}$$

$$z_L // (r_o + r_c // C_{cs}) = \frac{r_o + r_c + jC_{cs} \omega r_o r_c}{z_L + r_o + r_c + jC_{cs} \omega r_c (r_o + Z_L)} z_L$$

$$z_{in} = \frac{r_p + r_b (1 + jC_p \omega r_p) + (1 + g_m (r_p // C_p)) \frac{r_o + r_c + jC_{cs} \omega r_o r_c}{z_L + r_o + r_c + jC_{cs} \omega r_c (r_o + Z_L)} z_L}{1 + jC_p \omega r_p}$$

$$i_o = \frac{v_o}{r_o + (r_c // C_{cs})} + g_m \frac{(r_p // C_p)v_o}{z_s + r_b + (r_p // C_p)} + \frac{v_o}{z_s + r_b + (r_p // C_p)}$$

$$i_o = \frac{1 + jC_{cs}wr_c}{r_c + r_o(1 + jC_{cs}wr_c)}v_o + \frac{1 + b + jC_pwr_p}{r_p + (z_s + r_b)(1 + jC_pwr_p)}v_o$$

$$\frac{1}{z_{out}} = \frac{i_o}{v_o} = \frac{1 + jC_{cs}wr_c}{r_c + r_o(1 + jC_{cs}wr_c)} + \frac{1 + b + jC_pwr_p}{r_p + (z_s + r_b)(1 + jC_pwr_p)}$$

$$z_{out} = \frac{[r_c + r_o(1 + jC_{cs}wr_c)][r_p + (z_s + r_b)(1 + jC_pwr_p)]}{(1 + jC_{cs}wr_c)[r_p + (z_s + r_b)(1 + jC_pwr_p)] + (1 + b + jC_pwr_p)[r_c + r_o(1 + jC_{cs}wr_c)]}$$

At the low-and mid-frequency,

$$z_{in} \approx r_p + r_b + (1 + b) \frac{r_o + r_c}{z_L + r_o + r_c} z_L$$

$$z_{out} \approx \frac{(r_c + r_o)(z_s + r_b + r_p)}{(1 + b)(r_c + r_o) + (z_s + r_b + r_p)}$$

$$r_o \gg z_L \quad z_{in} \approx r_p + r_b + (1 + b)z_L$$

$$r_p \gg z_s \quad z_{out} \approx \frac{1}{1 + b + \frac{r_p}{r_c + r_o}} r_p$$

$$r_o \gg r_p \quad z_{out} \approx \frac{1}{g_m}$$

* Comparison between CE, CB, and CC devise

Table 6.2 Input and output impedances of a bipolar amplifier with CE, CB, and CC configuration in low frequency.
 $Z_{L,A}$ = Actual load impedance

<u>Input impedance</u>	<u>Output impedance</u>	<u>Z_L</u>
CE (Common emitter)		
$Z_{in} = r_p + r_b$	$Z_{out} = r_o + r_c$	
CB (Common base)		
$Z_{in} \approx \frac{r_p + r_b}{1 + (r_p + r_b)g_m} \left(1 + \frac{r_c + Z_L}{r_o} \right)$	$Z_{out} \approx r_o + r_c + \frac{Z_s r_p}{Z_s + r_p} (1 + g_m r_o)$	$Z_L = R_C // Z_{L,A}$
CC (Common collector, or Emitter follower)		
$Z_{in} \approx r_p + r_b + (1 + \beta) \frac{r_o + r_c}{Z_L + r_o + r_c} Z_L$	$Z_{out} \approx \frac{(r_o + r_c)(Z_s + r_b + r_p)}{(1 + \beta)(r_o + r_c) + (Z_s + r_b + r_p)}$	$Z_L = R_E // Z_{L,A}$

o **Small-signal model of a MOSFET transistor**

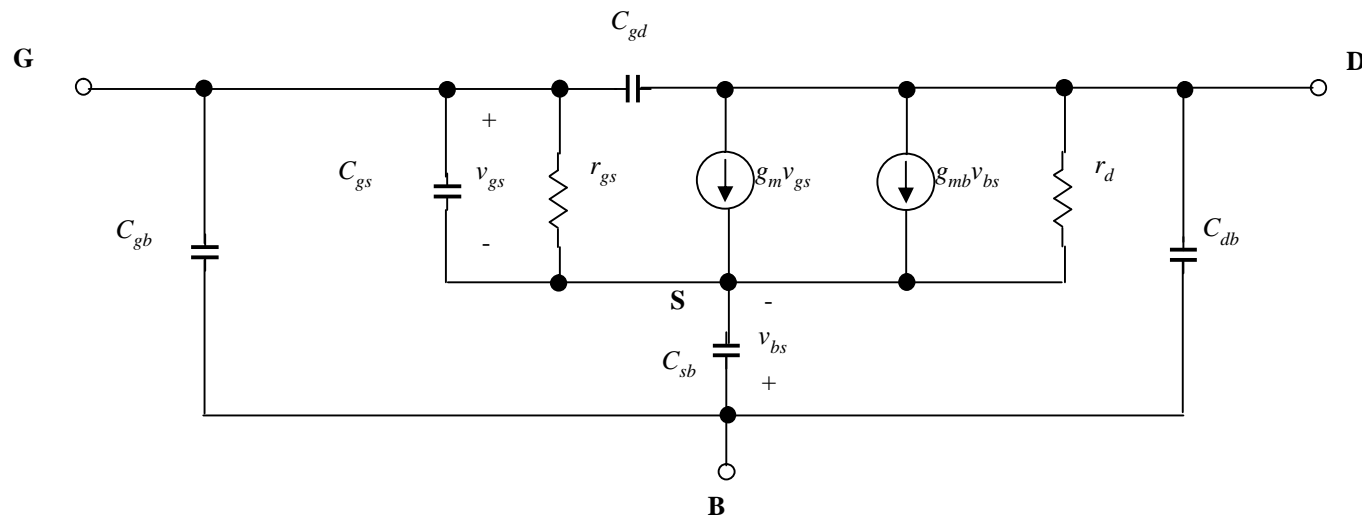


Figure 6.10 Small-signal equivalent circuit model of a MOSFET transistor

$$I_d = \frac{k'}{2} \frac{W}{L} (V_{gs} - V_t)^2 (1 + I V_{ds})$$

$$g_m = \frac{\partial I_d}{\partial V_{gs}} = k' \frac{W}{L} (V_{gs} - V_t) (1 + I V_{ds})$$

$$I V_{ds} \ll 1$$

$$I_d = \frac{k'}{2} \frac{W}{L} (V_{gs} - V_t)^2$$

$$g_m \approx k' \frac{W}{L} (V_{gs} - V_t) = \sqrt{2k' \frac{W}{L} I_d}$$

$$g_{mb} = c = \frac{C_{js}}{C_{ox}}$$

$$r_o = \frac{1}{II_d} = \frac{V_A}{I_d}$$

$$C_{gs} = \frac{2}{3} W L C_{ox}$$

$$f_t = \frac{1}{2p} \frac{g_m}{C_{gs} + C_{gd} + C_{gb}}$$

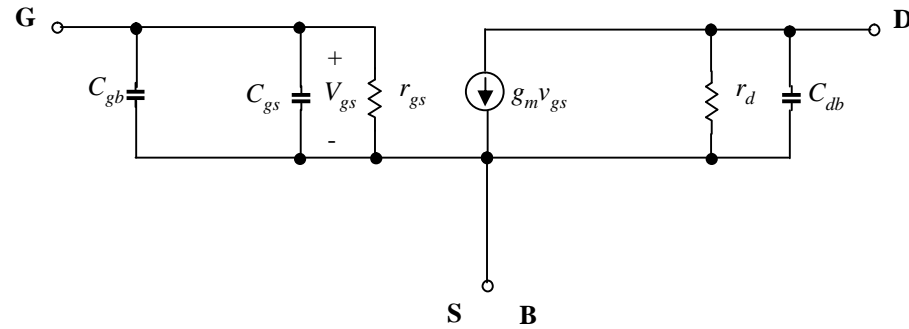


Figure 6.11 Small-signal equivalent circuit model of a MOSFET transistor in the high frequency (The source, S, is connected to the body, B.)

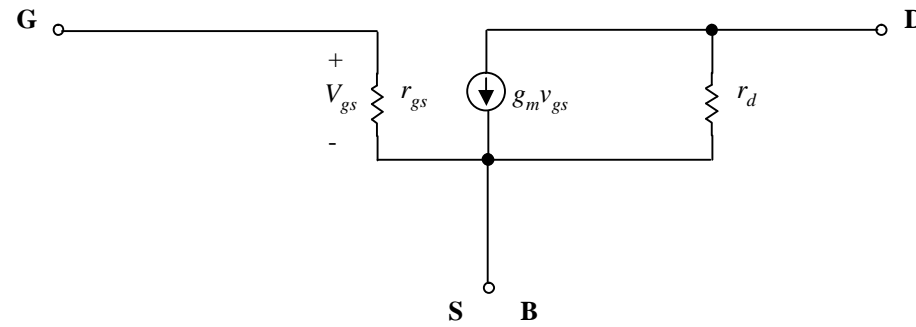


Figure 6.12 Small-signal equivalent circuit model of a MOSFET transistor in the low frequency (The source, S, is connected to the body, B.)

Translation

The similarity between bipolar and MOSFET model provides a short-cut to translate all of input and output impedance formula from the bipolar to MOSFET transistor, as long as we do the following replacements:

$$\begin{aligned} C_{\mu} &\rightarrow C_{gd}, \\ C_{cs} &\rightarrow C_{db}, \\ C_{\pi} &\rightarrow (C_{gs} + C_{gb}), \\ C_{sb} &\rightarrow \text{infinite} \end{aligned}$$

$$\begin{aligned} r_{\mu} &\rightarrow 0, \\ r_{ex} &\rightarrow 0, \\ r_b &\rightarrow 0, \end{aligned}$$

$$\begin{aligned} r_c &\rightarrow 0, \\ r_{\pi} &\rightarrow r_{gs}, \\ r_o &\rightarrow r_d, \\ \beta_o &\rightarrow g_m r_{gs}. \end{aligned}$$

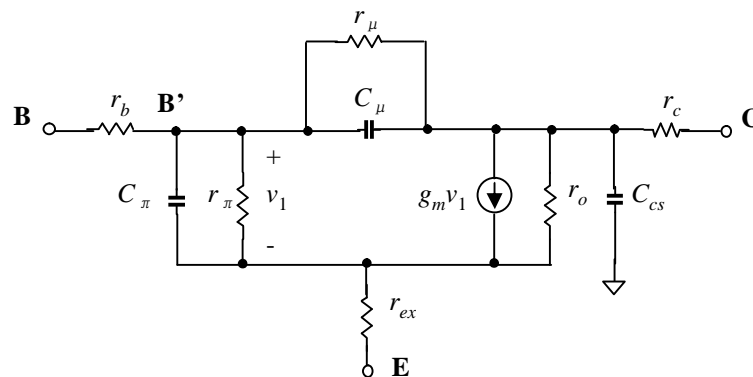


Figure 6.13 Small-signal equivalent circuit model of a bipolar transistor

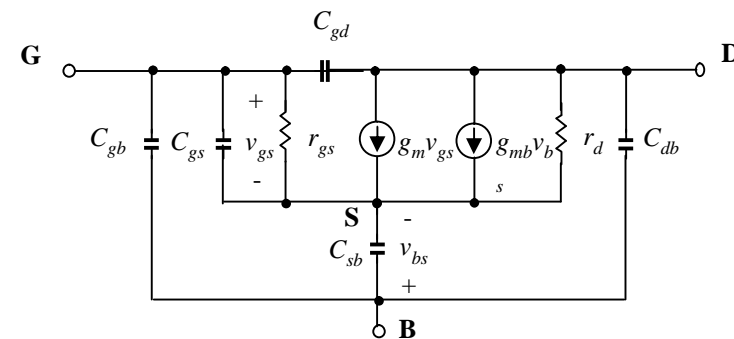


Figure 6.14 Small-signal equivalent circuit model of a MOSFET transistor

* Impedance of a CS (common source) device

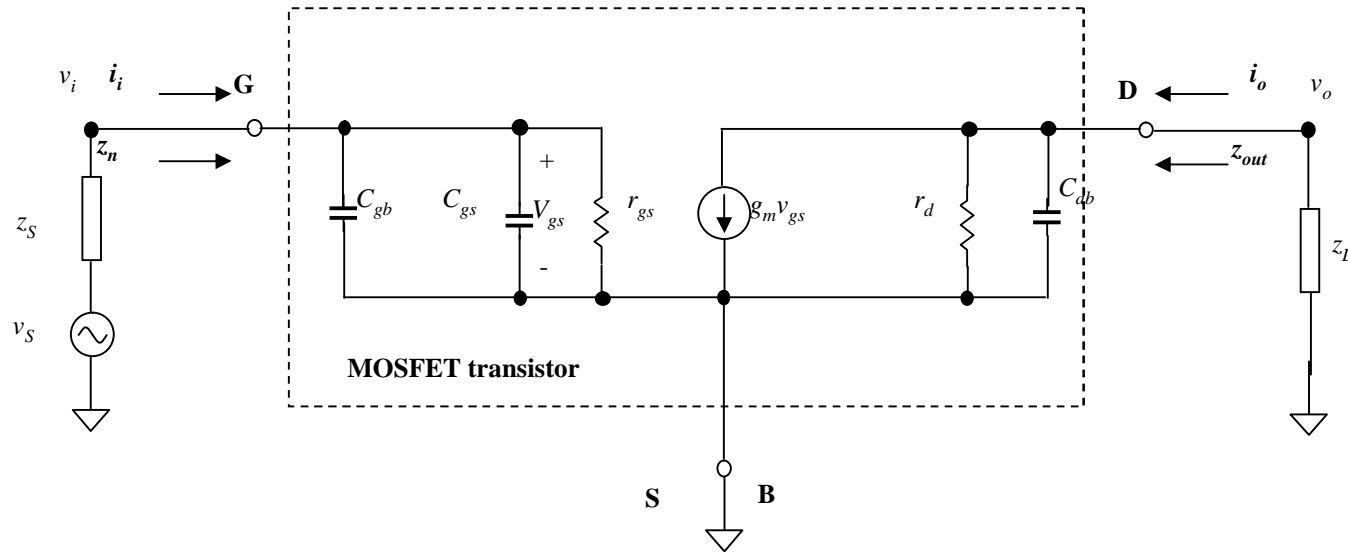


Figure 6.15 Small-signal equivalent circuit model of a CS (common source) device

$$z_{in} = \frac{r_{gs}}{[r_{gs}(C_{gs} + C_{gb})\omega]^2 + 1} - j \frac{[r_{gs}(C_{gs} + C_{gb})\omega]^2}{(C_{gs} + C_{gb})\omega\{[r_{gs}(C_{gs} + C_{gb})\omega]^2 + 1\}}$$

$$z_{out} = \frac{r_d}{(r_d C_{db} \omega)^2 + 1} - j \frac{(r_d C_{db} \omega)^2}{C_{db} \omega [(r_d C_{db} \omega)^2 + 1]}$$

At the low-and mid-frequency,

$$z_{in} = r_{gs}$$

$$z_{out} = r_d$$

* Impedance of a CG (common gate) device

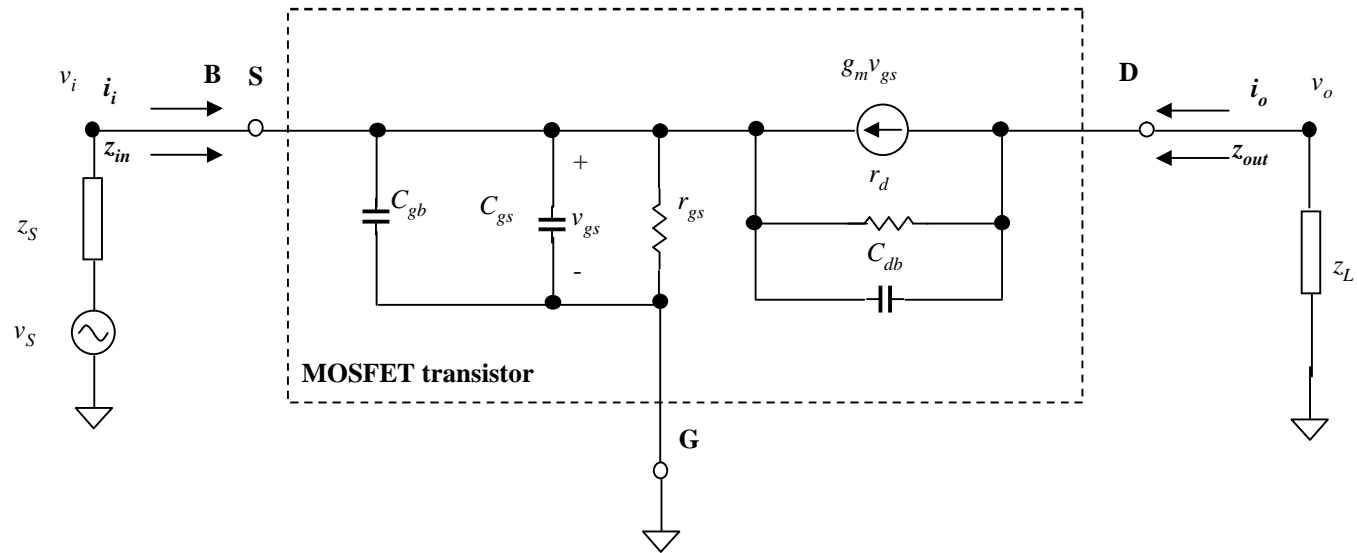


Figure 6.16 Small-signal equivalent circuit model of a CG (common gate) device

$$z_{in} = \frac{r_{gs}}{1 + r_{gs} [g_m + j(C_{gs} + C_{gd})\omega]} \left(1 + \frac{z_L}{r_d} \right) \quad z_{out} = \frac{1}{\frac{1}{r_d + \frac{z_S r_{gs}}{z_S + r_{gs} + j(C_{gs} + C_{gd})\omega}} + jC_{ds}\omega} (1 + g_m r_d)}$$

At the low-and mid-frequency,

$$z_{in} \approx \frac{r_{gs}}{1 + r_{gs} g_m} \left(1 + \frac{z_L}{r_d} \right) \quad z_{out} \approx r_d + \frac{z_S r_{gs}}{z_S + r_{gs}} (1 + g_m r_d)$$

* Impedance of a CD (common drain) device

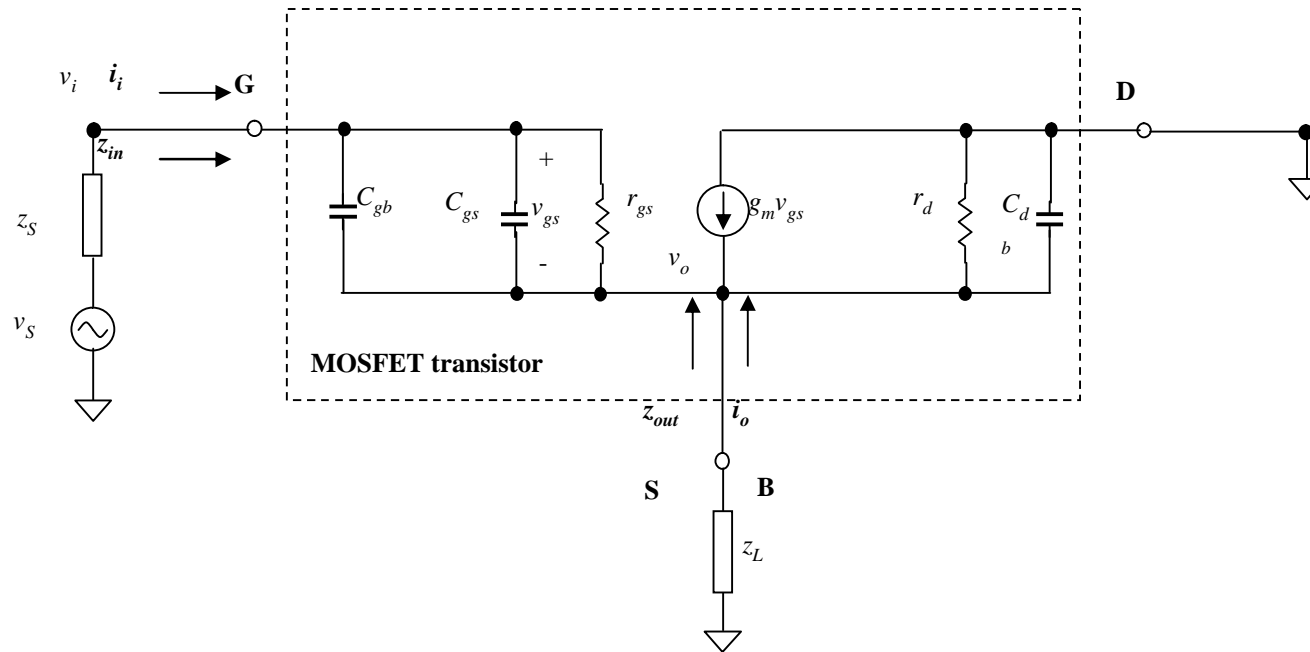


Figure 6.17 Small-signal equivalent circuit model of a CD (common drain) device

$$z_{in} = \frac{r_{gs} + [1 + g_m r_{gs} + j(C_{gs} + C_{gb})\omega r_{gs}] \frac{r_d}{z_L + r_d} z_L}{1 + j(C_{gs} + C_{gb})\omega r_{gs}}$$

$$z_{out} = \frac{r_d \{ r_{gs} + z_s [1 + j(C_{gs} + C_{gb})\omega r_{gs}] \}}{r_{gs} + z_s [1 + j(C_{gs} + C_{gb})\omega r_{gs}] + r_d [1 + g_m r_{gs} + j(C_{gs} + C_{gb})\omega r_{gs}]}$$

At the low-and mid-frequency,

$$z_{in} \approx r_{gs} + (1 + g_m r_{gs}) \frac{r_d}{z_L + r_d} z_L \quad z_{out} \approx \frac{r_d (z_s + r_{gs})}{(1 + g_m r_{gs}) r_d + (z_s + r_{gs})}$$

* **Comparison between CS, CG, and CD device**

Table 5.3 Input and output impedances of MOSFET transistor with CS,CG, and CD configuration in low and mid-frequency.

<u>Input impedance</u>	<u>Output impedance</u>	<u>Z_L</u>
CS (Common source)		
$z_{in} = r_{gs}$	$z_{out} = r_d$	
CG (Common gate)		
$z_{in} \approx \frac{r_{gs}}{1 + r_{gs} g_m} \left(1 + \frac{z_L}{r_d} \right)$	$z_{out} \approx r_d + \frac{z_s r_{gs}}{z_s + r_{gs}} (1 + g_m r_d)$	$z_L = R_d // z_{L,A}$
CD (Common drain or source follower)		
$z_{in} \approx r_{gs} + (1 + g_m r_{gs}) \frac{r_d}{z_L + r_d} z_L$	$z_{out} \approx \frac{r_d (z_s + r_{gs})}{(1 + g_m r_{gs}) r_d + (z_s + r_{gs})}$	$z_L = R_S // z_{L,A}$

2. Differential pair

o DC transfer characteristic

* Bipolar differential pair

 


Figure 6.18 A differential pair with bipolar devices

In the loop of V_{i1} à emitter of Q_1 à V_e à emitter of Q_2 à V_{i2} ,

$$V_{i1} - V_{be1} + V_{be2} - V_{i2} = 0$$

$$V_{be1} = V_T \ln \frac{I_{c1}}{I_{S1} \left(1 + \frac{V_{ce1}}{V_{A1}} \right)} \quad V_{be2} = V_T \ln \frac{I_{c2}}{I_{S2} \left(1 + \frac{V_{ce2}}{V_{A2}} \right)}$$

Assuming that the transistors are identical, that is

$$I_{s1} = I_{s2} = I_s$$

$$V_{ce1} = V_{ce2} = V_{ce}$$

$$V_{A1} = V_{A2} = V_A$$

$$a_{F1} = a_{F2} = a_F$$

$$\frac{I_{c1}}{I_{c2}} = \exp\left(\frac{V_{be1} - V_{be2}}{V_T}\right) = \exp\left(\frac{V_{i1} - V_{i2}}{V_T}\right) = \exp\left(\frac{V_{id}}{V_T}\right)$$

$$V_{id} = V_{i1} - V_{i2}$$

$$-(I_{e1} + I_{e2}) = I_{TL} = \frac{I_{c1} + I_{c2}}{a_F}$$

$$I_{c1} = \frac{a_F I_{TL}}{1 + \exp\left(-\frac{V_{id}}{V_T}\right)} \quad I_{c2} = \frac{a_F I_{TL}}{1 + \exp\left(\frac{V_{id}}{V_T}\right)}$$

$$V_{o1} = V_{cc} - I_{c1} R_c$$

$$V_{o2} = V_{cc} - I_{c2} R_c$$

$$R_{c1} = R_{c2} = R_c$$

$$V_{od} = V_{o1} - V_{o2} = a_F I_{TL} R_c \tanh\left(\frac{-V_{id}}{2V_T}\right)$$

***CMOS differential pair**

 


Figure 6.19 A differential pair with CMOS device

In the loop of V_{i1} à source of M_1 à V_s à source of M_2 à V_{i2} ,

$$V_{i1} - V_{gs1} + V_{gs2} - V_{i2} = 0$$

$$V_{gs1} - V_t = \sqrt{\frac{2I_{d1}}{k' \frac{W_1}{L_1} (1 + I V_{ds1})}} \quad V_{gs2} - V_t = \sqrt{\frac{2I_{d2}}{k' \frac{W_2}{L_2} (1 + I V_{ds2})}}$$

Assuming that the transistors are identical, that is

$$\begin{aligned} W_1 &= W_2 = W & L_1 &= L_2 = L \\ V_{ds1} &= V_{ds2} = V_{ds} \\ V_{id} &= V_{i1} - V_{i2} = V_{gs1} - V_{gs2} = \frac{\sqrt{I_{d1}} - \sqrt{I_{d2}}}{\sqrt{\frac{k' W}{2 L} (1 + I V_{ds})}} \end{aligned}$$

$$I_{d1} + I_{d2} = I_{TL}$$

$$I_{d1} = \frac{I_{TL}}{2} + \frac{k' W}{4 L} (1 + I V_{ds}) V_{id} = \sqrt{\frac{4I_{TL}}{\frac{k' W}{2 L} (1 + I V_{ds})} - V_{id}^2} \quad I_{d2} = \frac{I_{TL}}{2} - \frac{k' W}{4 L} (1 + I V_{ds}) V_{id} = \sqrt{\frac{4I_{TL}}{\frac{k' W}{2 L} (1 + I V_{ds})} - V_{id}^2}$$

$$\Delta I_d = I_{d1} - I_{d2} = \frac{k' W}{2 L} (1 + I V_{ds}) V_{id} \sqrt{\frac{4I_{TL}}{\frac{k' W}{2 L} (1 + I V_{ds})} - V_{id}^2}$$

$$V_{od} = V_{o1} - V_{o2} = (V_{dd} - I_{d1} R_d) - (V_{dd} - I_{d2} R_d) = -\Delta I_d R_d$$

$$V_{od} = -R_d \frac{k' W}{2 L} (1 + I V_{ds}) V_{id} \sqrt{\frac{4I_{TL}}{\frac{k' W}{2 L} (1 + I V_{ds})} - V_{id}^2}$$

o Small signal characteristic

Important reference : Paul R. Gray, Paul J. Hurst, Stephen H. Lewis, and Robert G. Meyer, "Analysis and Design of Analog Integrated Circuits," (Book), Fourth Edition, John Wiley & Sons, Inc., 2001.

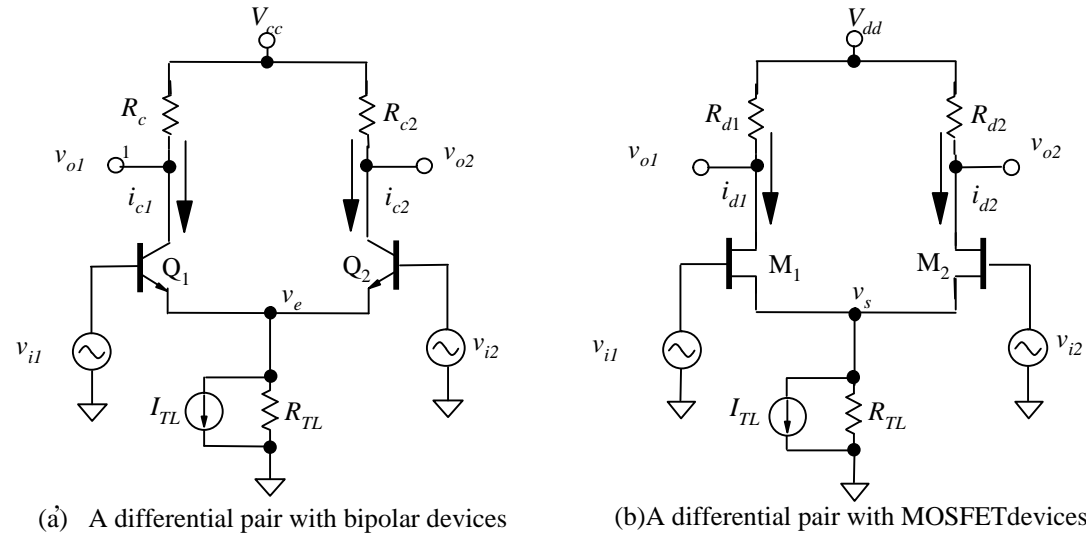


Figure 6.20 Differential pair

$$v_{o1} = A_{11}v_{i1} + A_{12}v_{i2}$$

$$v_{o2} = A_{21}v_{i1} + A_{22}v_{i2}$$

$$v_{ic} = \frac{v_{i1} + v_{i2}}{2}$$

$$v_{id} = v_{i1} - v_{i2}$$

$$v_{od} = v_{o1} - v_{o2}$$

$$v_{oc} = \frac{v_{o1} + v_{o2}}{2}$$

$$A_{dm} = \frac{A_{11} - A_{12} - A_{21} + A_{22}}{2}$$

$$A_{dm-cm} = \frac{A_{11} - A_{12} + A_{21} - A_{22}}{4}$$

$$A_{cm-dm} = A_{11} + A_{12} - A_{21} - A_{22}$$

$$A_{cm} = \frac{A_{11} + A_{12} + A_{21} + A_{22}}{2}$$

$$v_{od} = A_{dm}v_{id} + A_{cm-dm}v_{ic}$$

$$v_{oc} = A_{dm-cm}v_{id} + A_{cm}v_{ic}$$

$$v_{i1} = v_{ic} + \frac{v_{id}}{2}$$

$$v_{i2} = v_{ic} - \frac{v_{id}}{2}$$

$$v_{o1} = v_{oc} + \frac{v_{od}}{2}$$

$$v_{o2} = v_{oc} - \frac{v_{od}}{2}$$

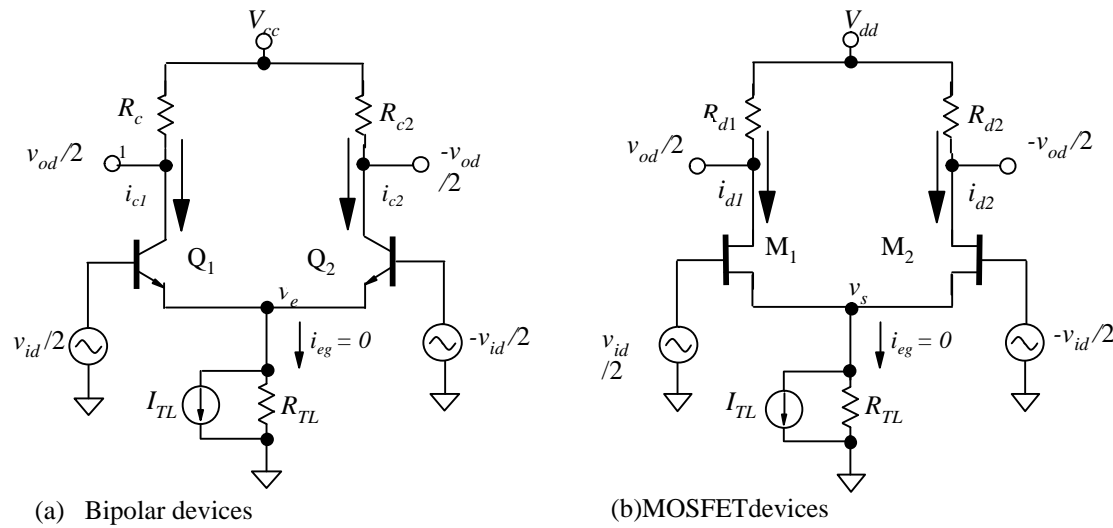


Figure 6.21 Differential mode portion of a differential pair

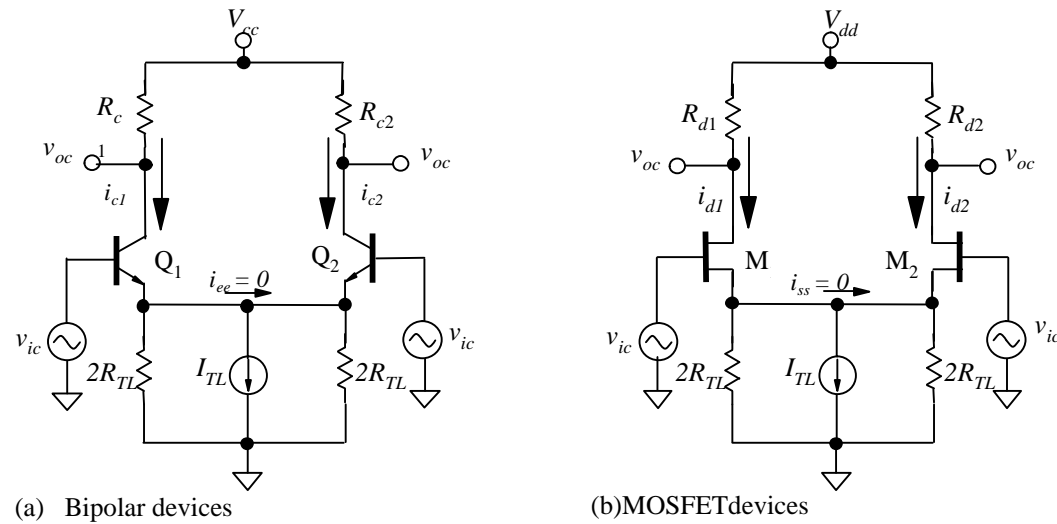


Figure 6.22 Commonmode portion of a differential pair

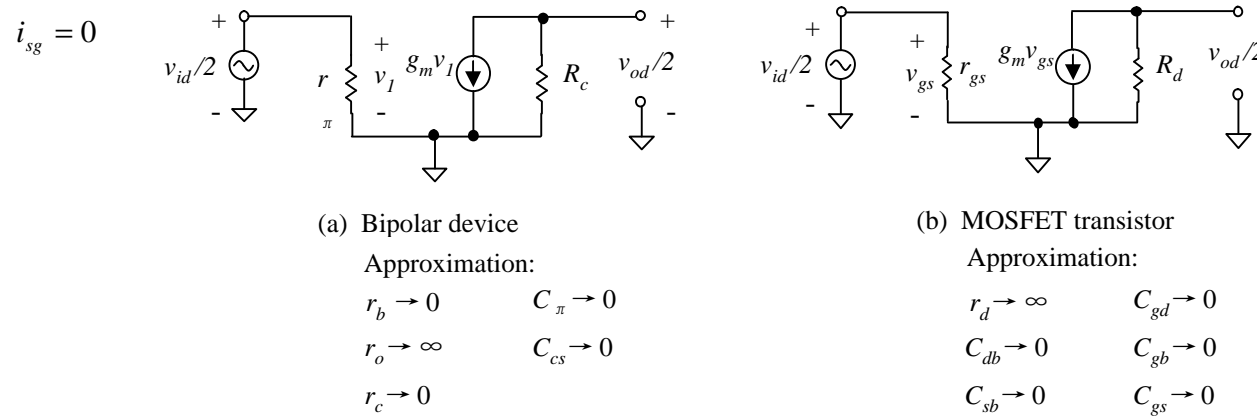


Figure 6.23 Equivalent of differential mode half circuit

$$\frac{v_{od}}{2} = -g_m v_1 R_c = -g_m \frac{v_{id}}{2} R_c$$

$$\frac{v_{od}}{2} = -g_m v_{gs} R_d = -g_m \frac{v_{id}}{2} R_d$$

$$R_c = R_{c1} = R_{c2}$$

$$R_d = R_{d1} = R_{d2}$$

$$\frac{v_{od}}{2} = -g_m \frac{v_{id}}{2} R$$

$$A_{dm} = \frac{v_{od}}{v_{id}} = -g_m R$$

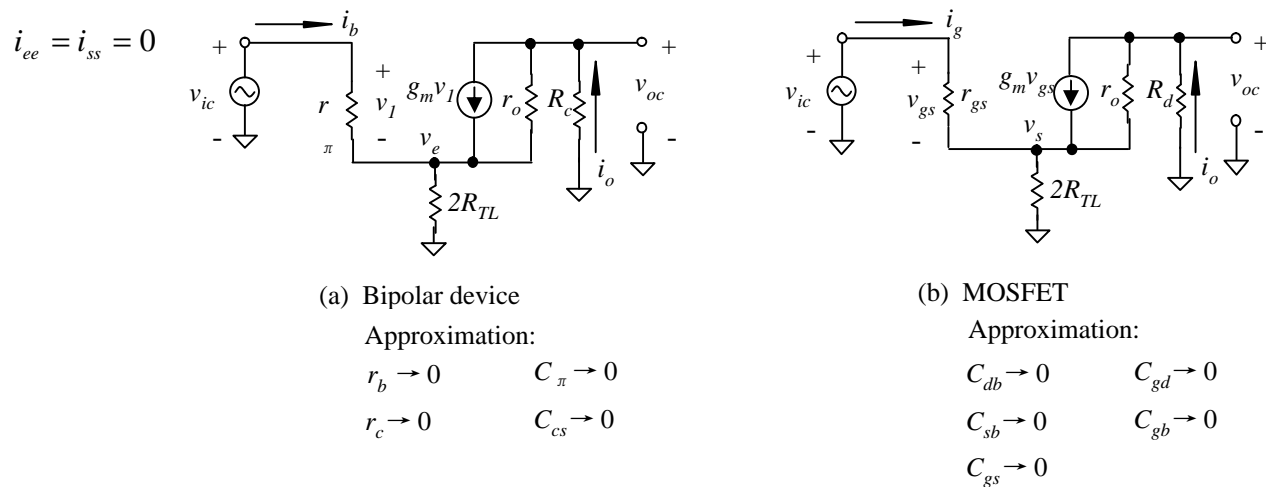


Figure 6.24 Equivalent of common mode half circuit

$$G_m = \frac{i_o}{v_{ic}} = g_m \frac{g_m}{1 + 2g_m R_{TL}(g_m r_p + 1)}$$

$$G_m = \frac{i_o}{v_{ic}} = \frac{g_m}{1 + 2g_m R_{TL}(g_m r_{gs} + 1)}$$

$$G_m = \frac{i_o}{v_{ic}} = \frac{g_m}{1 + 2g_m R_{TL}(g_m r_{p\,gs} + 1)}$$

$$r_o \gg R_{TL}$$

$$v_{oc} = -i_o R = -G_m R v_{ic}$$

$$A_{cm} = \frac{v_{oc}}{v_{ic}} = -G_m R = -\frac{g_m R}{1 + 2g_m R_{TL}(g_m r_{p\,gs} + 1)}$$

* **CMRR (Common Mode Rejection Ratio)**

$$CMRR = \frac{A_{dm}}{A_{cm}} = 1 + 2g_m R_{TL} \left(1 + \frac{1}{g_m r_{pgs}} \right)$$

* CMRR caused by a single-ended device

$$v_{i2} = v_{o2} = \mathbf{0}$$

$$v_{id} = v_{i1}$$

$$v_{ic} = v_{i1}/2$$

$$v_{od} = v_{o1}$$

$$v_{oc} = v_{o1}/2$$

and

$$v_{o1} = A_{11}v_{i1}$$

$$0 = A_{21}v_{i1}$$

or,

$$v_{od} = A_{dm} v_{id} + A_{cm-dm}v_{ic}/2$$

$$v_{oc} = A_{dm-cm}v_{id} + A_{cm} v_{ic}/2$$



$$\mathbf{CMRR} = A_{dm} / A_{cm} = \mathbf{1}$$

* A pseudo-differential pair



$$R_{TL} = 0$$

$$CMRR = 1$$

$$CMRR = 0 \text{ , dB.}$$

  

  (a) $R_{TL}=0, R_{e1}=0, R_{e2}=0$
 $R_{TL}=0, R_{s1}=0, R_{s2}=0$



(b) $R_{TL}=0, R_{e1} \neq 0, R_{e2} \neq 0$
 $R_{TL}=0, R_{s1} \neq 0, R_{s2} \neq 0$

Figure 6.25 Pseudo-differential pair.

o Improvement of CMRR

 


Figure 6.26 Emitter or source-coupled pair with degeneration resistors

$$A_{dm} = \frac{-g_m R}{1 + g_m R_{dg} \left(1 + \frac{1}{g_m R_{pgs}} \right)}$$

$$A_{cm} \approx \frac{-g_m R}{1 + 2g_m R_{TL} \left(1 + \frac{1}{g_m R_{pgs}} \right) \left(1 + \frac{R_{dg}}{2R_{TL}} \right)}$$

$$CMRR \approx \frac{A_{dm}}{A_{cm}} = \frac{1 + 2g_m R_{TL} \left(1 + \frac{1}{g_m R_{pgs}} \right) \left(1 + \frac{R_{dg}}{2R_{TL}} \right)}{1 + g_m R_{dg} \left(1 + \frac{1}{g_m R_{pgs}} \right)}$$

o **Improvement of CMRR (Continued)**

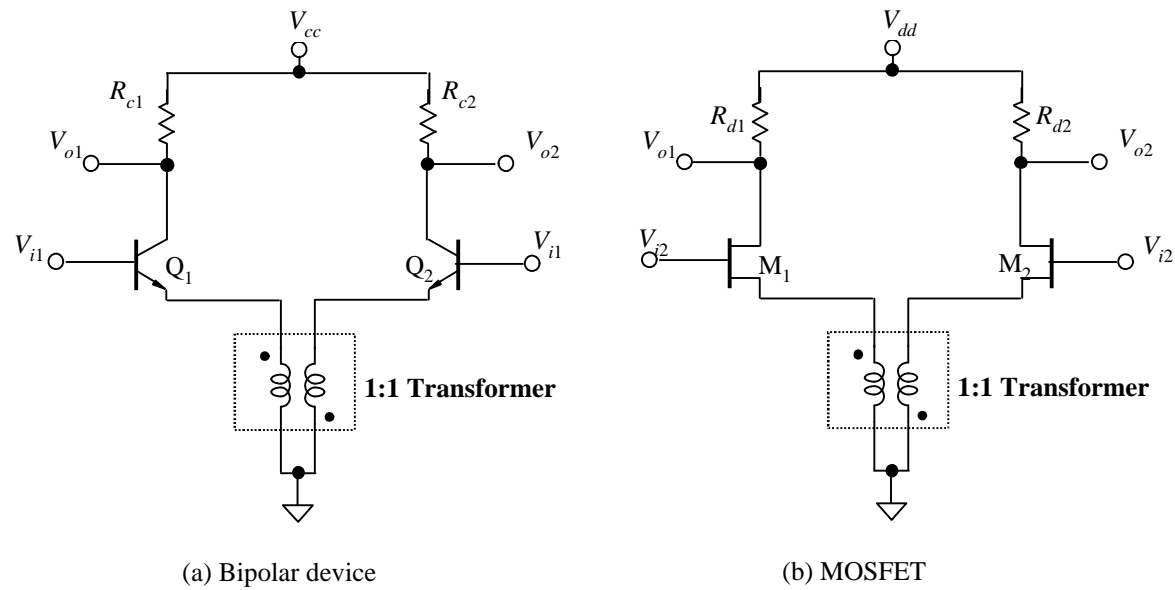


Figure 6.27 Improvement of CMRR by a 1:1 transformer

o Increase of voltage swing

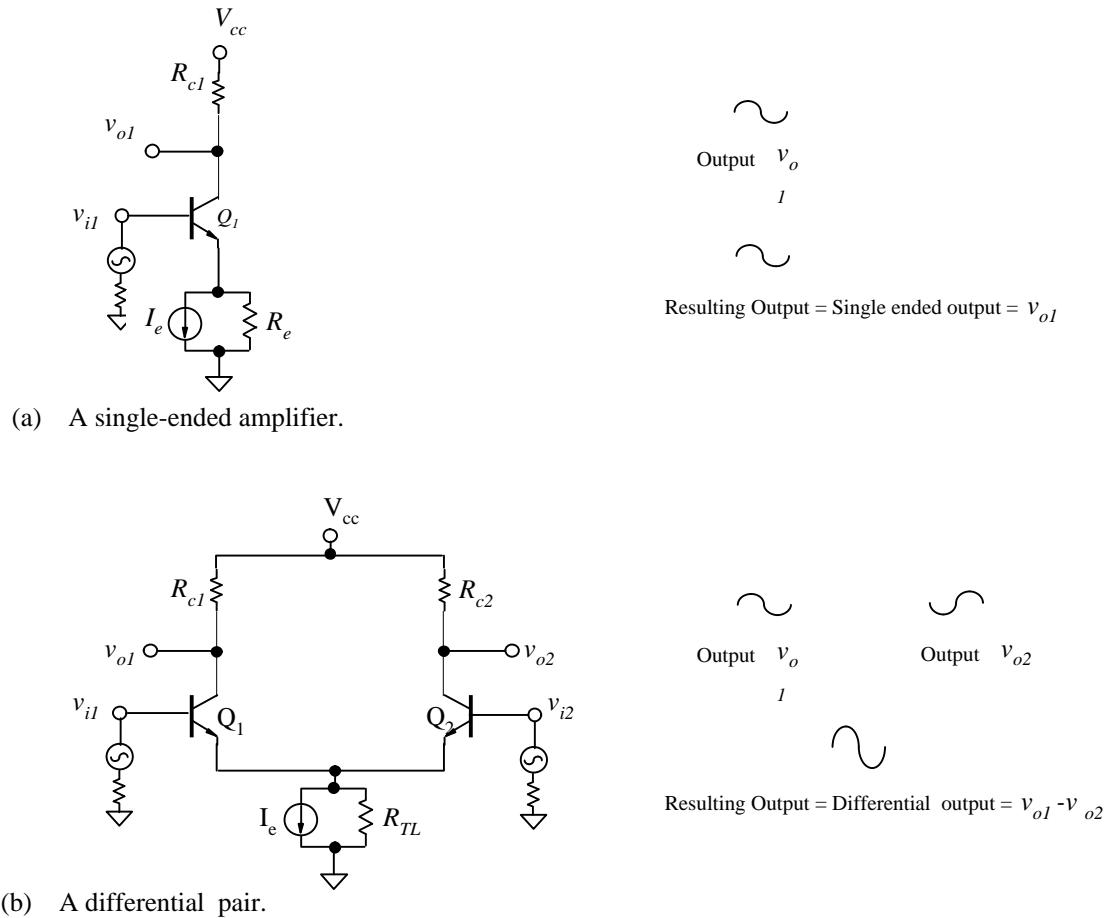


Figure 6.28 Increase of voltage swing in a differential pair

o Interference cancellation

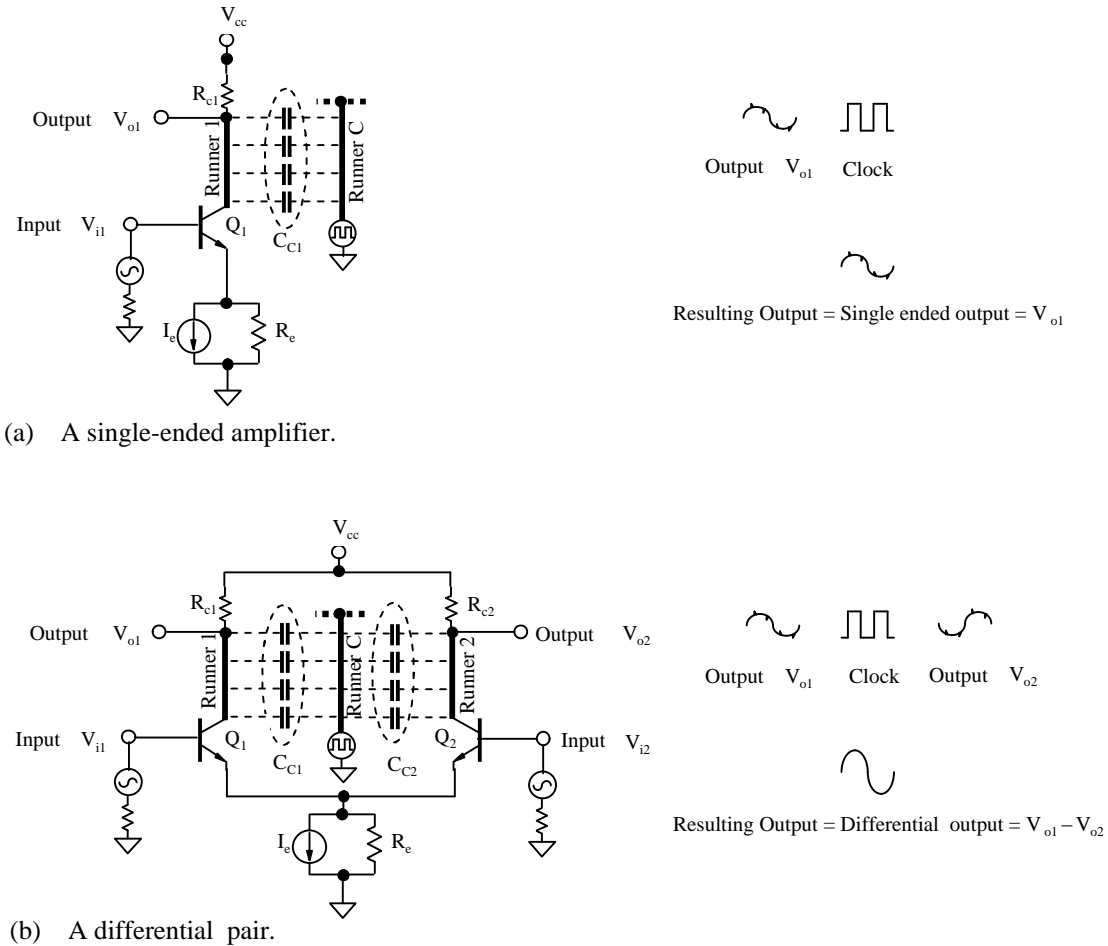


Figure 6.29 Interference cancellation in a differential pair

o Interference cancellation (Continued)

- **Figure 4.27** shows that a differential pair can reject the interference but no “**common mode noise**” .
- Noise is a random stochastic process.
It is nonsense to talk about “**common mode noise**” or “**differential mode noise**”
- **A differential pair rejects interference partially**
if the differential pair is in an imperfect symmetrical condition.
A differential pair rejects interference from outside totally
if the differential pair is in a perfect symmetrical condition.

oIncrease of noise

- * Noise can never be cancelled due to its differential function in a differential pair.
- * Noise figure of a differential pair is about 3 dB more than that of a single-ended branch.

 


Figure 6.30 At differential outputs, noise from DC power supply cannot be “differentiated away”!

 


Figure 6.31 At differential outputs, noise from Q_0 cannot be “differentiated away”!

Reasons:

- Two devices, Q1 and Q2, can be equivalent to two resistors, R_{c1} and R_{c2} .
- Then, by the same reasons as described in the previous problem, the process that these two devices attenuate or magnify the noise from Q_0 is a random stochastic process also.
- It is therefore concluded that it is impossible to keep attenuated or magnified noise exactly the same at two differential output terminals, V_{01} and V_{02} .

3. Apparent difference between single ended and differential stage

 


Figure 6.32 Single-ended block

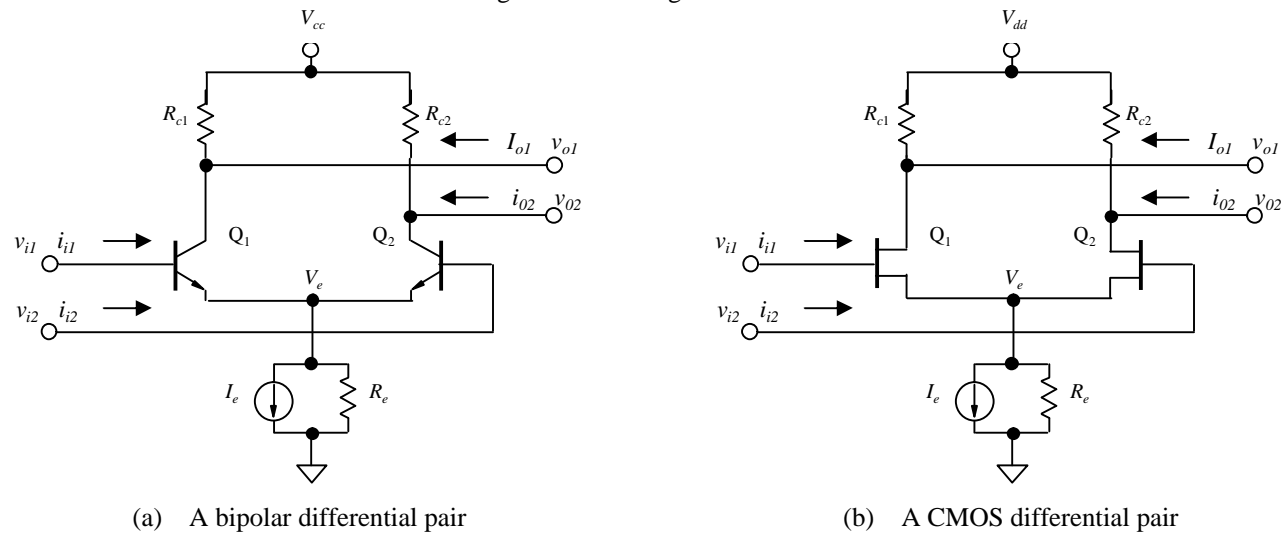


Figure 6.33 Differential pair .

o Definition of a differential pair:

$$\begin{array}{ll}
 v_{i1} = -v_{i2} & \text{or} & |v_{i1}| = |v_{i2}| & & i_{i1} = -i_{i2} & \text{or} & |i_{i1}| = |i_{i2}| \\
 & & \angle v_{i1} - \angle v_{i2} = 180^\circ & & & & \angle i_{i1} - \angle i_{i2} = 180^\circ \\
 \\
 v_{o1} = -v_{o2} & \text{or} & |v_{o1}| = |v_{o2}| & & i_{o1} = -i_{o2} & \text{or} & |i_{o1}| = |i_{o2}| \\
 & & \angle v_{o1} - \angle v_{o2} = 180^\circ & & & & \angle i_{o1} - \angle i_{o2} = 180^\circ
 \end{array}$$

o Apparent difference between single ended block and differential pair


Table 5.4 Apparent difference between single ended block and differential pair

	<u>Single-ended</u>	<u>Differential</u>
Current drain	1x	2x
Layout area	1x	2x
Symmetry	No	Yes
DC offset (In deal case)	Yes	No (Ideal)
CMRR (In deal case)	1	Infinitive (Ideal)




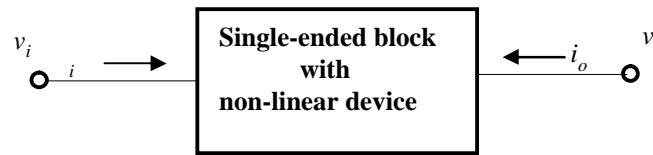4. DC offset

- o DC offset (In deal case) is formed by a single-ended device



(a) Block diagram

 

(b) Schematic

Figure 6.34 A single-ended block with non-linear device

$$V_{in} = V_i \sin \omega t$$

$$I_{out} = a_1 V_{in} + a_2 V_{in}^2 + a_3 V_{in}^3 + a_4 V_{in}^4 + \dots$$

$$= a_1 V_i \sin \omega t + a_2 V_i^2 \sin^2 \omega t + a_3 V_i^3 \sin^3 \omega t + a_4 V_i^4 \sin^4 \omega t + \dots$$

$$= a_1 V_i \sin \omega t + a_2 V_i [1 - \cos 2 \omega t] / 2 + a_3 V_i^3 [3 \sin \omega t - \sin 3 \omega t] / 4 + a_4 V_i^4 [3 - 4 \cos 2 \omega t + \cos 4 \omega t] / 8 +$$

.....


$$= a_1 V_i \sin \omega t - a_2 V_i^2 [\cos 2 \omega t] / 2 + a_3 V_i^3 [3 \sin \omega t - \sin 3 \omega t] / 4 + a_4 V_i^4 [-4 \cos 2 \omega t + \cos 4 \omega t] / 8 + a_2 V_i^2 / 2 + 3a_4 V_i^4 / 8 + \dots$$

$$I_{out, DC-offset} = a_2 V_i^2 / 2 + 3a_4 V_i^4 / 8 + \dots$$


DC offset is contributed by the even order non-linearity of the device.



 o DC offset (In deal case) caused by a pair of devices



(a) Block diagram

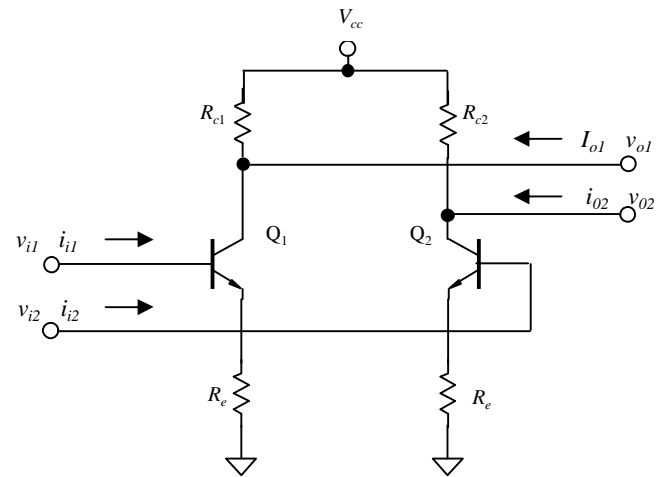

(b) schematic

Figure 6.35 A differential pair with non-linear devices without coupling

$$V_{id} = V_{i1} \sin \omega t - V_{i2} \sin(\omega t + 180^\circ)$$

$$I_{od} = I_{o1} - I_{o2}$$

$$\begin{aligned} I_{o1} &= a_1 V_{i1} \sin \omega t + a_2 V_{i1}^2 \sin^2 \omega t + a_3 V_{i1}^3 \sin^3 \omega t + a_4 V_{i1}^4 \sin^4 \omega t + \dots \\ &= a_1 V_{i1} \sin \omega t - a_2 V_{i1}^2 [\cos 2 \omega t] / 2 + a_3 V_{i1}^3 [3 \sin \omega t - \sin 3 \omega t] / 4 + a_4 V_{i1}^4 [-4 \cos 2 \omega t + \cos 4 \omega t] / 8 \end{aligned}$$

+

$$a_2 V_{i1}^2 / 2 + 3a_4 V_{i1}^4 / 8 + \dots$$

$$\begin{aligned} I_{o2} &= -a_1 V_{i2} \sin \omega t + a_2 V_{i2}^2 \sin^2 \omega t - a_3 V_{i2}^3 \sin^3 \omega t + a_4 V_{i2}^4 \sin^4 \omega t + \dots \\ &= -a_1 V_{i2} \sin \omega t + a_2 V_{i2}^2 [\cos 2 \omega t] / 2 - a_3 V_{i2}^3 [3 \sin \omega t - \sin 3 \omega t] / 4 + a_4 V_{i2}^4 [- \end{aligned}$$

4cos2 ω t + cos4 ω t] / 8 +

$$a_2 V_{i2}^2 / 2 + 3a_4 V_{i2}^4 / 8 + \dots$$

If $V_{i1} = V_{i2} = V_{in}$, then,

$$\begin{aligned} I_{od} &= I_{o1} - I_{o2} \\ &= 2 a_1 V_{in} \sin \omega t + 2 a_3 V_{i2}^3 [3 \sin \omega t - \sin 3 \omega t] / 4 + \dots \end{aligned}$$


$$I_{out, DC-offset} = 0$$

DC offset is zero due to the differential configuration.




o Why “zero” IF or direct conversion ?

 * In order to reduce the cost down, Zero-IF system replaces dual conversion system.



(a) Dual conversion receiver

 

(b) Direct conversion receiver

Figure 6.36 Block diagram of dual conversion and direct conversion receiver

- * **Zero-IF system hurt by DC-offset**
- * **DC-offset = 0 in a differential pair.**

o DC offset cancellation

* “Chopping” mixer

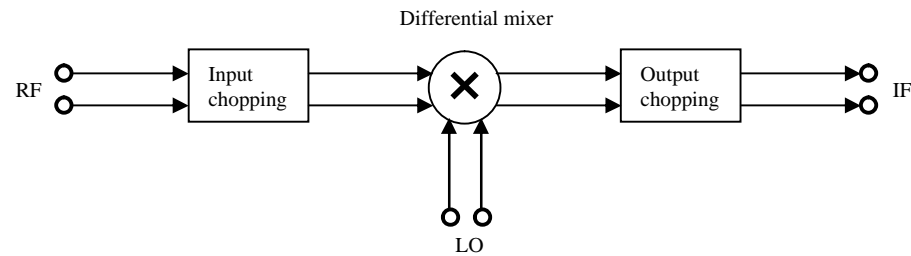


Figure 6.37 Block diagram of a “chopping” mixer

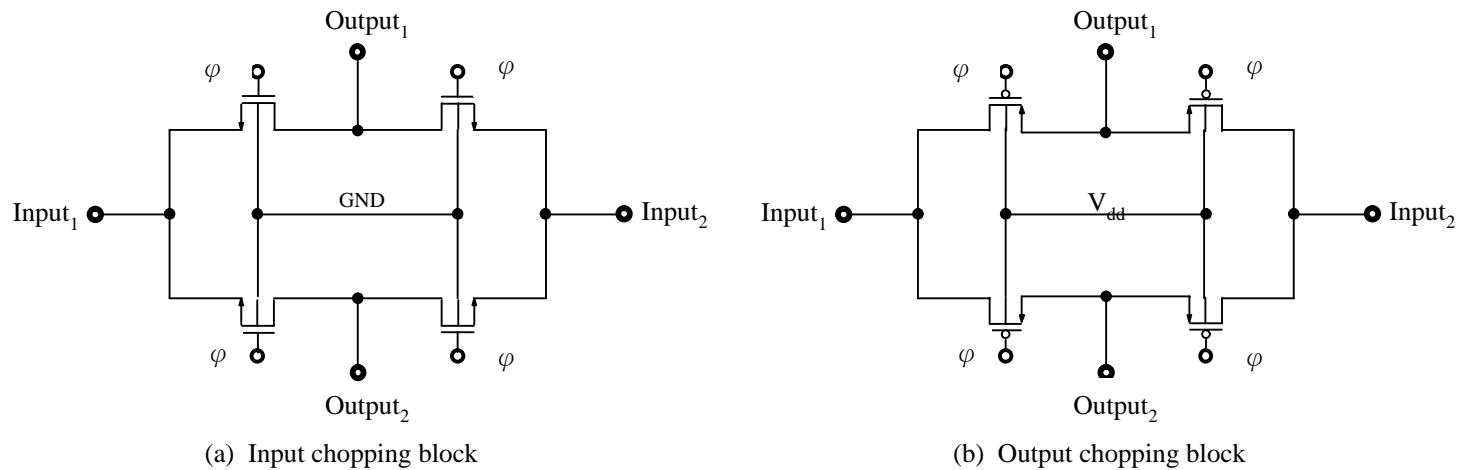


Figure 6.38 Input and output chopping block of a “chopping” mixer

 


Figure 6.39 Topology of a “chopping” mixer

 


Figure 6.40 Two interferers result an un-desired IP2 product in a mixer.

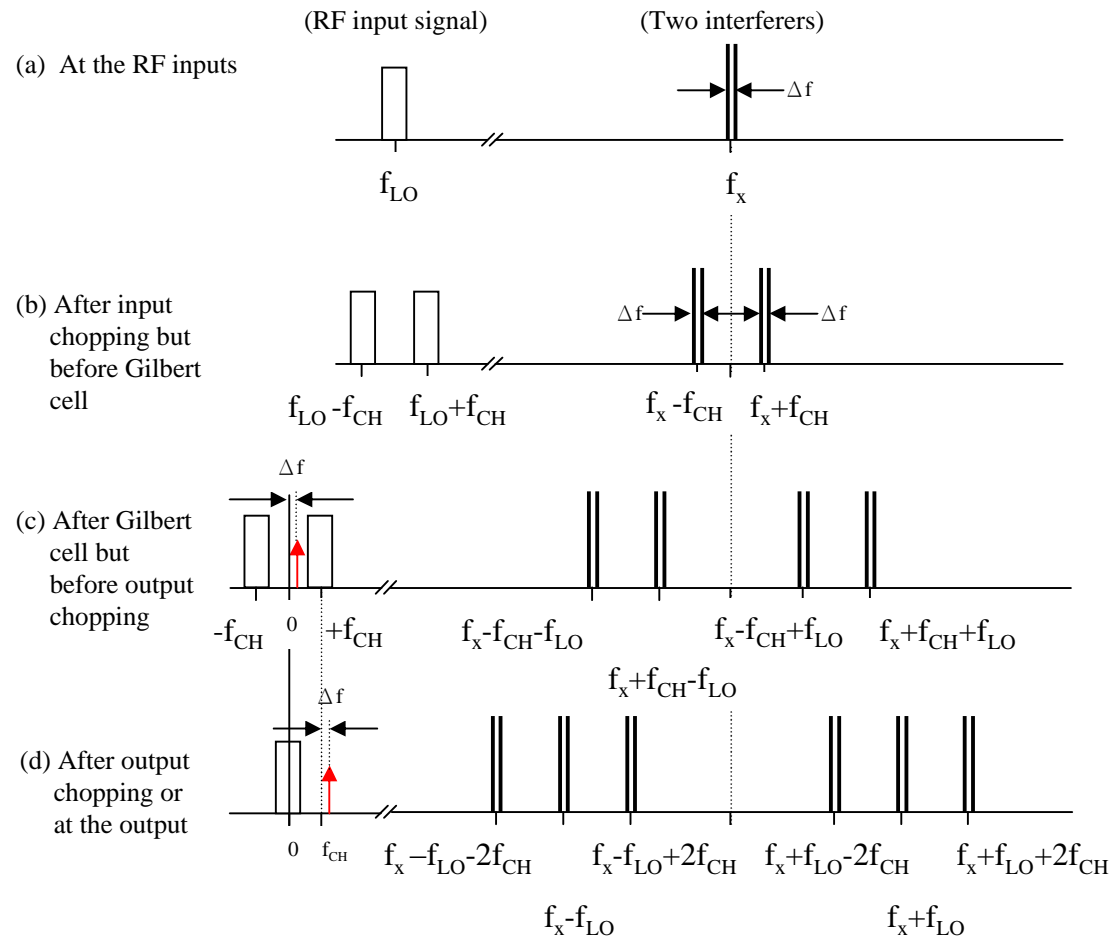


Figure 6.41 Principle of DC offset reduction in the "Chopping" mixer

* DC offset calibration

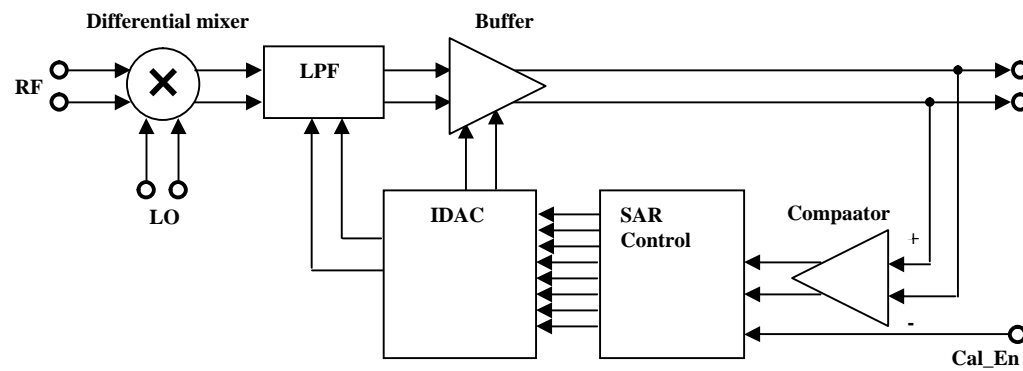


Figure 6.42 Block diagram of DC offset calibration
(SAR: Successive Approximation Register)

* **Hardware scheme**

 


Figure 6.43 DC offset cancelled by the combination of a low frequency amplifier and a LPF.

射频和天线设计培训课程推荐

易迪拓培训(www.edatop.com)由数名来自于研发第一线的资深工程师发起成立,致力并专注于微波、射频、天线设计研发人才的培养;我们于 2006 年整合合并微波 EDA 网(www.mweda.com),现已发展成为国内最大的微波射频和天线设计人才培养基地,成功推出多套微波射频以及天线设计经典培训课程和 ADS、HFSS 等专业软件使用培训课程,广受客户好评;并先后与人民邮电出版社、电子工业出版社合作出版了多本专业图书,帮助数万名工程师提升了专业技术能力。客户遍布中兴通讯、研通高频、埃威航电、国人通信等多家国内知名公司,以及台湾工业技术研究院、永业科技、全一电子等多家台湾地区企业。

易迪拓培训课程列表: <http://www.edatop.com/peixun/rfe/129.html>



射频工程师养成培训课程套装

该套装精选了射频专业基础培训课程、射频仿真设计培训课程和射频电路测量培训课程三个类别共 30 门视频培训课程和 3 本图书教材;旨在引领学员全面学习一个射频工程师需要熟悉、理解和掌握的专业知识和研发设计能力。通过套装的学习,能够让学员完全达到和胜任一个合格的射频工程师的要求...

课程网址: <http://www.edatop.com/peixun/rfe/110.html>

ADS 学习培训课程套装

该套装是迄今国内最全面、最权威的 ADS 培训教程,共包含 10 门 ADS 学习培训课程。课程是由具有多年 ADS 使用经验的微波射频与通信系统设计领域资深专家讲解,并多结合设计实例,由浅入深、详细而又全面地讲解了 ADS 在微波射频电路设计、通信系统设计和电磁仿真设计方面的内容。能让您在最短的时间内学会使用 ADS,迅速提升个人技术能力,把 ADS 真正应用到实际研发工作中去,成为 ADS 设计专家...



课程网址: <http://www.edatop.com/peixun/ads/13.html>



HFSS 学习培训课程套装

该套课程套装包含了本站全部 HFSS 培训课程,是迄今国内最全面、最专业的 HFSS 培训教程套装,可以帮助您从零开始,全面深入学习 HFSS 的各项功能和在多个方面的工程应用。购买套装,更可超值赠送 3 个月免费学习答疑,随时解答您学习过程中遇到的棘手问题,让您的 HFSS 学习更加轻松顺畅...

课程网址: <http://www.edatop.com/peixun/hfss/11.html>

CST 学习培训课程套装

该培训套装由易迪拓培训联合微波 EDA 网共同推出,是最全面、系统、专业的 CST 微波工作室培训课程套装,所有课程都由经验丰富的专家授课,视频教学,可以帮助您从零开始,全面系统地学习 CST 微波工作的各项功能及其在微波射频、天线设计等领域的设计应用。且购买该套装,还可超值赠送 3 个月免费学习答疑...

课程网址: <http://www.edatop.com/peixun/cst/24.html>



HFSS 天线设计培训课程套装

套装包含 6 门视频课程和 1 本图书,课程从基础讲起,内容由浅入深,理论介绍和实际操作讲解相结合,全面系统的讲解了 HFSS 天线设计的全过程。是国内最全面、最专业的 HFSS 天线设计课程,可以帮助您快速学习掌握如何使用 HFSS 设计天线,让天线设计不再难...

课程网址: <http://www.edatop.com/peixun/hfss/122.html>

13.56MHz NFC/RFID 线圈天线设计培训课程套装

套装包含 4 门视频培训课程,培训将 13.56MHz 线圈天线设计原理和仿真设计实践相结合,全面系统地讲解了 13.56MHz 线圈天线的工作原理、设计方法、设计考量以及使用 HFSS 和 CST 仿真分析线圈天线的具体操作,同时还介绍了 13.56MHz 线圈天线匹配电路的设计和调试。通过该套课程的学习,可以帮助您快速学习掌握 13.56MHz 线圈天线及其匹配电路的原理、设计和调试...

详情浏览: <http://www.edatop.com/peixun/antenna/116.html>



我们的课程优势:

- ※ 成立于 2004 年,10 多年丰富的行业经验,
- ※ 一直致力并专注于微波射频和天线设计工程师的培养,更了解该行业对人才的要求
- ※ 经验丰富的一线资深工程师讲授,结合实际工程案例,直观、实用、易学

联系我们:

- ※ 易迪拓培训官网: <http://www.edatop.com>
- ※ 微波 EDA 网: <http://www.mweda.com>
- ※ 官方淘宝店: <http://shop36920890.taobao.com>