



Measurement of S11 & S12

(1) Apply input to Port 1 , terminate at Port 2 with a Matched Load $\therefore a_2 = 0$.

$$\therefore S_{11} = \left. \frac{b_1}{a_1} \right)_{a_2=0} = \text{reflection coefficient at Port 1 (matched load at Port 2).}$$

$$S_{21} = \left. \frac{b_2}{a_1} \right)_{a_2=0} = \text{Voltage transfer ratio Port 1 to Port 2 (matched load at Port 2).}$$

(2) Apply input to Port 2 , terminate at Port 1 with a matched load $\therefore a_1 = 0$.

$$\therefore S_{22} = \left. \frac{b_2}{a_2} \right)_{a_1=0} = \text{reflection coefficient at Port 2 (matched load at Port 1).}$$

$$S_{12} = \left. \frac{b_1}{a_2} \right)_{a_1=0} = \text{transfer ratio Port 2 to Port 1 (matched load at Port 1).}$$

Note each S matrix element is in general complex eg

$$S_{i,j} = \left| S_{i,j} \right| e^{j\theta_{i,j}}$$

ratio of amplitudes phase difference of signals


$$\text{eg } S_{11} = 0.9 \angle -37 \equiv 0.9e^{j(-37)}$$

$$S_{21} = 4.0 \angle 127$$

Note S11,S22 are reflection coefficients \therefore can plot these on a Smith Chart.

S12,S21 are not reflection coefficients and are usually plotted on a Polar diagram.

Change of reference plane

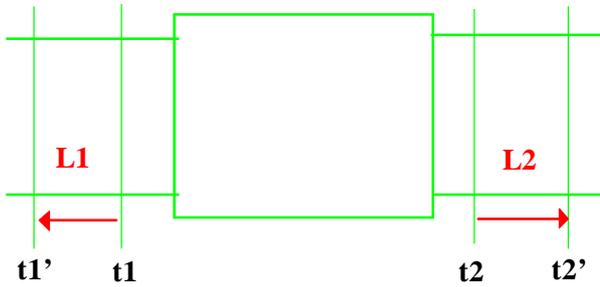

Note positive signs for L1 & L2 are taken to be movements away from the device

Planes t1' and t2'


$$S_{11}' = S_{11} e^{-j2\beta L1} \quad S_{22}' = S_{22} e^{-j2\beta L2}$$

\uparrow \uparrow
 t1', t2' t1, t2


$$S_{21}' = S_{21} e^{-j\beta(L1 + L2)} \quad S_{12} = S_{12} e^{-j\beta(L1 + L2)}$$

S Matrix for simple elements

Series normalised impedance

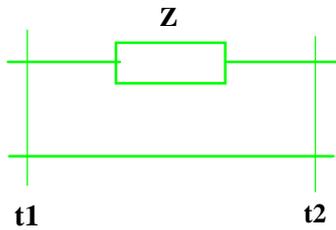


(1) Connect a matched load at t2 ie

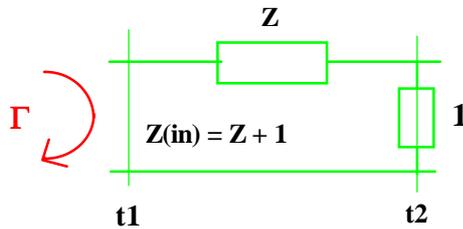

$$\Gamma = \frac{Z_{(in)} - Z_0}{Z_{(in)} + Z_0} = \frac{Z_{(in)} - 1}{Z_{(in)} + 1} = \frac{z + 1 - 1}{z + 1 + 1} = \frac{z}{z + 2} = S_{11}$$

divide by Z_0
to normalise
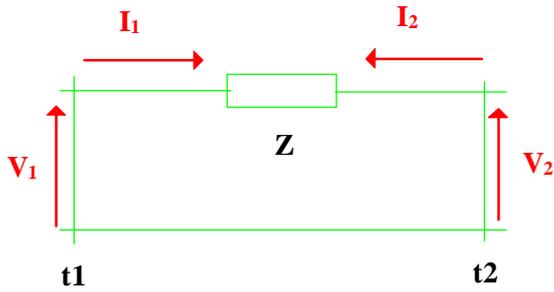
$$S_{11} = S_{22} \text{ (By symmetry)} = \underline{\underline{\frac{z}{z + 2}}}$$



$$\left. \begin{array}{ll} V_1 = a_1 + b_1 & V_2 = a_2 + b_2 \\ I_1 = a_1 - b_1 & I_2 = a_2 - b_2 \end{array} \right\} \text{General}$$

Series connection $\therefore I_2 = -I_1$.

$$\therefore a_2 - b_2 = -(a_1 - b_1)$$

Matched load @ Port 2 $a_2 = 0$


$$\therefore b_2 = a_1 - b_1$$

$$\therefore \left. \frac{b_2}{a_1} \right|_{a_2=0} = 1 - \frac{b_1}{a_1} = 1 - S_{11} \equiv S_{21}$$

$$S_{21} = 1 - S_{11} = 1 - \frac{z}{z+2} = \frac{2}{z+2} = S_{12} \text{ (by symmetry)}$$

$$\frac{z+2}{z+2} - \frac{z}{z+2} = \frac{\cancel{z} + 2}{z+2}$$

Shunt normalised Admittance

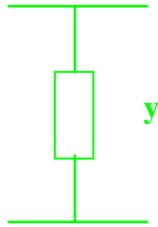


$$\text{Let } z = \frac{1}{y}$$

$$\therefore z_{in} = \frac{\frac{1}{y} \cdot 1}{\frac{1}{y} + 1} = \frac{\frac{1}{y}}{\frac{1}{y} + 1} \quad \text{x top \& bottom by } y$$

$$\frac{1}{y+1} = Z_{in}$$

$$\Gamma = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{\frac{1}{y+1} - 1}{\frac{1}{y+1} + 1} \quad \text{x top \& bottom by } y+1$$
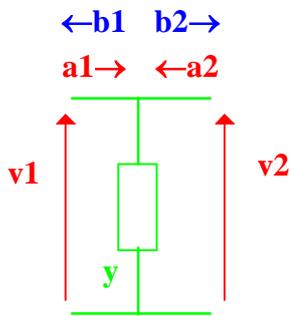
$$\frac{1 - y + 1}{1 + y + 1} = \frac{-y}{2 + y}$$



$$V_1 = V_2$$

$$\therefore a_2 + b_2 = a_1 + b_1$$


$$\text{matched load on Port 2 } \therefore a_2 = 0$$

$$S_{21} = \frac{b_2}{a_1} = \frac{a_1 + b_1}{a_1} = 1 + S_{11}$$

$$1 + \frac{-y}{2+y} = \frac{2+y}{2+y} + \frac{-y}{2+y} = \frac{2}{2+y} = S_{21}$$



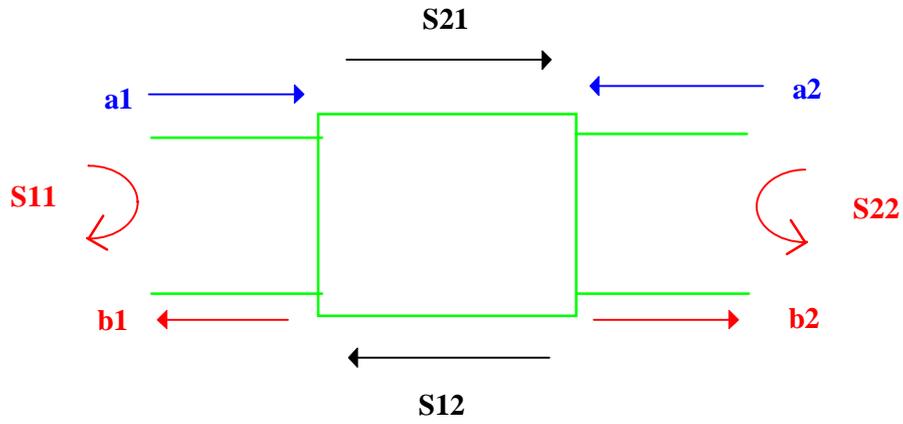S Parameters for a reciprocal, lossless network



At Port 1 Power in $|a_1|^2$

Power out $|b_1|^2$

\therefore Net power in $|a_1|^2 - |b_1|^2$



Reciprocal network

$$S_{21} = S_{12} \text{ (generally } S_{ij} = S_{ji} \text{)}$$

For a lossless network Power out = Power in

$$\sum_{\text{Port } i} |b_i|^2 = \sum_{\text{Port } i} |a_i|^2$$

$\Rightarrow [S]$ is a unitary matrix

$$\sum_{\text{Port } i} S_{i,s} \cdot S_{i,r}^* = \delta_{s,r} = 1 \quad \text{if } s=r$$

$$= 0 \quad \text{if } s \neq r$$

2port $i=1,2$ $s,r=1 \& 2$

$$S=1, r=1 \quad S_{11} \cdot S_{11}^* + S_{21} \cdot S_{21}^* = 1$$

$$|S_{11}|^2 + |S_{21}|^2 = 1$$

$$\therefore |S_{21}| = \sqrt{1 - |S_{11}|^2}$$

$$S=2, r=2 \quad S_{12} \cdot S_{12}^* + S_{22} \cdot S_{22}^* = 1$$

$$|S_{12}|^2 + |S_{22}|^2 = 1$$

$$\therefore |S_{12}| = \sqrt{1 - |S_{22}|^2}$$

If the junction is reciprocal $\therefore |S_{12}| = |S_{21}| \quad \therefore |S_{22}| = |S_{11}|$



$$S = 1; r = 2 \quad S_{11} \cdot S_{12}^* + S_{21} \cdot S_{22}^* = 0$$

$$|S_{11}| e^{j\theta_{11}} \times |S_{12}| e^{-j\theta_{12}} + |S_{21}| e^{j\theta_{21}} \times |S_{22}| e^{-j\theta_{22}} = 0$$

$$\Rightarrow e^{j(\theta_{12} + \theta_{21})} = -e^{j(\theta_{11} + \theta_{22})}$$

$$\theta_{12} = \theta_{21} \quad (\text{reciprocal})$$

$$e^{j(2\theta_{12})} = -e^{j(\theta_{11} + \theta_{22})}$$

$$\cos 2\theta_{12} = -\cos(\theta_{11} + \theta_{22})$$


$$\sin 2\theta_{12} = -\sin(\theta_{11} + \theta_{22})$$

$$\Rightarrow \theta_{12} = \theta_{21} = \underline{\underline{\frac{1}{2}(\theta_{11} + \theta_{22}) + \frac{\pi}{2} \pm m\pi}} \quad m = 0, 1, 2, \dots$$

∴ For a reciprocal lossless 2 - port network we only need

$$|S_{11}|, \theta_{11} \text{ \& \ } \theta_{22}$$

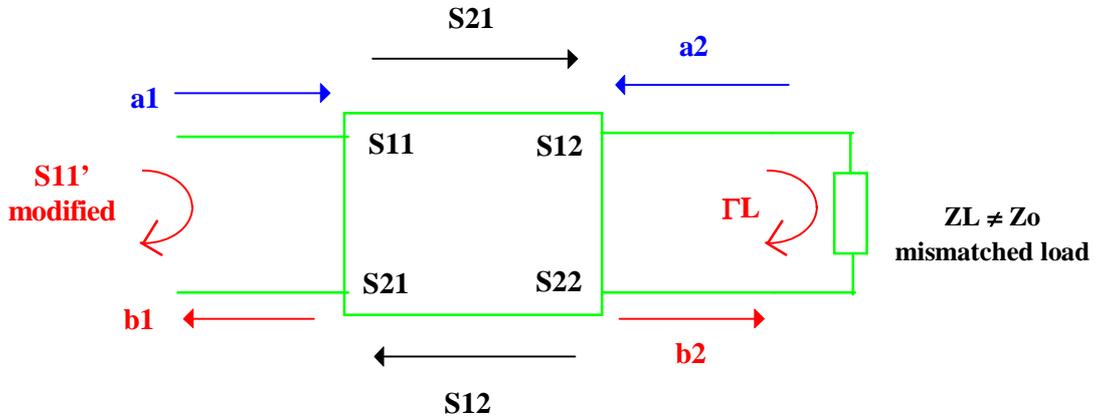Modified S Parameters - mismatched source & load



$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} \quad \Gamma_L = \frac{a_2}{b_2} \quad \therefore a_2 = b_2 \cdot \Gamma_L$$

$$b_1 = S_{11} \cdot a_1 + S_{12} \cdot a_2 = S_{11} \cdot a_1 + S_{12} \cdot b_2 \cdot \Gamma_L$$

$$b_2 = S_{21} \cdot a_1 + S_{22} \cdot a_2 = S_{21} \cdot a_1 + S_{22} \cdot b_2 \cdot \Gamma_L$$

$$S_{11}' = \frac{b_1}{a_1} \quad ; \quad S_{21}' = \frac{b_2}{a_1}$$

$$S_{21}' = \frac{b_2}{a_1} = \frac{S_{21} \cdot a_1 + S_{22} \cdot b_2 \cdot \Gamma_L}{a_1} \quad \text{rearrange gives} \quad \frac{b_2}{a_1} - \frac{S_{22} \cdot b_2 \cdot \Gamma_L}{a_1} = \frac{S_{21} \cdot a_1}{a_1}$$


$$S_{21}' (1 - S_{22} \cdot \Gamma_L) = S_{21} \quad \therefore S_{21}' = \frac{S_{21}}{1 - S_{22} \cdot \Gamma_L}$$

$$b_1 = S_{11} \cdot a_1 + S_{12} \cdot \Gamma_L \cdot \left(\frac{S_{21}}{1 - S_{22} \cdot \Gamma_L} \right) \cdot a_1 \quad (\text{divide by } a_1 \text{ on both sides})$$

$$S_{11}' = S_{11} + \frac{S_{21} \cdot S_{12} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$



Mismatched Source

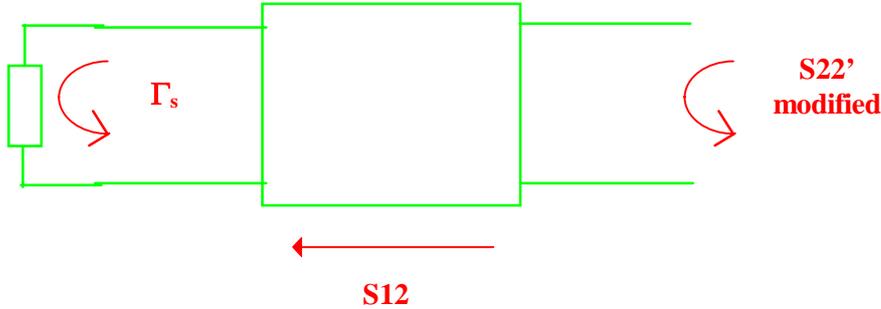


$$S_{22}' = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_s}{1 - S_{11} \cdot \Gamma_s}$$

$$S_{12}' = \frac{S_{12}}{1 - S_{11} \cdot \Gamma_s}$$

Circuit performance from S Parameters

Reflection characteristics:-

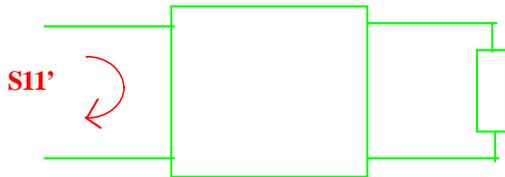


Input V.S.W.R = $\frac{1 + |S_{11}'|}{1 - |S_{11}'|}$ **modulus**

Return Loss (dB) = $10 \cdot \text{Log}_{10} \frac{\text{Power in}}{\text{Power reflected}}$

$$= 10 \cdot \text{Log}_{10} \frac{|a_1|^2}{|b_1|^2} = -20 \cdot \text{log}_{10} |S_{11}'|$$

$\frac{Z_{(in)}}{Z_o} = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 + S_{11}'}{1 - S_{11}'}$ **complex**

Multiple Reflection Effects

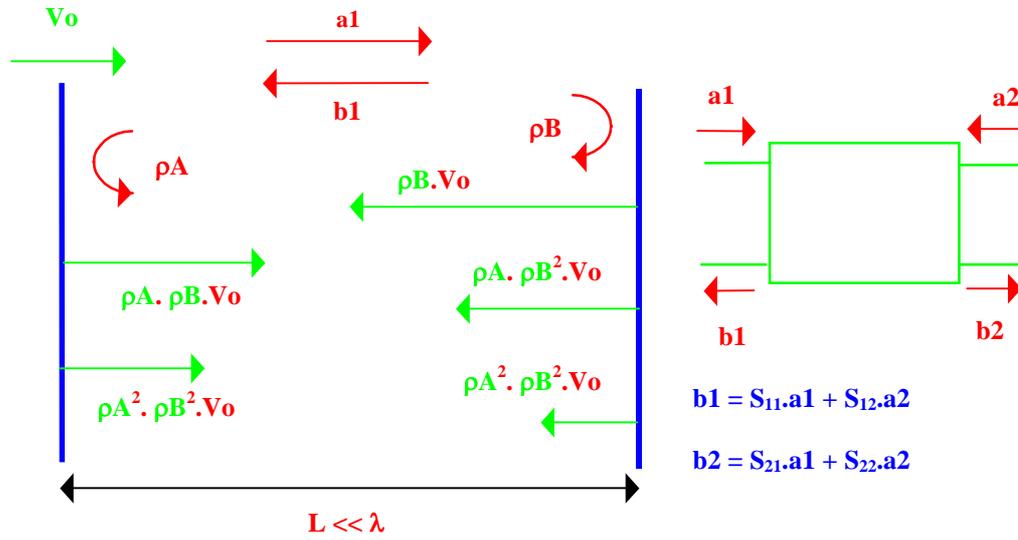

$$b1 = \rho_B.V_B + \rho_A.\rho_B^2 + \rho_A^2.\rho_B^2.V_o + \dots$$

$$= \rho_B.V_o[1 + \rho_A.\rho_B + (\rho_A.\rho_B)^2 + \dots]$$

$$b1 = \frac{\rho_B.V_o}{1 - \rho_A.\rho_B} \quad \rho_B = \frac{b1}{a1} \quad \therefore a1 = \frac{b1}{\rho_B}$$

$$\therefore a1 = \frac{V_o}{(1 - \rho_A.\rho_B)}$$

射频和天线设计培训课程推荐

易迪拓培训(www.edatop.com)由数名来自于研发第一线的资深工程师发起成立,致力并专注于微波、射频、天线设计研发人才的培养;我们于 2006 年整合合并微波 EDA 网(www.mweda.com),现已发展成为国内最大的微波射频和天线设计人才培养基地,成功推出多套微波射频以及天线设计经典培训课程和 ADS、HFSS 等专业软件使用培训课程,广受客户好评;并先后与人民邮电出版社、电子工业出版社合作出版了多本专业图书,帮助数万名工程师提升了专业技术能力。客户遍布中兴通讯、研通高频、埃威航电、国人通信等多家国内知名公司,以及台湾工业技术研究院、永业科技、全一电子等多家台湾地区企业。

易迪拓培训课程列表: <http://www.edatop.com/peixun/rfe/129.html>



射频工程师养成培训课程套装

该套装精选了射频专业基础培训课程、射频仿真设计培训课程和射频电路测量培训课程三个类别共 30 门视频培训课程和 3 本图书教材;旨在引领学员全面学习一个射频工程师需要熟悉、理解和掌握的专业知识和研发设计能力。通过套装的学习,能够让学员完全达到和胜任一个合格的射频工程师的要求...

课程网址: <http://www.edatop.com/peixun/rfe/110.html>

ADS 学习培训课程套装

该套装是迄今国内最全面、最权威的 ADS 培训教程,共包含 10 门 ADS 学习培训课程。课程是由具有多年 ADS 使用经验的微波射频与通信系统设计领域资深专家讲解,并多结合设计实例,由浅入深、详细而又全面地讲解了 ADS 在微波射频电路设计、通信系统设计和电磁仿真设计方面的内容。能让您在最短的时间内学会使用 ADS,迅速提升个人技术能力,把 ADS 真正应用到实际研发工作中去,成为 ADS 设计专家...



课程网址: <http://www.edatop.com/peixun/ads/13.html>



HFSS 学习培训课程套装


该套课程套装包含了本站全部 HFSS 培训课程,是迄今国内最全面、最专业的 HFSS 培训教程套装,可以帮助您从零开始,全面深入学习 HFSS 的各项功能和在多个方面的工程应用。购买套装,更可超值赠送 3 个月免费学习答疑,随时解答您学习过程中遇到的棘手问题,让您的 HFSS 学习更加轻松顺畅...

课程网址: <http://www.edatop.com/peixun/hfss/11.html>

CST 学习培训课程套装

该培训套装由易迪拓培训联合微波 EDA 网共同推出,是最全面、系统、专业的 CST 微波工作室培训课程套装,所有课程都由经验丰富的专家授课,视频教学,可以帮助您从零开始,全面系统地学习 CST 微波工作的各项功能及其在微波射频、天线设计等领域的设计应用。且购买该套装,还可超值赠送 3 个月免费学习答疑...

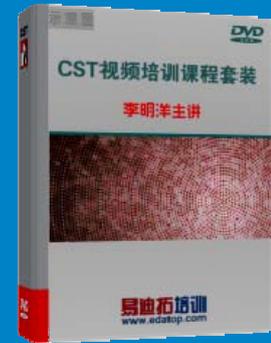课程网址: <http://www.edatop.com/peixun/cst/24.html>



HFSS 天线设计培训课程套装

套装包含 6 门视频课程和 1 本图书,课程从基础讲起,内容由浅入深,理论介绍和实际操作讲解相结合,全面系统的讲解了 HFSS 天线设计的全过程。是国内最全面、最专业的 HFSS 天线设计课程,可以帮助您快速学习掌握如何使用 HFSS 设计天线,让天线设计不再难...

课程网址: <http://www.edatop.com/peixun/hfss/122.html>

13.56MHz NFC/RFID 线圈天线设计培训课程套装

套装包含 4 门视频培训课程,培训将 13.56MHz 线圈天线设计原理和仿真设计实践相结合,全面系统地讲解了 13.56MHz 线圈天线的工作原理、设计方法、设计考量以及使用 HFSS 和 CST 仿真分析线圈天线的具体操作,同时还介绍了 13.56MHz 线圈天线匹配电路的设计和调试。通过该套课程的学习,可以帮助您快速学习掌握 13.56MHz 线圈天线及其匹配电路的原理、设计和调试...

详情浏览: <http://www.edatop.com/peixun/antenna/116.html>



我们的课程优势:

- ※ 成立于 2004 年,10 多年丰富的行业经验,
- ※ 一直致力并专注于微波射频和天线设计工程师的培养,更了解该行业对人才的要求
- ※ 经验丰富的一线资深工程师讲授,结合实际工程案例,直观、实用、易学

联系我们:

- ※ 易迪拓培训官网: <http://www.edatop.com>
- ※ 微波 EDA 网: <http://www.mweda.com>
- ※ 官方淘宝店: <http://shop36920890.taobao.com>